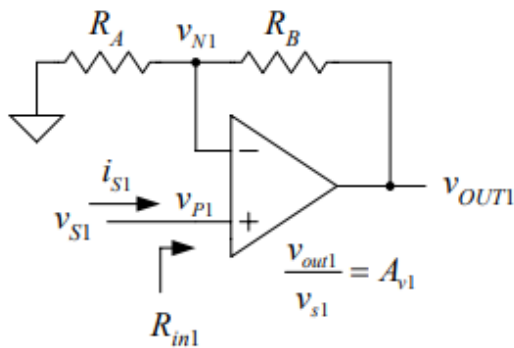


**Lab Number 2**  
**EEE 108L – Electronics I - Laboratory**  
**Introduction to Operational Amplifiers (One Week)**


**Background**

The purpose of this experiment is to provide the students an introduction to operational amplifiers. The basic amplifier circuits are shown in the figures below. These circuits will be constructed using a 741 or similar op-amp and  $\pm 5$  V. The lab consists of three different parts:



**1) Preliminary Calculations 2) Spice Simulations 3) Laboratory Experiments**



**Figure 1. Non-Inverting Amplifier**

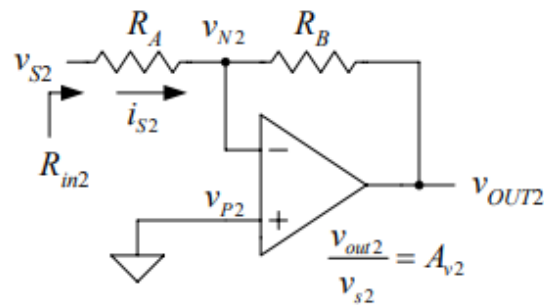

**Figure 2. Inverting Amplifier**

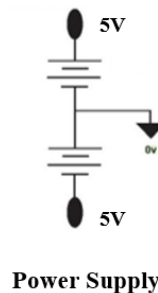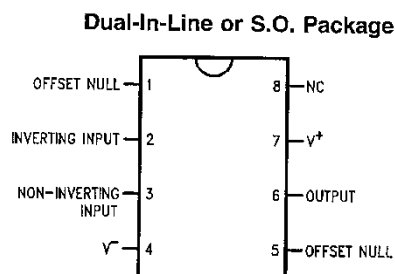

**Preliminary Calculations:**

For this lab, apply  $\pm 5$  V supplies.

- 1.** Write an expression for the voltage gain  $A_{v1} = \frac{v_{out}}{v_{s1}}$  in terms of  $R_A$  and  $R_B$ .
- 2.** Select a standard resistor value for  $R_A$  such that  $3.3\text{k}\Omega \leq R_A \leq 15\text{k}\Omega$  and select  $R_B$  such that the gain calculated from the standard resistor values is given  $A_{v1} = 3 \frac{v}{v} \pm 10\%$ .
- 3.** Calculate the input resistance  $R_{in1} = \frac{v_{s1}}{i_{s1}}$  of the circuit in Figure 1.
- 4.** Calculate the voltage  $V_{N1}$ .
- 5.** Write an expression for the voltage gain  $A_{v2} = \frac{v_{out2}}{v_{s2}}$  in terms of  $R_A$  and  $R_B$ .
- 6.** Using the same value for  $R_A$  and  $R_B$  as in step 1, calculate the gain  $A_{v2}$ .
- 7.** Calculate the input resistance  $R_{in2} = \frac{v_{s2}}{i_{s2}}$  of the circuit in Figure 2.
- 8.** Calculate the voltage  $V_{N2}$ .

### Spice Simulations:

1. Enter the circuit of Figure 1 into PSpice. Use the resistor values determined in preliminary calculation. Use 741 model for the operational amplifier and  $\pm 5V$  power supplies.  
Use input source Vsin:  $V_{off}=0V$ ,  $V_{amp}=0.5V$ ,  $F_{req.}=1K$  and  $AC=1$
2. Perform a DC sweep simulation in which  $v_{s1}$  is swept over from  $-5V$  to  $+5V$ .
3. Identify  $V_{outmax}$  and  $V_{outmin}$  on the plot.
4. In the range for which amplifier is not saturated and is functioning as a linear amplifier, determine the slope of the transfer characteristic  $\frac{\Delta V_{out1}}{\Delta V_{s1}}$ .
5. Enter the circuit of Figure 2 into PSpice. Use the resistor values determined in preliminary calculation. Use 741 model for the operational amplifier and  $\pm 5V$  power supplies.
6. Perform a DC sweep simulation in which  $v_{s2}$  is swept from  $-5V$  to  $+5V$ .
7. Identify  $V_{outmax}$  and  $V_{outmin}$  on the plot.
8. In the range for which amplifier is not saturated and is functioning as a linear amplifier, determine the slope of the transfer characteristic  $\frac{\Delta V_{out2}}{\Delta V_{s2}}$ .
9. Obtain a plot of  $i_{s2}$  as a function of  $v_{s2}$ .
10. Determine  $\frac{\Delta V_{s2}}{\Delta i_{s2}}$  in the linear range and compare that value with the calculated value of  $R_{in2}$ .
11. Are  $V_{outmax}$  and  $V_{outmin}$  are same for both circuits?
12. Consider the assumption that  $V_N = V_P$ . Does the assumption hold when the output is saturated?
13. For the circuit, change  $v_{s2}$  to a sine wave and observe the waveform at  $v_{OUT2}$  for:  
Amplitude:  $0.5V$ ,  $1.5V$  and  $3V$ . (Run Transient Analysis)
14. Discuss the three outputs plots.

### Laboratory Measurements:

1. Construct the circuit of Figure 1, using the same resistor values and a  $\pm 5V$  power supply.
2. Ground the node labeled  $v_{s1}$  and record  $v_{OUT1}$ .
3. Find offset voltage  $V_{OS} = V_{out1}/Gain$ . The condition  $-3mV < V_{OS} < 3mV$  should be satisfied.
4. Connect  $v_{s1}$  to an AC signal source and adjust it so that  $v_{s1}$  is a  $1V_{pp}$ ,  $1KHz$  triangle wave with zero DC offset.
5. Plot the waveforms of  $v_{s1}$  and  $v_{OUT1}$  and calculate the small-signal gain  $\frac{v_{out1}}{v_{s1}}$  and compare this to the value calculated before.
6. Increase/decrease the input signal amplitude until clipping at the output is obvious, record the voltage corresponding to the positive and negative output clipping levels.
7. Verify that these are the same as  $v_{OUTmax}$  and  $v_{OUTmin}$  measured before.
8. Construct the inverting amplifier circuit of Figure 2 using the same resistors and power supply voltages as before.
9. Adjust the signal source so that  $v_{s2}$  is a  $1V_{pp}$ ,  $1KHz$  triangle wave with zero DC offset.
10. Plot the waveforms of  $v_{s2}$  and  $v_{OUT2}$  and calculate the small-signal gain  $\frac{v_{out2}}{v_{s2}}$  and compare this to the value calculated before.
11. Increase / decrease the input signal amplitude until clipping at the output is obvious, record the voltage corresponding to the positive and negative output clipping levels.
12. Verify that these are the same as  $v_{OUTmax}$  and  $v_{OUTmin}$  measured before.
13. For the circuit, change  $v_{s2}$  to a sine wave and observe the waveform at  $v_{OUT2}$ .