

CALIFORNIA STATE UNIVERSITY SACRAMENTO



DEPARTMENT OF ELECTRICAL AND ELECTRONIC ENGINEERING

EEE 117 Network Analysis


Text: Electric Circuits by J. Nilsson and S. Riedel Prentice Hall

Examples Set 4: Laplace Transform in Circuit Analysis

Instructor: Riaz Ahmad

Ex-1: The circuit shown below is driven by a voltage source whose voltage increases linearly with time, namely $v_g = 50 t$

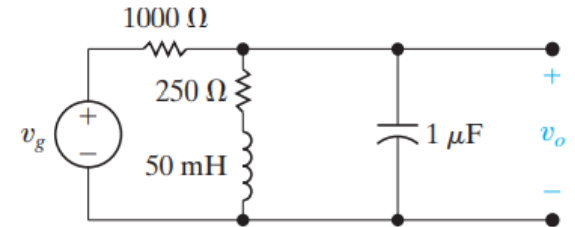- Use the transfer function to find v_o .
- Identify the transient component of the response.
- Identify the steady-state component of the response.
- Sketch v_o versus t for $0 \leq t \leq 1.5$ ms.



$$H(s) = \frac{1000(s + 5000)}{s^2 + 6000s + 25 \times 10^6}.$$

The transform of the driving voltage is $50/s^2$; therefore, the s -domain expression for the output voltage is

$$V_o = \frac{1000(s + 5000)}{(s^2 + 6000s + 25 \times 10^6)} \frac{50}{s^2}.$$

The partial fraction expansion of V_o is

$$V_o = \frac{K_1}{s + 3000 - j4000} + \frac{K_1^*}{s + 3000 + j4000} + \frac{K_2}{s^2} + \frac{K_3}{s}.$$

$$K_1 = 5\sqrt{5} \times 10^{-4} \angle 79.70^\circ;$$

$$K_1^* = 5\sqrt{5} \times 10^{-4} \angle -79.70^\circ,$$

$$K_2 = 10,$$

$$K_3 = -4 \times 10^{-4}.$$

The time-domain expression for v_o is

$$v_o = [10\sqrt{5} \times 10^{-4} e^{-3000t} \cos(4000t + 79.70^\circ) \\ + 10t - 4 \times 10^{-4}] u(t) \text{ V.}$$

b) The transient component of v_o is


$$10\sqrt{5} \times 10^{-4} e^{-3000t} \cos(4000t + 79.70^\circ).$$

Note that this term is generated by the poles $(-3000 + j4000)$ and $(-3000 - j4000)$ of the transfer function.

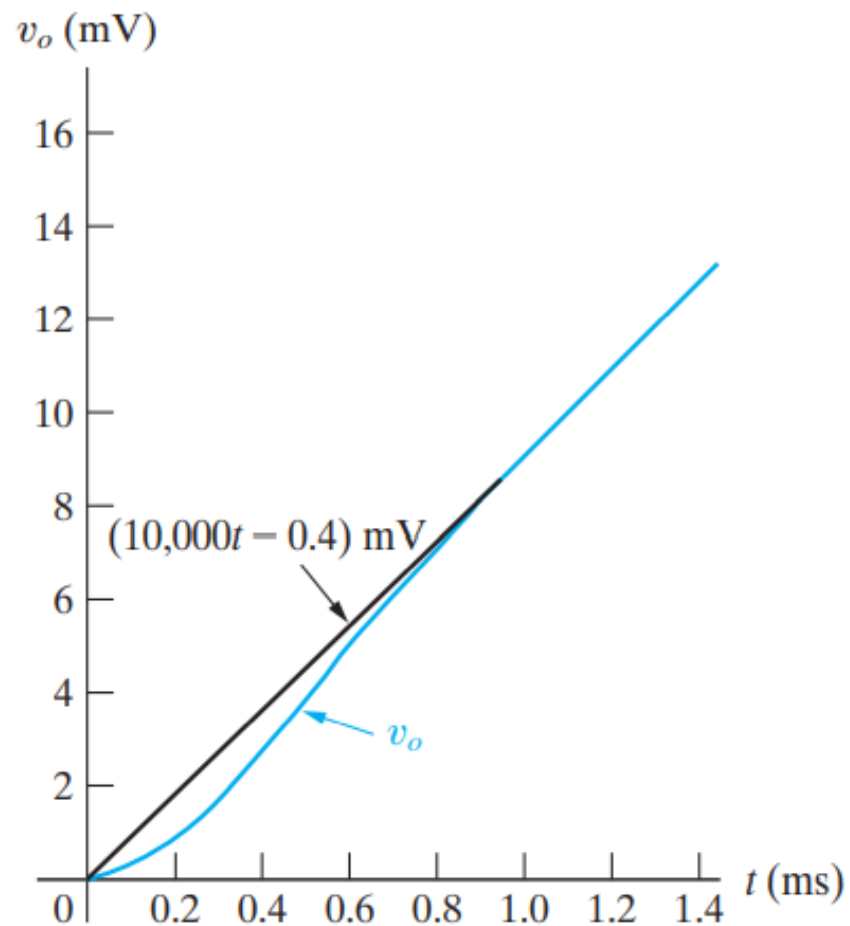
c) The steady-state component of the response is

$$(10t - 4 \times 10^{-4})u(t).$$

These two terms are generated by the second-order pole (K/s^2) of the driving voltage.



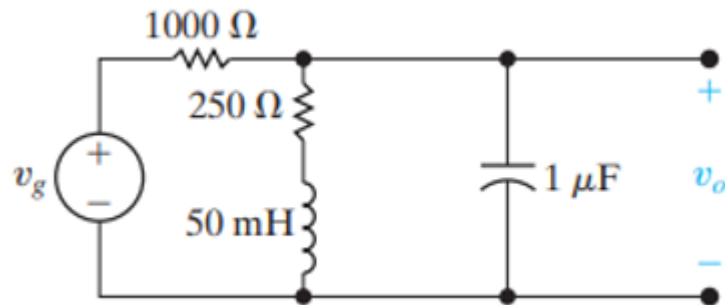Ex-2: For the circuit shown below, the sinusoidal source voltage is $120 \cos(5000t + 30^\circ)$ V. Find the steady-state expression for v_o .



From previous example, $H(s) = \frac{1000(s + 5000)}{s^2 + 6000s + 25 * 10^6}$

The frequency of the voltage source is 5000 rad/s;
hence we evaluate $H(s)$ at $H(j5000)$:


$$H(j5000) = \frac{1000(5000 + j5000)}{-25 * 10^6 + j5000(6000) + 25 \times 10^6}$$

$$= \frac{1 + j1}{j6} = \frac{1 - j1}{6} = \frac{\sqrt{2}}{6} \angle -45^\circ.$$

$$v_{o_{ss}} = \frac{(120)\sqrt{2}}{6} \cos(5000t + 30^\circ - 45^\circ)$$

$$= 20\sqrt{2} \cos(5000t - 15^\circ) \text{ V.}$$

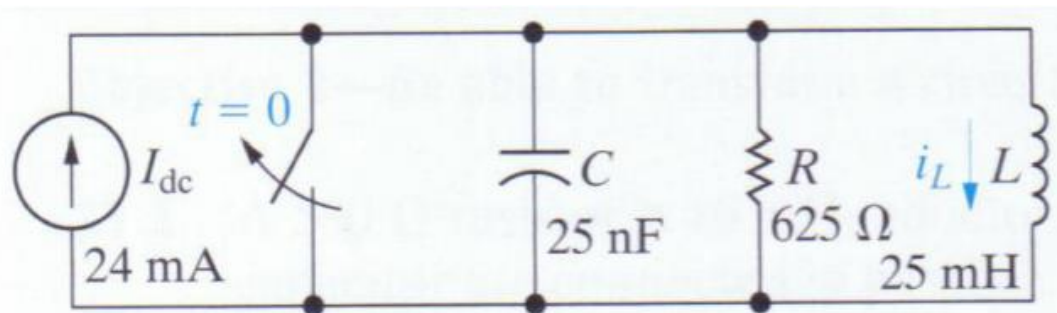Ex-3: Step Response of a Parallel RLC Circuit.



Find the current i_L through the inductor for $t > 0$.

Assume that the switch has been closed for “a long time”.

What are the initial conditions? $v_C(t < 0) = 0$


$$i_L(t < 0) = 0$$

$$v_R(t < 0) = 0$$

$$I_{DC}u(t) \Leftrightarrow \frac{I_{DC}}{s}$$

$$Z_C = \frac{1}{sC}$$

$$Z_L = sL$$

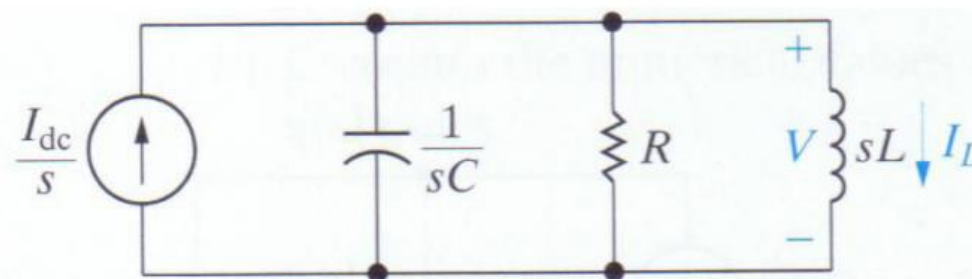

Apply KCL:

$$-\frac{I_{DC}}{s} + \frac{V}{Z_C} + \frac{V}{R} + \frac{V}{Z_L} = 0$$

$$V \left(\frac{1}{\frac{1}{sC}} + \frac{1}{R} + \frac{1}{sL} \right) = \frac{I_{DC}}{s}$$

$$V = \frac{I_{DC}}{s \left(sC + \frac{1}{R} + \frac{1}{sL} \right)} = \frac{\frac{I_{DC}}{C}}{s^2 + s \frac{1}{RC} + \frac{1}{LC}}$$

Now we can write the current I_L as

$$I_L = \frac{V}{sL} = \frac{1}{sL} \frac{\frac{I_{DC}}{C}}{s^2 + s \frac{1}{RC} + \frac{1}{LC}} = \frac{\frac{I_{DC}}{LC}}{s \left(s^2 + s \frac{1}{RC} + \frac{1}{LC} \right)}$$

$$\frac{I_{DC}}{LC} = \frac{24 \times 10^{-3}}{(25 \times 10^{-3})(25 \times 10^{-9})} = 384 \times 10^5$$

$$\frac{1}{RC} = \frac{1}{(625)(25 \times 10^{-3})} = 64,000$$

$$\frac{1}{LC} = \frac{1}{(25 \times 10^{-3})(25 \times 10^{-9})} = 16 \times 10^8$$

$$I_L = \frac{384 \times 10^5}{s(s^2 + 64,000s + 16 \times 10^8)}$$

Now find the partial fraction expansion.

$$\frac{384 \times 10^5}{s(s^2 + 64,000s + 16 \times 10^8)} = \frac{A}{s} + \frac{B}{s + 32,000 - j24,000} + \frac{B^*}{s + 32,000 + j24,000}$$

$$A = \frac{384 \times 10^5}{s^2 + 64,000s + 16 \times 10^8} \Big|_{s=0} = \frac{384 \times 10^5}{16 \times 10^8} = 24 \times 10^{-3}$$

$$\begin{aligned} B &= \frac{384 \times 10^5}{s(s + 32,000 + j24,000)} \Big|_{s=-32,000+j24,000} \\ &= \frac{384 \times 10^5}{(-32,000 + j24,000)(-32,000 + j24,000 + 32,000 + j24,000)} \\ &= \frac{384 \times 10^5}{(-32,000 + j24,000)(j48,000)} = \frac{384 \times 10^5}{-1.152 \times 10^9 - j1.536 \times 10^9} \\ &= \frac{384 \times 10^5}{1.92 \times 10^9 \angle -126.87^\circ} = 20 \times 10^{-3} \angle 126.87^\circ \end{aligned}$$

The PFE is

$$I_L = \frac{24 \times 10^{-3}}{s} + \frac{20 \times 10^{-3} \angle 126.87^\circ}{s + 32,000 - j24,000} + \frac{20 \times 10^{-3} \angle -126.87^\circ}{s + 32,000 + j24,000}$$


So now write $i_L(t)$ from the inverse Laplace transform. I will write the current in terms of milli Amps.

$$\begin{aligned} i_L(t) &= \left[24 + 2(20e^{-32,000t} \cos(24,000t + 126.87^\circ)) \right] u(t) \text{ mA} \\ &= \left[24 + 40e^{-32,000t} \cos(24,000t + 126.87^\circ) \right] u(t) \text{ mA} \end{aligned}$$

$$\frac{K \angle \theta}{s + \alpha - j\beta} + \frac{K \angle -\theta}{s + \alpha + j\beta} \Leftrightarrow 2|K|e^{-\alpha t} \cos(\beta t + \theta)$$

Ex-4: A $500\ \Omega$ resistor, a 16 mH inductor, and a 25 nF capacitor are connected in parallel. Find the zeros and poles.

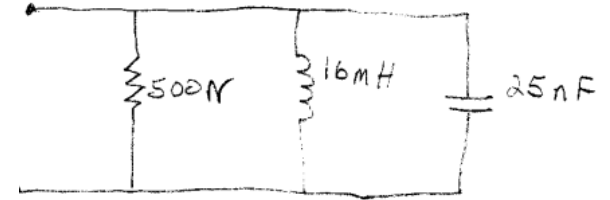Analyze the circuit and find the zeros and poles.



Admittance is given by

$$Y = \frac{1}{Z} = \frac{1}{R} + \frac{1}{sL} + \frac{1}{\frac{1}{sC}} = \frac{1}{R} + \frac{1}{sL} + sC$$
$$= \frac{\frac{s}{R} + \frac{1}{L} + s^2 C}{s} = \frac{C \left(\frac{s}{RC} + \frac{1}{LC} + s^2 \right)}{s} = \frac{C \left(s^2 + s \frac{1}{RC} + \frac{1}{LC} \right)}{s}$$

Now find the numeric result.

$$\frac{1}{RC} = \frac{1}{(500\Omega)(25 \times 10^{-9} F)} = 80,000 \frac{1}{\text{sec}}$$

$$\frac{1}{LC} = \frac{1}{(16 \times 10^{-3} H)(25 \times 10^{-9} F)} = 25 \times 10^8 \frac{1}{\text{sec}^2}$$

Thus the numerical admittance is

$$Y = \frac{(25 \times 10^{-9}) (s^2 + 80,000s + 25 \times 10^8)}{s}$$


Now find the zeros and poles of the admittance Y.

$$Y = \frac{(25 \times 10^{-9})(s^2 + 80,000s + 25 \times 10^8)}{s}$$
$$= \frac{(25 \times 10^{-9})(s + 40,000 + j30,000)(s + 40,000 - j30,000)}{s}$$

There is a single pole at $s = 0$.

There is a complex zero.


$$s = -40,000 \pm j30,000$$

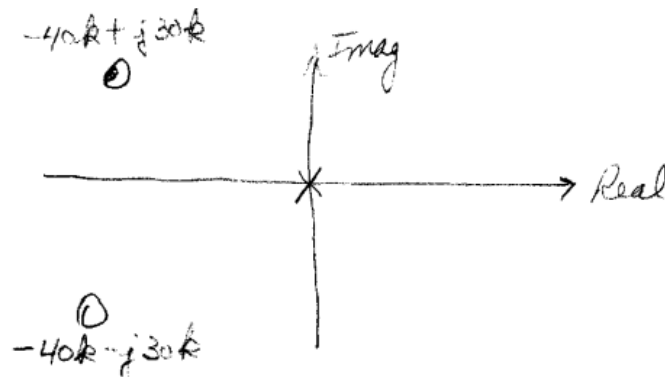

Ex-5: In the circuit above, the capacitor C_1 is charged to an initial voltage V_0 prior to closing the switch at $t = 0$.

The capacitor C_2 is discharged so that $V_{C2} = 0$ prior to closing the switch at $t = 0$.

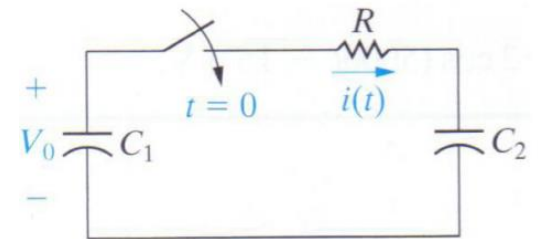Analyze the circuit and find the current $i(t)$ expression.




The s-domain equivalent circuit for $t > 0$

Apply KVL:

$$-\frac{V_0}{s} + V_{C1} + IR + V_{C2} = 0 \quad \text{Where } V_{C1} = I \frac{1}{sC_1} \quad V_{C2} = I \frac{1}{sC_2}$$
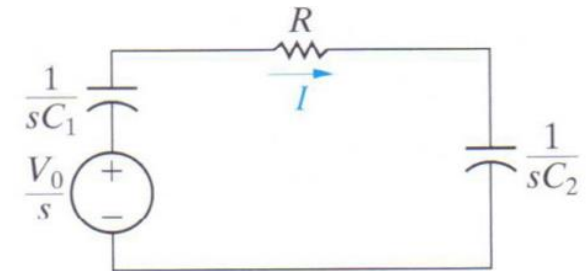
$$\frac{V_0}{s} = I \left(\frac{1}{sC_1} + R + \frac{1}{sC_2} \right) = I \left(R + \frac{1}{sC_1} + \frac{1}{sC_2} \right) = I \left[R + \frac{1}{s} \left(\frac{1}{C_1} + \frac{1}{C_2} \right) \right]$$



The equivalent capacitance for this series connection is

$$\frac{1}{C_{Equivalent}} = \frac{1}{C_1} + \frac{1}{C_2}$$

$$\frac{1}{sC_1} + \frac{1}{sC_2} = \frac{1}{s} \left(\frac{1}{C_1} + \frac{1}{C_2} \right) = \frac{1}{s} \left(\frac{1}{C_{Equiv}} \right)$$

Thus

$$I \left(R + \frac{1}{sC_{Equiv}} \right) = \frac{V_0}{s}$$

$$I \left(\frac{RsC_{Equiv} + 1}{sC_{Equiv}} \right) = \frac{V_0}{s} \Rightarrow I = \frac{V_0}{s} \left(\frac{sC_{Equiv}}{RsC_{Equiv} + 1} \right) \Rightarrow I = \frac{V_0}{s} \left(\frac{sC_{Equiv}}{RC_{Equiv} \left[s + \frac{1}{RC_{Equiv}} \right]} \right)$$

$$I = \frac{V_0}{R} \left(\frac{1}{s + \frac{1}{RC_{Equiv}}} \right)$$


Thus the inverse Laplace transform is

$$i(t) = \frac{V_0}{R} e^{-\frac{t}{RC_{Equiv}}} u(t)$$

Example - 6

$$H(s) = \frac{100(s+1)}{(s+10)(s+100)} = \frac{0.1(1+\frac{s}{1})}{(1+\frac{s}{10})(1+\frac{s}{100})}$$


MAGNITUDE

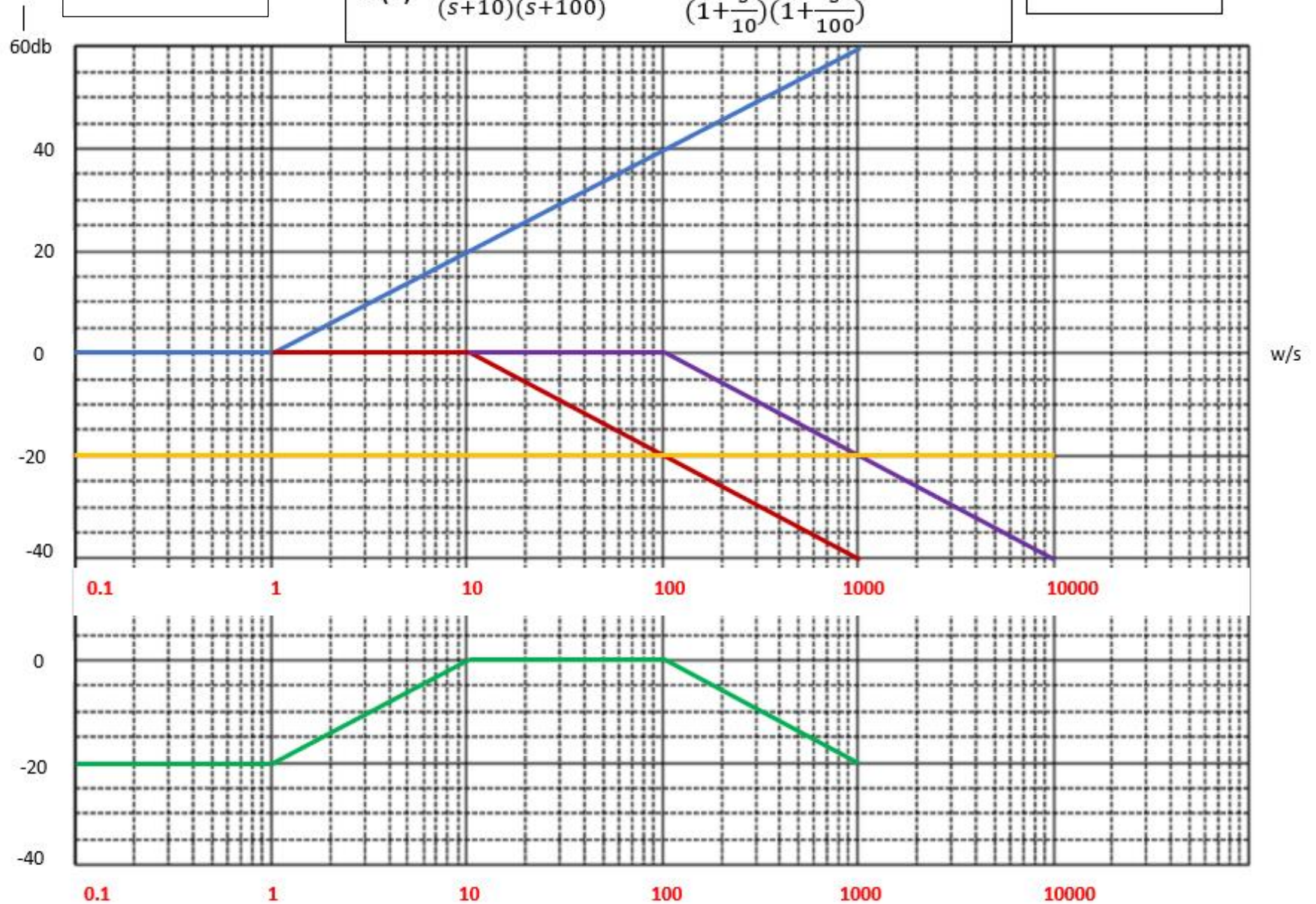

Example - 6

$$H(s) = \frac{100(s+1)}{(s+10)(s+100)} = \frac{0.1(1+\frac{s}{1})}{(1+\frac{s}{10})(1+\frac{s}{100})}$$


Phase

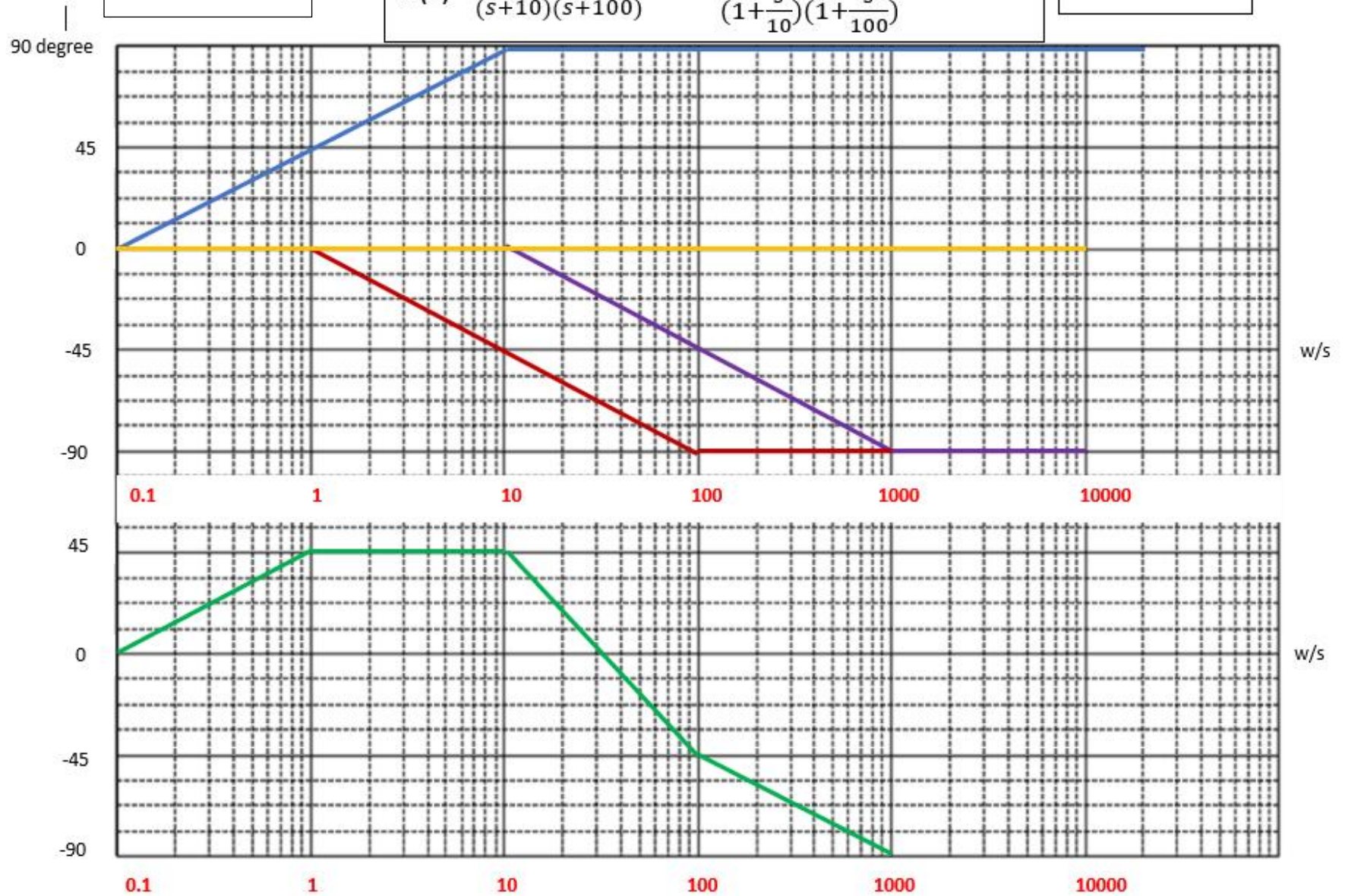

Example - 7

$$H(s) = \frac{50(s+200)(s+2000)}{(s+20)(s+20000)} = \frac{50(1+\frac{s}{200})(1+\frac{s}{2000})}{(1+\frac{s}{20})(1+\frac{s}{20000})}$$


MAGNITUDE

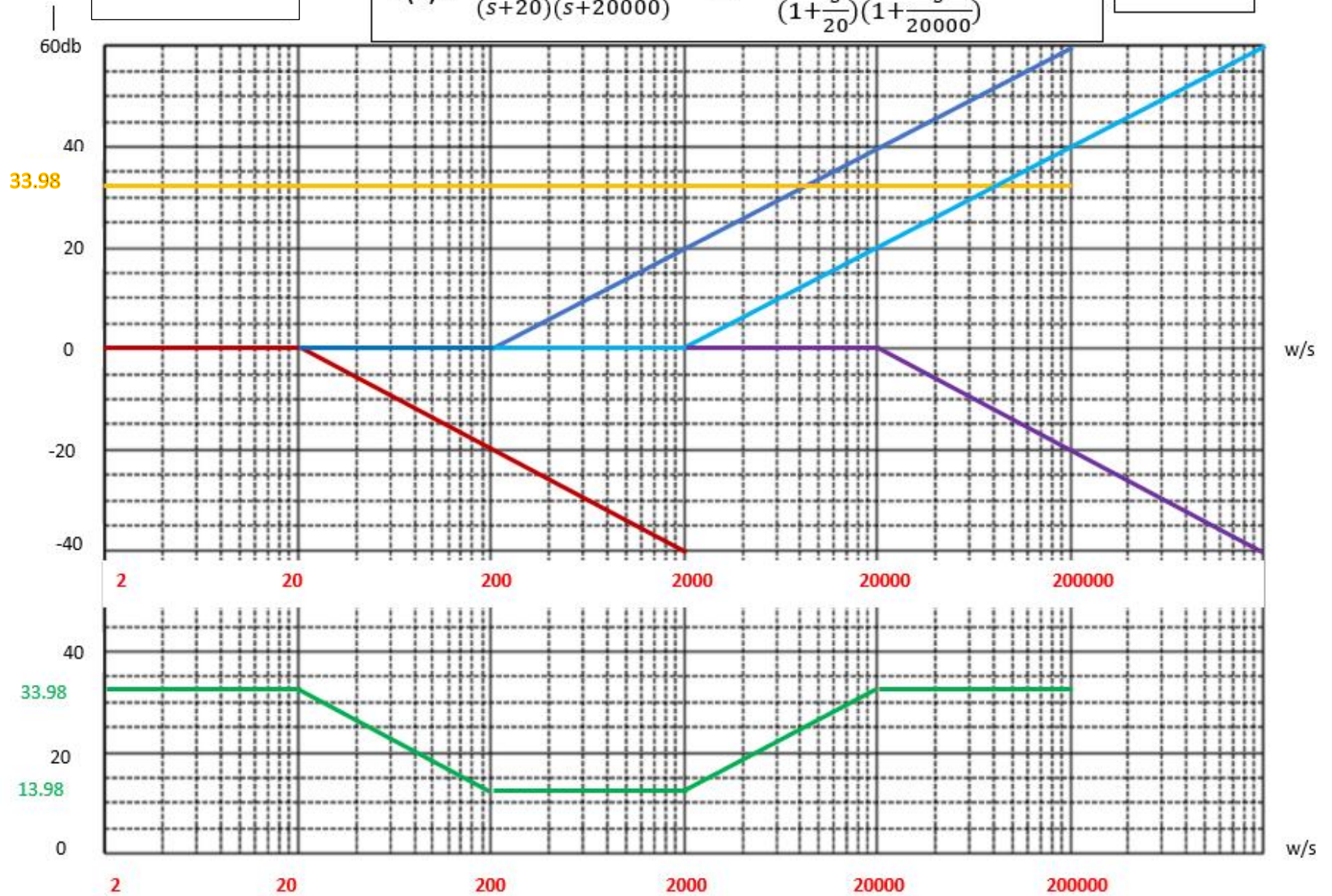

Example - 7

$$H(s) = \frac{50(s+200)(s+2000)}{(s+20)(s+20000)} = \frac{50(1+\frac{s}{200})(1+\frac{s}{2000})}{(1+\frac{s}{20})(1+\frac{s}{20000})}$$


PHASE

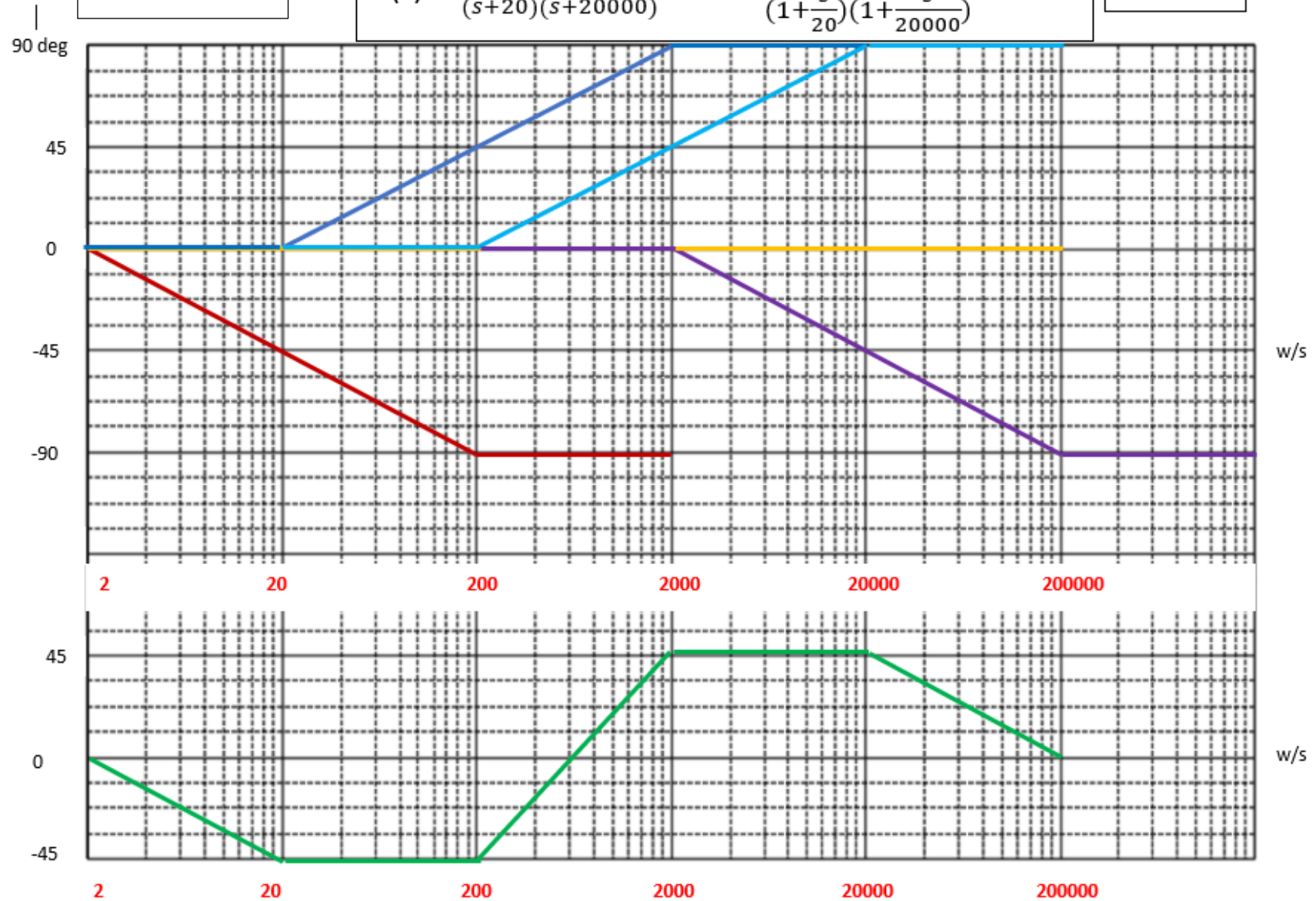

Example - 8

$$H(s) = \frac{100s}{(s+10)(s+100)} = \frac{0.1s}{(1+\frac{s}{10})(1+\frac{s}{100})}$$


MAGNITUDE

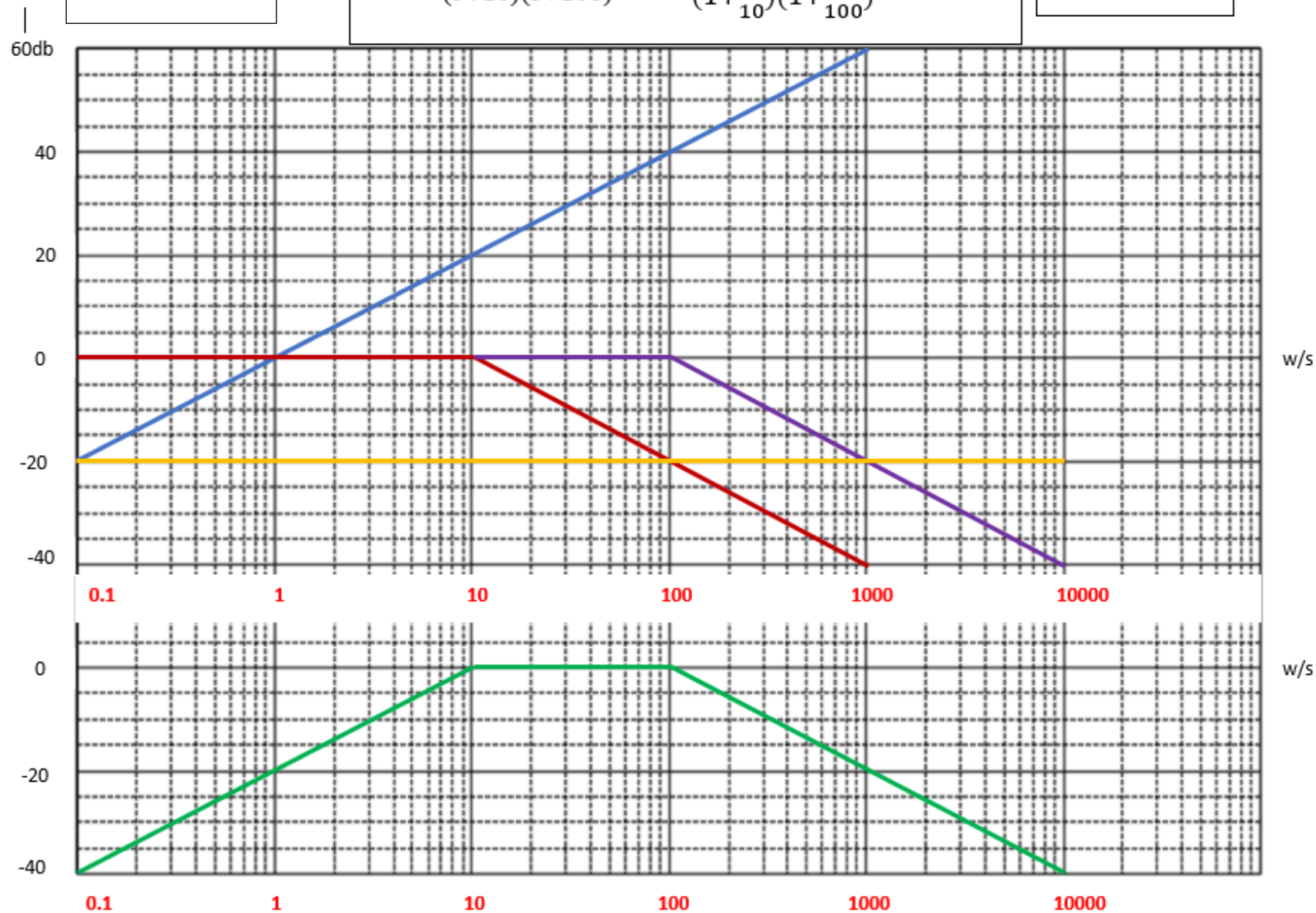

Example - 8

$$H(s) = \frac{100s}{(s+10)(s+100)} = \frac{0.1 s}{(1+\frac{s}{10})(1+\frac{s}{100})}$$


Phase

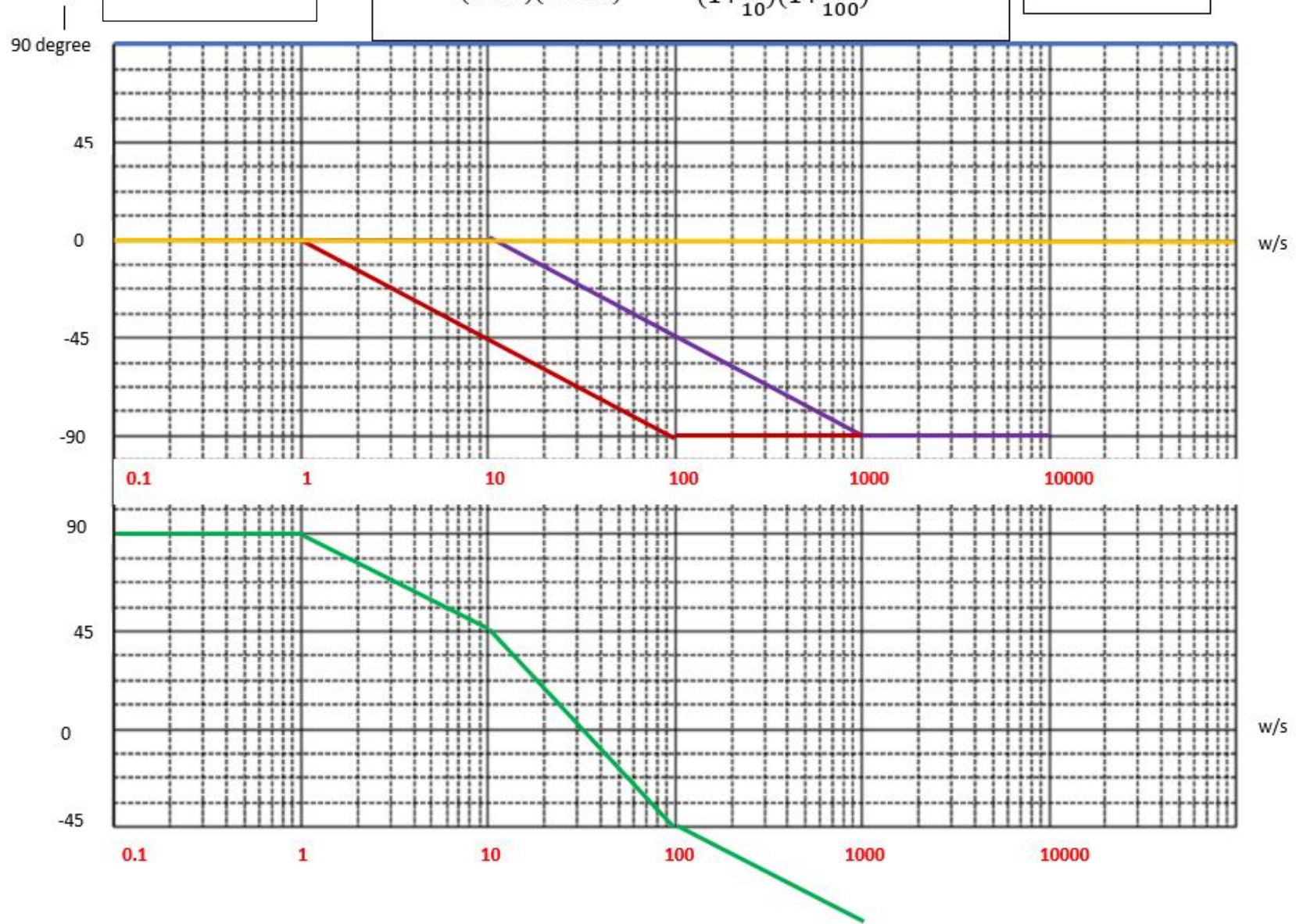

Example - 9

$$H(s) = \frac{10000(s+1)}{(s+10)(s+100)^2} = \frac{0.1(1+\frac{s}{1})}{(1+\frac{s}{10})(1+\frac{s}{100})^2}$$

MAGNITUDE


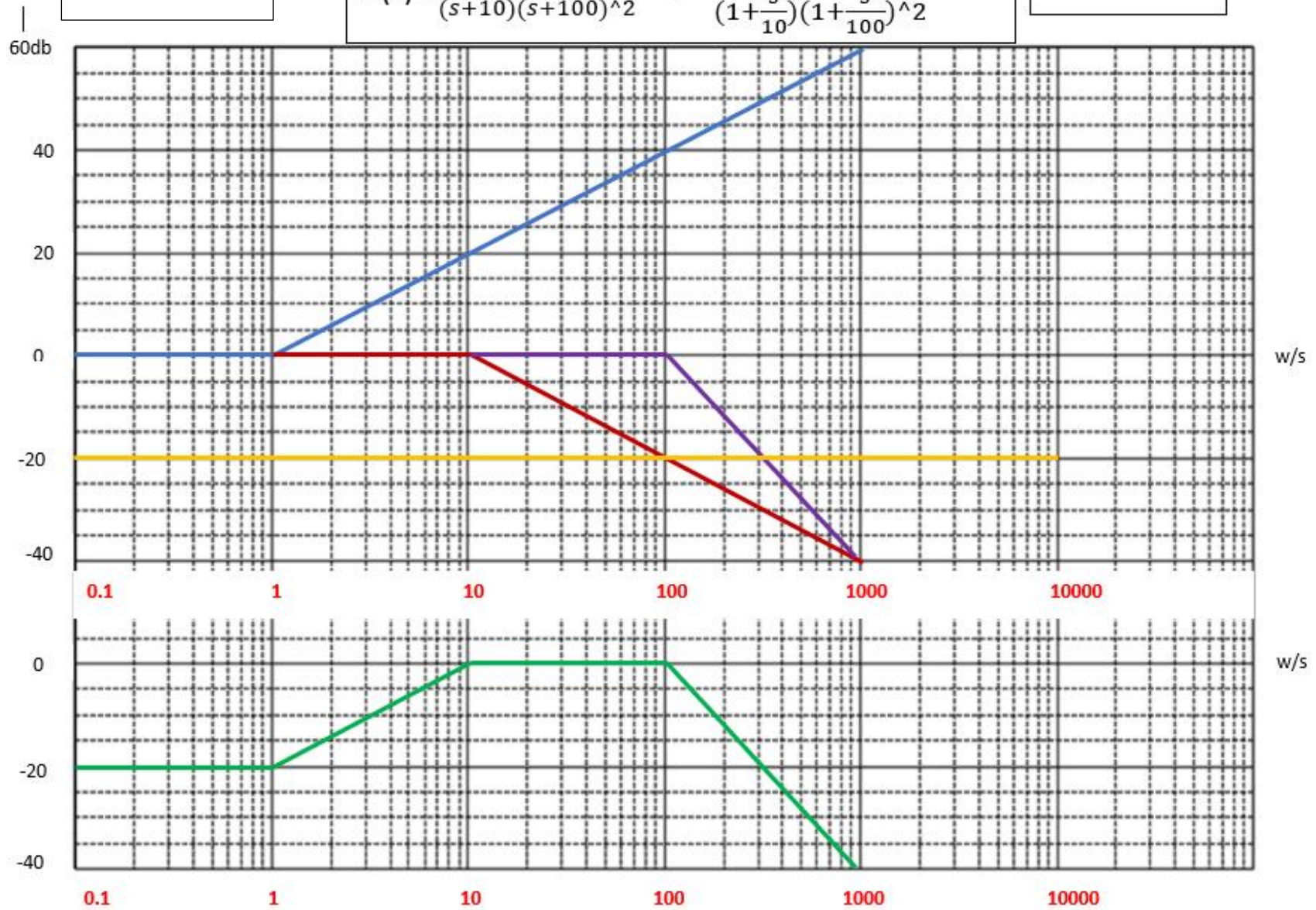


Example - 9

$$H(s) = \frac{10000(s+1)}{(s+10)(s+100)^2} = \frac{0.1(1+\frac{s}{1})}{(1+\frac{s}{10})(1+\frac{s}{100})^2}$$

Phase


90 degree

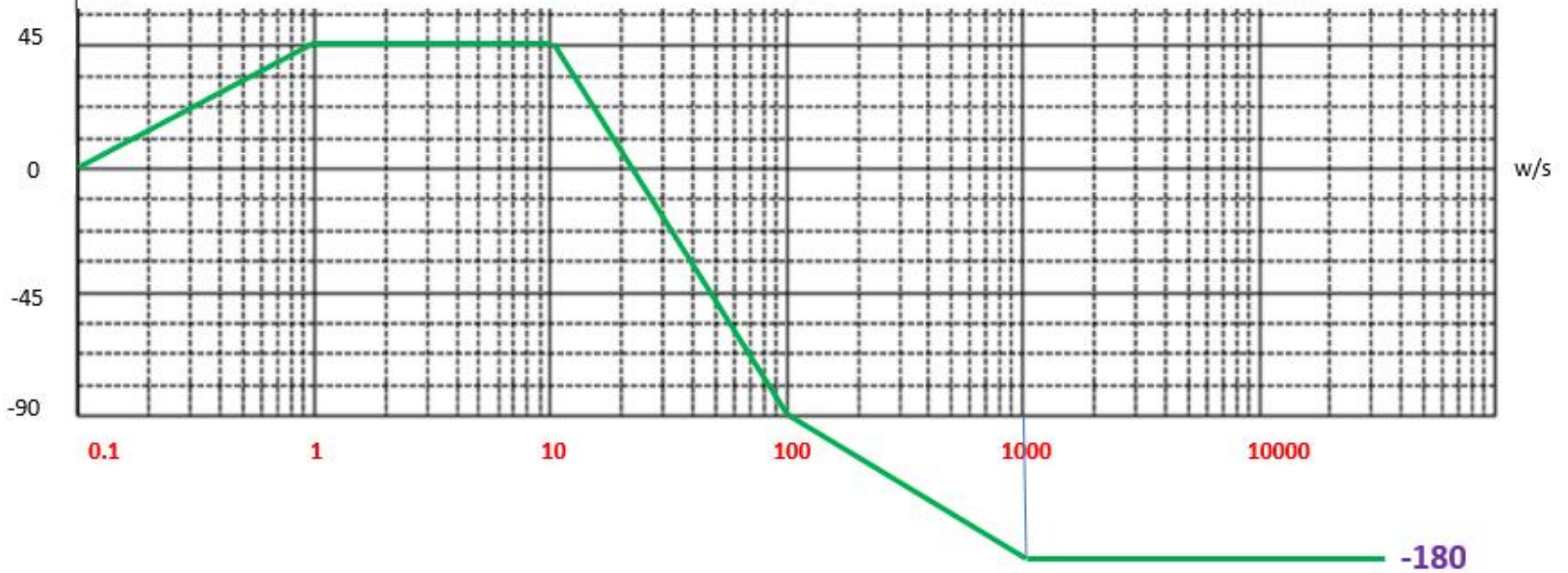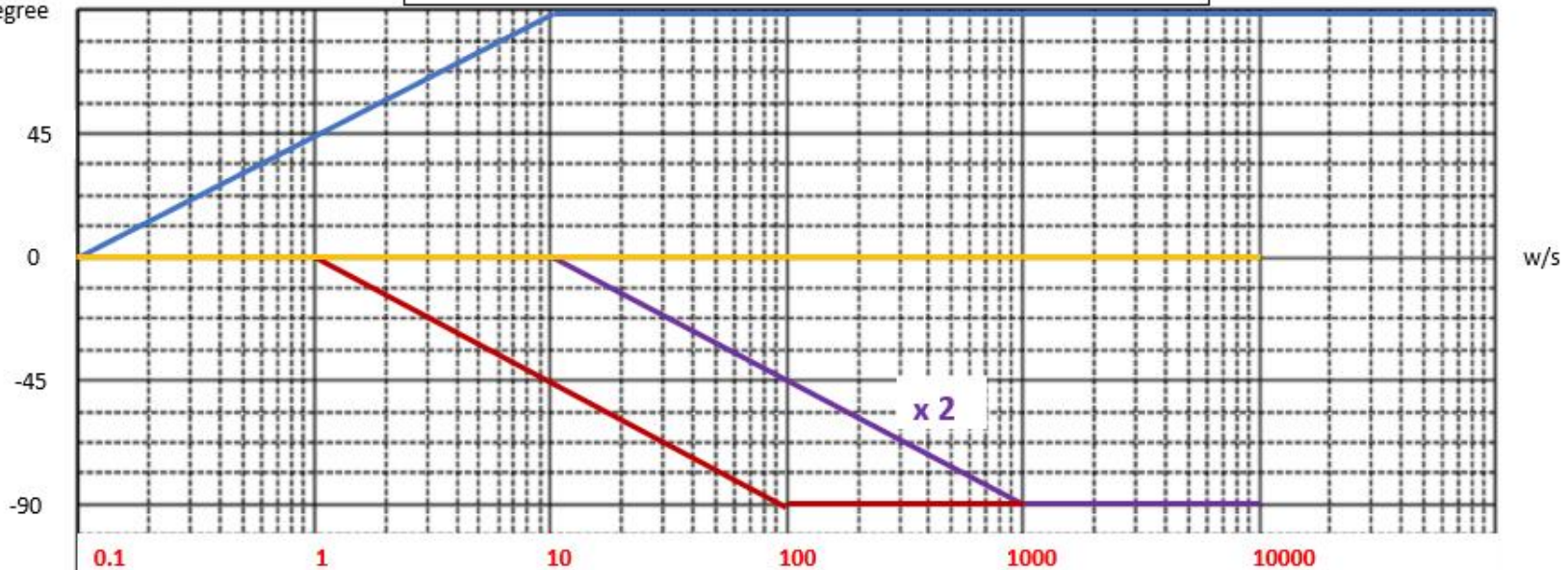

Example - 10

$$H(s) = \frac{4(s+25)}{(s^2+4s+100)} = \frac{(1+\frac{s}{25})}{1+(\frac{s}{10})^2+0.4(\frac{s}{10})}$$

MAGNITUDE

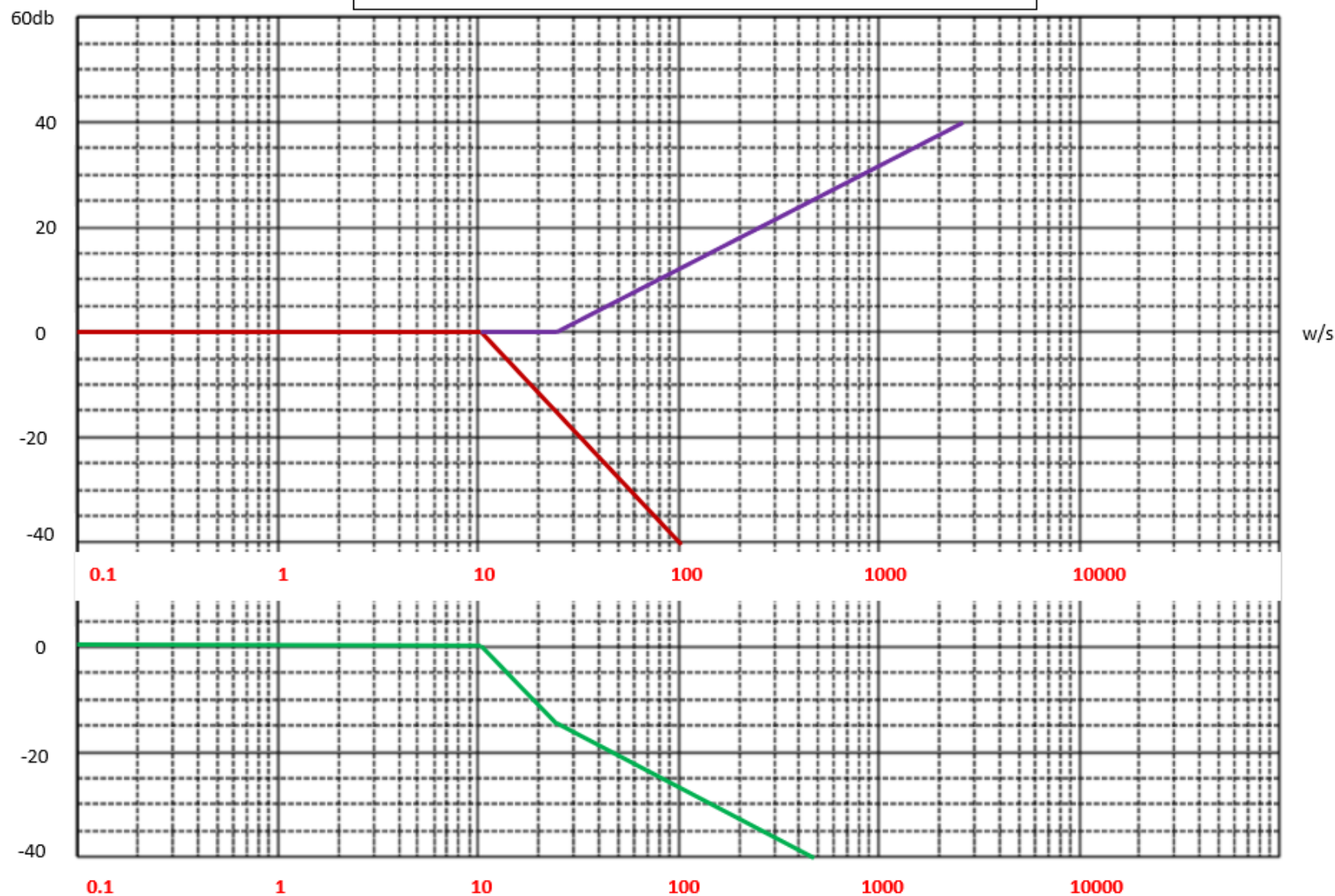

Example - 10

$$H(s) = \frac{4(s+25)}{(s^2+4s+100)} = \frac{(1+\frac{s}{25})}{1+(\frac{s}{10})^2 + 0.4(\frac{s}{10})}$$

Phase

