


## Homework-02      ENGR 117      Due date 02/21/2022

5 Questions    20 points each

- Q-1** Find the average power delivered by the ideal current source in the circuit

$$i_g = 8 \cos 5000t \text{ A}$$


Here 8 is max value

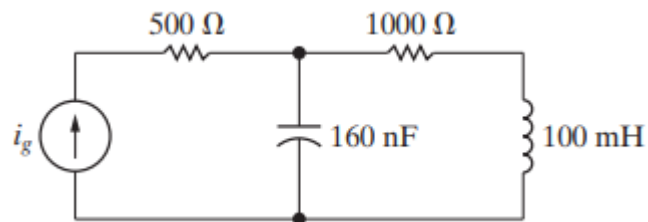

- Q-2** Find the average power dissipated in the  $60 \Omega$  resistor in the circuit

$$i_g = 6 \cos 20,000t \text{ A.}$$


Here 6 is max value

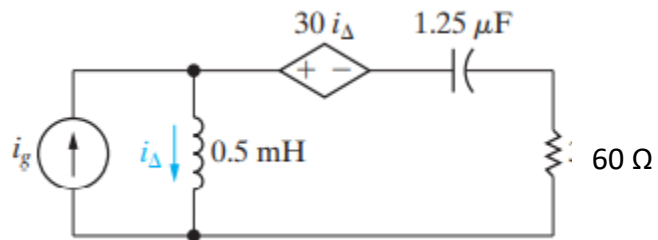

- Q-3** Find the average power, the reactive power, and the apparent power supplied by the voltage source in the circuit

$$v_g = 40 \cos 10^6 t \text{ V.}$$

Here 40 is max value

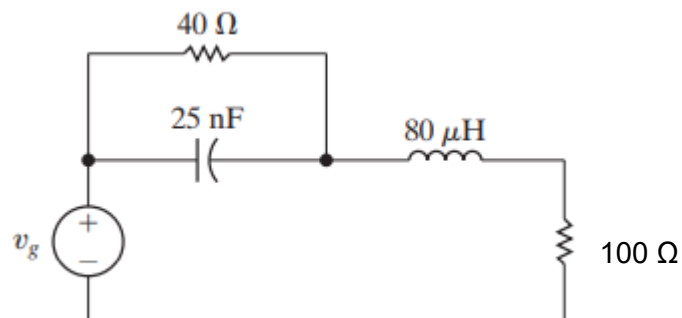

**Q- 4** A single-phase source is applied to a two-terminal, passive circuit with equivalent impedance  $Z = 2.0 \angle -45^\circ \Omega$  measured from the terminals. The source current is  $i(t) = 4\sqrt{2} \cos(\omega t)$  kA. Determine the (a) instantaneous power, (b) real power, and (c) reactive power delivered by the source. (d) Also determine the source power factor.

Here current is max value representation.

**Q-5** The real power delivered by a source to two impedances,  $Z_1 = 3 + j4 \Omega$  and  $Z_2 = 10 \Omega$ , connected in parallel, is 1100 W. Determine (a) the real power absorbed by each of the impedances and (b) the source current.

Here V is RMS value representation