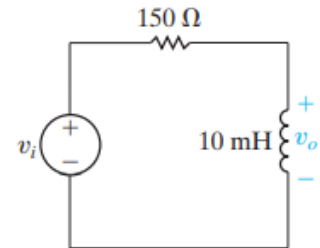


Homework-05 ENGR 117 Due date 04/25/2022

5 Questions 20 points each


Q-1 Consider the circuit shown below.

- a) This circuit behaves like what type of filter?
- b) What is the transfer function, of this filter?
- c) What is the cutoff frequency of this filter?
- d) Find the magnitude and phase of the transfer function at $s=j\omega_c$?




Q-2 For the bandpass filter shown. Find:

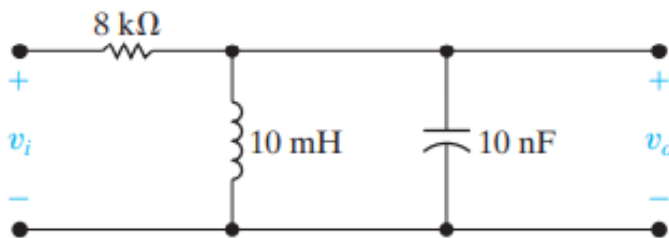(a) ω_o , (b) f_o , (c) Q , (d) ω_{c1} , (e) f_{c1} , (f) ω_{c2} , (g) f_{c2} , and (h) β .



Q-3 Verify the following for the bandpass filter: (show your work)
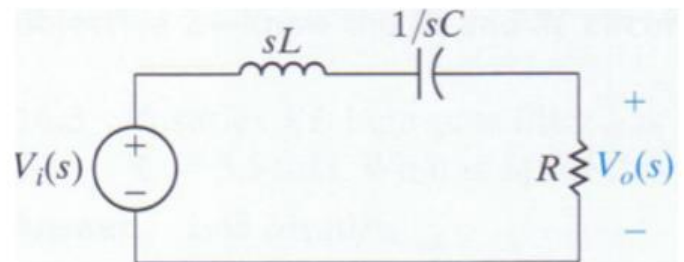
$$\omega_{c1} = \frac{-R}{2L} + \sqrt{\left(\frac{R}{2L}\right)^2 + \frac{1}{LC}}$$
$$\omega_{c2} = \frac{+R}{2L} + \sqrt{\left(\frac{R}{2L}\right)^2 + \frac{1}{LC}}$$



Q-4 Use a 5 nF capacitor to design a series RLC bandpass filter. The center frequency of the filter is 8 kHz, and the quality factor is 2. (Show your circuit)


- a) Specify the values of R and L.
- b) What is the lower cutoff frequency in kilohertz?
- c) What is the upper cutoff frequency in kilohertz?
- d) What is the bandwidth of the filter in kilohertz?

Q-5 Design the component values for the series RLC band reject filter so that the center frequency is 4 kHz and the quality factor is 5. Use a 500 nF capacitor. (Show your circuit)

- a) Specify the values of R and L.
- b) Find quality factor Q.

Q-1 (a) High Pass Filter

(b)

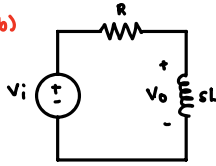

$$V_o(s) = \frac{sL}{R+sL} V_i(s)$$

$$H(s) = \frac{s}{s + R/L} = \frac{s}{s + 150/10 \times 10^{-3}} = \frac{s}{s + 15000}$$

$$H(j\omega) = \frac{j\omega}{j\omega + 15000}$$

$$(c) \quad \omega_c = R/L = 150/10 \times 10^{-3} = 15000 \text{ rad/s}$$

$$\theta = 45^\circ$$

$$(d) \quad H(j\omega_c) = \frac{\omega_c \angle 90^\circ}{\sqrt{\omega_c^2 + (15000)^2} \angle \tan^{-1}(\frac{\omega_c}{15000})}$$

$$= \frac{15000 \angle 90^\circ}{\sqrt{(15000)^2 + (15000)^2} \angle \tan^{-1}(\frac{15000}{15000})}$$

$$= 0.7071 \angle 90^\circ - 45^\circ$$

$$\text{Magnitude: } |H(j\omega)| = 0.7071$$

$$\text{Phase: } \theta(j\omega) = 45^\circ$$

$$Q-2 (a) \quad \omega_0 = \sqrt{\frac{1}{LC}} = \sqrt{\frac{1}{(10 \times 10^{-3})(10 \times 10^{-9})}} = 100000 \text{ rad/s}$$

$$(b) \quad \omega_0 = 2\pi f_0$$

$$f_0 = \frac{100000}{2\pi} = 15915.49 \text{ Hz}$$

$$(c) \quad Q = \sqrt{\frac{R^2 C}{L}} = \sqrt{\frac{(8k)^2 (10 \times 10^{-9})}{10 \times 10^{-3}}} = 8$$

$$(d) \quad \omega_{c1} = \frac{-1}{2RC} + \sqrt{\left(\frac{1}{2RC}\right)^2 + \frac{1}{LC}} = \frac{-1}{2(8k)(10 \times 10^{-9})} + \sqrt{\left[\frac{1}{2(8k)(10 \times 10^{-9})}\right]^2 + \frac{1}{(10 \times 10^{-3})(10 \times 10^{-9})}}$$

$$= 93945.12 \text{ rad/s}$$

$$(e) \quad f_{c1} = \frac{93945.12}{2\pi} = 14951.83 \text{ Hz}$$

$$(f) \quad \omega_{c2} = \frac{+1}{2RC} + \sqrt{\left(\frac{1}{2RC}\right)^2 + \frac{1}{LC}} = \frac{+1}{2(8k)(10 \times 10^{-9})} + \sqrt{\left[\frac{1}{2(8k)(10 \times 10^{-9})}\right]^2 + \frac{1}{(10 \times 10^{-3})(10 \times 10^{-9})}}$$

$$= 106445.12 \text{ rad/s}$$

$$(g) \quad f_{c2} = \frac{106445.12}{2\pi} = 16941.27 \text{ Hz}$$

$$(h) \quad \beta = \frac{1}{RC} = \frac{1}{(8k)(10 \times 10^{-9})} = 12500 \text{ Hz}$$

Q-3 - $V_i(s) + I(s) \cdot sL + I(s) \cdot \frac{1}{sC} + I(s) \cdot R = 0$

$$V_i(s) = I(s) \left[sL + \frac{1}{sC} + R \right]$$

$$= \frac{V_o}{R} \left[\frac{s^2 LC + 1 + sCR}{sC} \right]$$

$$\frac{V_i(s)}{V_o(s)} = \frac{1}{H(s)} = \frac{s^2 LC + 1 + sCR}{sCR}$$

$$H(s) = \frac{sCR}{s^2 LC + 1 + sCR} = \frac{s(R/L)}{s^2 + s(R/L) + (1/LC)}$$

$$H(j\omega) = \frac{R/L(j\omega)}{(j\omega)^2 LC + (j\omega)CR + 1}$$

$$|H(j\omega)| = \frac{\omega(R/L)}{\sqrt{(\frac{1}{LC} - \omega^2)^2 + [\omega(R/L)]^2}}$$

$$I(s) \cdot R = V_o$$

$$I(s) = V_o/R$$

$$H_{max} = |H(j\omega_0)| = \frac{\omega_0(R/L)}{\sqrt{(\frac{1}{LC} - \omega_0^2)^2 + [\omega_0(R/L)]^2}}$$

$$(1/\sqrt{2}) H_{max}$$

$$\frac{1}{\sqrt{2}} = \frac{\omega_c(R/L)}{\sqrt{(\frac{1}{LC} - \omega_c^2)^2 + [\omega_c(R/L)]^2}}$$

$$= \frac{1}{\sqrt{(\frac{\omega_c L}{R} - \frac{1}{\omega_c RC})^2 + 1}}$$


$$\pm 1 = \frac{\omega_c L}{R} - \frac{1}{\omega_c RC}$$

$$\omega_c^2 L \pm \omega_c R - 1/C = 0$$

$$\omega_{c1} = -\frac{R}{2L} + \sqrt{\left(\frac{R}{2L}\right)^2 + \frac{1}{LC}}$$

$$\omega_{c2} = \frac{R}{2L} + \sqrt{\left(\frac{R}{2L}\right)^2 + \frac{1}{LC}}$$

Q-4

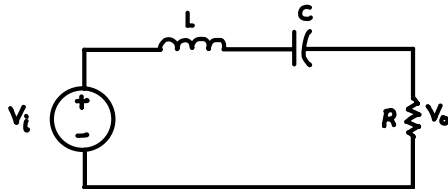

$$C = 5 \text{ nF}$$

$$Q = 2$$

$$f_0 = 8 \text{ kHz} \rightarrow \omega_0 = 16 \text{ k}\pi$$

(a) $\omega_0 = \sqrt{\frac{1}{LC}} \rightarrow L = \frac{1}{\omega_0^2 C} = \frac{1}{(16 \text{ k}\pi)^2 (5 \times 10^{-9})} = 0.07916 \text{ H}$

$Q = \sqrt{\frac{L}{CR^2}} \rightarrow R = \sqrt{\frac{L}{CQ^2}} = \sqrt{\frac{0.07916}{(5 \times 10^{-9})(2)^2}} = 1989.47 \Omega$

(b) $\omega_{c1} = -\frac{R}{2L} + \sqrt{\left(\frac{R}{2L}\right)^2 + \left(\frac{1}{LC}\right)}$

$$= \frac{-1989.47}{2(0.07916)} + \sqrt{\left[\frac{1989.47}{2(0.07916)}\right]^2 + \left[\frac{1}{(0.07916)(5 \times 10^{-9})}\right]}$$

$$= 39245.41 \text{ rad/s}$$

$$f_{c1} = \frac{39245.41}{2\pi} = 6246.10 \text{ Hz}$$

(c) $\omega_{c2} = \frac{R}{2L} + \sqrt{\left(\frac{R}{2L}\right)^2 + \left(\frac{1}{LC}\right)}$

$$= \frac{1989.47}{2(0.07916)} + \sqrt{\left[\frac{1989.47}{2(0.07916)}\right]^2 + \left[\frac{1}{(0.07916)(5 \times 10^{-9})}\right]}$$


$$= 64377.68 \text{ rad/s}$$

$$f_{c2} = \frac{64377.68}{2\pi} = 10246.03 \text{ Hz}$$

(d) $\beta = \omega_{c2} - \omega_{c1} = 10246.03 \text{ Hz} - 6246.10 \text{ Hz}$

$$= 3999.93 \text{ Hz} \approx 4 \text{ kHz}$$

Q-5

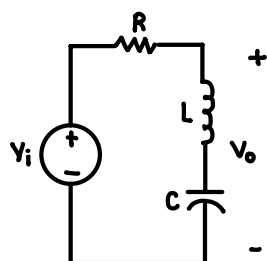

$$C = 500 \text{ nF}$$

$$f_o = 4 \text{ kHz} \longrightarrow \omega_o = 8000\pi \text{ rad/s}$$

$$Q = 5$$

$$(a) \quad \omega_o = \sqrt{\frac{1}{LC}} \longrightarrow L = \frac{1}{\omega_o^2 C} = \frac{1}{(8000\pi)^2 (500 \times 10^{-9})} = 3.166 \text{ mH}$$

$$Q = \sqrt{\frac{L}{CR^2}} \longrightarrow R = \sqrt{\frac{L}{CQ^2}} = \sqrt{\frac{3.166 \times 10^{-3}}{(500 \times 10^{-9})(5)^2}} = 15.915 \text{ } \Omega$$

$$(b) \quad Q = 5$$

$$\text{KVL: } -V_{in} + iR + iZ_c = 0$$

$$V_{in} = i(R + Z_c)$$


$$V_{in} = \frac{V_{out}}{Z_c} (R + Z_c)$$

$$\frac{V_{out}}{V_{in}} = \frac{Z_c}{R + Z_c} = \frac{1/sC}{R + 1/sC}$$

$$H(s) = \frac{1}{1 + sRC}$$

$$V_{out} = iZ_c \rightarrow i = \frac{V_{out}}{Z_c}$$

$$Z_c = 1/sC$$

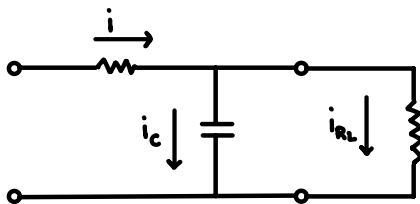

$$\text{KVL: } -V_{in} + iR + V_{out} = 0$$

$$V_{in} = (V_{out} sC + \frac{V_{out}}{R_L}) R + V_{out}$$

$$V_{in} = V_{out} (sCR + \frac{R}{R_L} + 1)$$

$$\frac{V_{out}}{V_{in}} = \frac{R_L}{sCRR_L + R + R_L}$$

$$H(s) = \frac{R_L}{sCRR_L + R + R_L}$$

$$i = i_c + i_{R_L}$$

$$i_c = \frac{V_{out}}{1/sC} = V_{out} sC \quad i_{R_L} = \frac{V_{out}}{R_L}$$