

# CALIFORNIA STATE UNIVERSITY SACRAMENTO



DEPARTMENT OF ELECTRICAL AND ELECTRONIC ENGINEERING

## **EEE 117 Network Analysis**

**Text:** Electric Circuits by J. Nilsson and S. Riedel Prentice Hall

**Lecture Set 4: Laplace Transform in Circuit Analysis**

**Instructor: Riaz Ahmad**

## **Laplace Transform in Circuit Analysis**

- Preview
- Circuit Elements in the “s” Domain
- Circuit Analysis in the “s” Domain
- The Transfer Function
- The Transfer Function in Partial Fraction Expansions
- The Transfer Function and the Steady-State Sinusoidal Response
- The Impulse Function in Circuit Analysis
- Bode Diagram
- What is Decibel (dB)
- Magnitude in terms of Linear versus dB
- Bode Plot for Real, First-Order Poles and Zeros
- Bode Plot for Complex Poles and Zeros

## Preview

$$\mathcal{L}\{f(t)\} = \int_0^{\infty} f(t) e^{-st} dt$$

- The Laplace transform has two unique characteristics:
- First, it transforms a set of linear constant-coefficient differential equations into a set of linear polynomial equations, which are easier to manipulate.
- Second, it automatically introduces into the polynomial equations the initial values of the current and voltage variables. Thus, initial conditions are an inherent part of the transform process.

Time Domain

Freq Domain

Volts  $\longleftrightarrow$  Volts sec

Amps  $\longleftrightarrow$  Amps sec

$\Omega = \frac{V}{A} \longleftrightarrow \frac{V \text{ sec}}{A \text{ sec}} = \frac{V}{A} = \Omega$

## Circuit Elements in the “s” Domain

- The procedure for developing an s-domain equivalent for each circuit element is simple and straightforward.
- Find Laplace transform of each element.

**Resistor:** A resistive circuit in time domain can be represented:

$$v = Ri$$


Take the Laplace of both sides

$$V(s) = R I(s)$$


$$\text{Where } V = \mathcal{L}\{v\}$$

$$\text{And } I = \mathcal{L}\{i\}$$

Time Domain

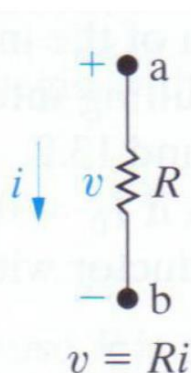

Freq Domain

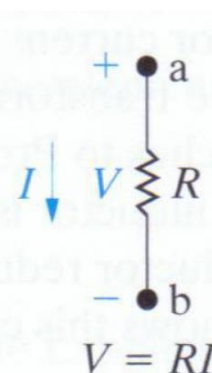


**Inductor:** An Inductive circuit can be represented as:


$$v = L \frac{di}{dt}$$

Take the Laplace of both sides
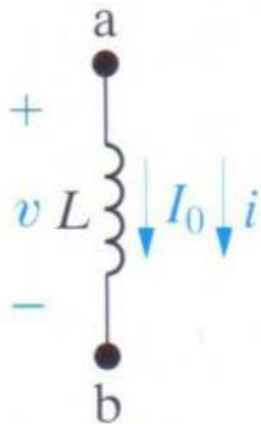
$$\begin{aligned} V &= L[sI - i(0^-)] = sLI - L\underbrace{i(0^-)}_{I_0} \\ &= sLI - LI_0 \end{aligned}$$




$$V = sLI - LI_0$$

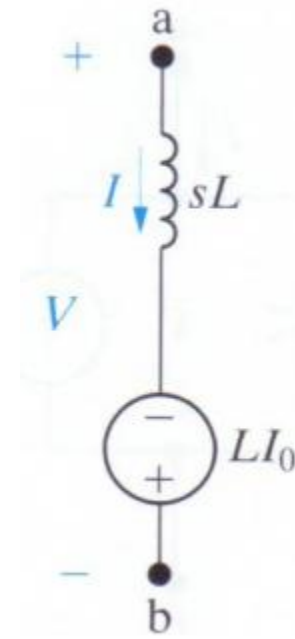


- The same inductor element can be modeled by a parallel connection by solving the previous equation for  $I$ . (or by source transformation)

$$V = sLI - LI_0 \Rightarrow I = \frac{V + LI_0}{sL} = \frac{V}{sL} + \frac{I_0}{s}$$

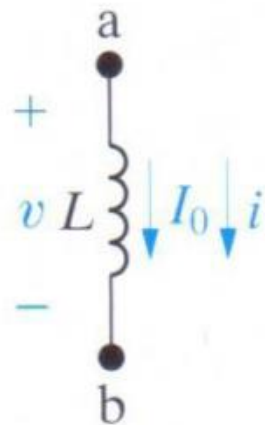- Thus, the inductor can also be shown as:



$$I = \frac{V}{sL} + \frac{I_0}{s}$$

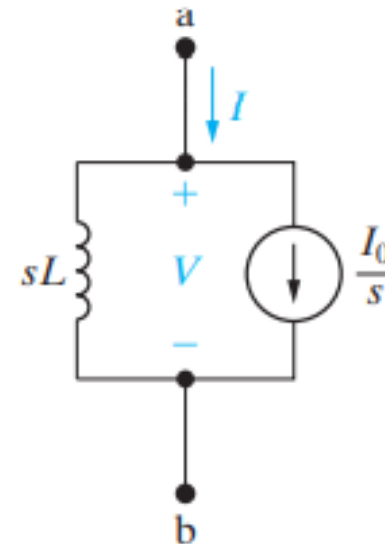

- Note that the passive sign convention determines the direction of current flow.


**Capacitor:** A Capacitive circuit can be represented as:

$$i = C \frac{dv}{dt}$$


Take the Laplace of both sides

$$I = C \left[ sV - v(0^-) \right] = \frac{V}{\frac{1}{sC}} - CV_0$$

Note that  $Z_C = \frac{1}{sC}$

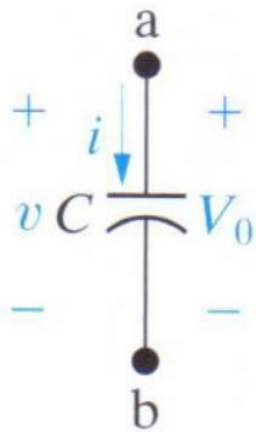


$$I = \frac{V}{\frac{1}{sC}} - CV_0$$

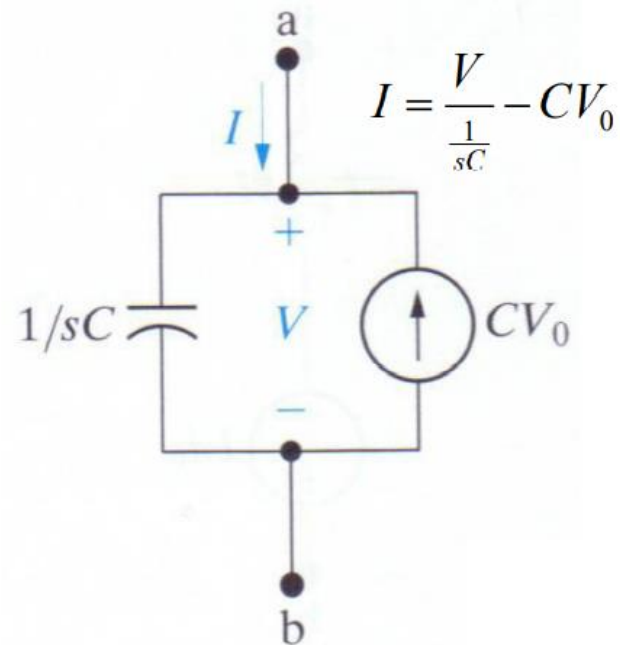


- The same capacitor element can be modeled by a series connection by solving the previous equation for  $V$ . (or by source transformation)
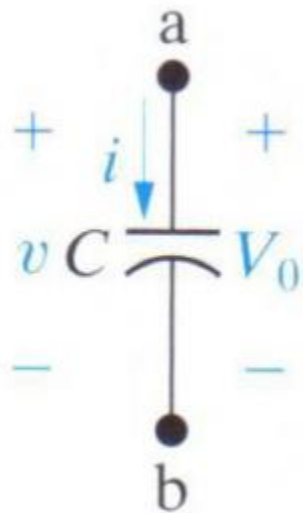
$$I = sCV - CV_0 \Rightarrow V = \frac{I + CV_0}{sC} = I \frac{1}{sC} + \frac{V_0}{s}$$









$$V = I \frac{1}{sC} + \frac{V_0}{s}$$

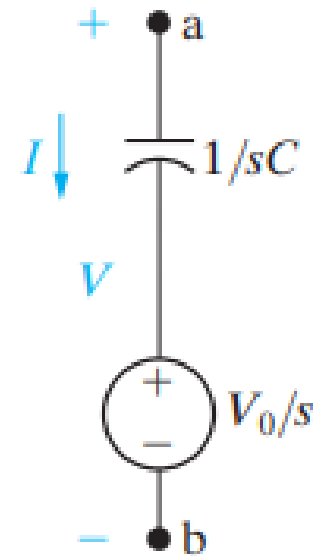

- Note that the passive sign convention again determines the direction of current flow.



**TABLE 13.1 Summary of the s-Domain Equivalent Circuits**

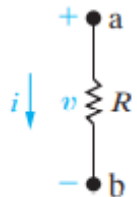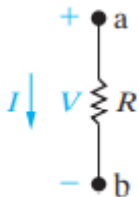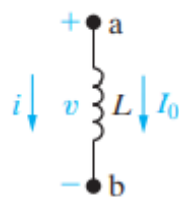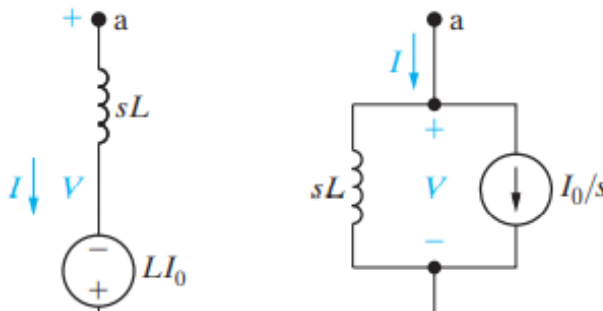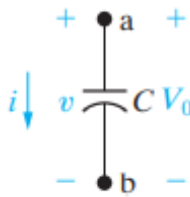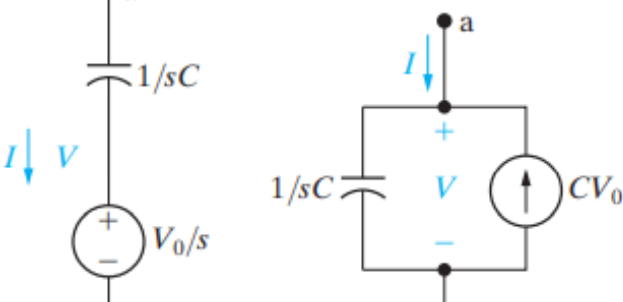TIME DOMAIN	FREQUENCY DOMAIN
 <p><math>v = Ri</math></p>	 <p><math>V = RI</math></p>
 <p><math>v = L di/dt,</math>  <math>i = \frac{1}{L} \int_0^t v dx + I_0</math></p>	 <p><math>V = sLI - LI_0</math>  <math>I = \frac{V}{sL} + \frac{I_0}{s}</math></p>
 <p><math>i = C dv/dt,</math>  <math>v = \frac{1}{C} \int_0^t i dx + V_0</math></p>	 <p><math>V = \frac{I}{sC} + \frac{V_0}{s}</math>  <math>I = sCV - CV_0</math></p>

## Circuit Analysis in the “s” Domain

- When no initial conditions are present, we can write the following equation in the “s” domain for any of the three circuit elements.

$$V = ZI$$

For the resistor  $Z = R$  Ohms.

For the inductor  $Z = sL$  Ohms.

For the capacitor  $Z = 1/(sC)$  Ohms.

## The Transfer Function

- The transfer function is defined as the s-domain ratio of the (Laplace transformed) output to the input with all initial conditions =0

$$H(s) = \frac{Y(s)}{X(s)}$$

- Y(s) is called the response of the system.
- X(s) is the input to the system.
- For linear lumped parameter circuits (which is most of your undergraduate study), H(s) is always a rational function of s.

$$H(s) = \frac{1000(s + 5000)}{s^2 + 6000s + 25 \times 10^6}$$

- The poles of are the roots of the denominator.
- The zeros of are the roots of the numerator.

$$\begin{aligned} p_1 &= -3000 - j4000, \\ p_2 &= -3000 + j4000. \end{aligned}$$

$$z_1 = -5000.$$


- Complex poles and zeros always appear in conjugate pairs.
- The poles (from the denominator) of  $H(s)$  must lie in the left-hand plane (LHP) for a bounded response.
- The zeros (from the numerator) of  $H(s)$  may lie anywhere.
- We can write the circuit output  $Y(s)$  as the product of the transfer function  $H(s)$  and the driving function  $X(s)$ .

$$Y(s) = H(s)X(s)$$

- For the inputs of common use in circuits, the input  $X(s)$  is also a rational function.
- Thus, by partial fraction expansion, we can form the poles of  $H(s)$  and  $X(s)$  into a summation of terms.
- The terms generated by poles of  $X(s)$  give rise to the steady state component of total response.
- The terms generated by poles of  $H(s)$  give rise to the transient components of total response.

**Ex-1:** The circuit shown below is driven by a voltage source whose voltage increases linearly with time, namely  $v_g = 50 t$

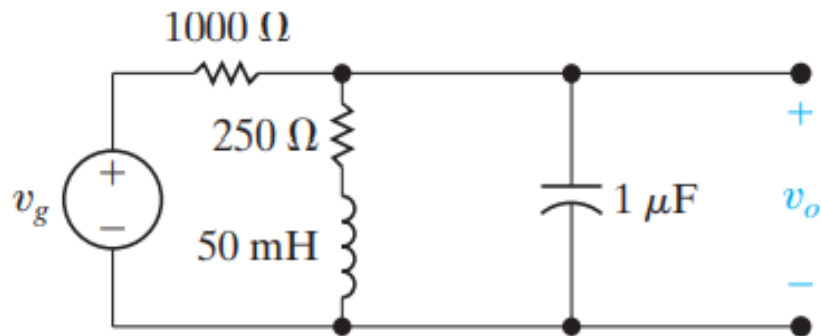- a) Use the transfer function to find  $v_o$ .
- b) Identify the transient component of the response.
- c) Identify the steady-state component of the response.
- d) Sketch  $v_o$  versus  $t$  for  $0 \leq t \leq 1.5$  ms.



## The Transfer Function and the Steady-State Sinusoidal Response

- Consider the following sinusoidal signal:

$$x(t) = A \cos(\omega t + \phi),$$

$$x(t) = A \cos \omega t \cos \phi - A \sin \omega t \sin \phi,$$

- Note,  $\cos \phi$  and  $\sin \phi$  are constant values.
- Take Laplace of both sides.

$$\begin{aligned} X(s) &= \frac{(A \cos \phi)s}{s^2 + \omega^2} - \frac{(A \sin \phi)\omega}{s^2 + \omega^2} = \frac{A(s \cos \phi - \omega \sin \phi)}{s^2 + \omega^2} \\ &= \frac{A(s \cos \phi - \omega \sin \phi)}{(s - j\omega)(s + j\omega)} \end{aligned}$$

- Note that the input transforms to the s-domain is complex conjugate.

- The output can be written as:

$$Y(s) = H(s)X(s) = H(s) \frac{A(s \cos \phi - \omega \sin \phi)}{(s - j\omega)(s + j\omega)}$$

$$Y(s) = \frac{K}{s - j\omega} + \frac{K^*}{s + j\omega} + \sum \text{terms generated by the poles of } H(s)$$

- Now poles of  $H(s)$  contributes only to the transient response and not to steady state response.
- Since we are interested in the steady-state solution at the moment, this allows us to simplify the derivation.
- Thus, the first two terms on the right-hand side of equation determine the steady-state response.

$$Y(s) = \frac{K}{s - j\omega} + \frac{K^*}{s + j\omega}$$

$$Y(s) = H(s) \cdot \frac{A(s \cos \phi - \omega \sin \phi)}{(s - j\omega)(s + j\omega)} = \frac{K}{(s - j\omega)} + \frac{K^*}{(s + j\omega)} \quad \text{--- (1)}$$

$$H(s) \cdot A(s \cos \phi - \omega \sin \phi) = K(s + j\omega) + K^*(s - j\omega)$$

For  $s = j\omega$

$$H(j\omega) \cdot A(j\omega \cos \phi - \omega \sin \phi) = K(j\omega + j\omega)$$

$$K = \frac{H(j\omega) \cdot A(j\omega \cos \phi - \omega \sin \phi)}{2j\omega}$$

$$K = \frac{H(j\omega) \cdot A(j\omega \cos \phi + j^2 \omega \sin \phi)}{2j\omega}$$

$$K = \frac{H(j\omega) \cdot A(\cos \phi + j \sin \phi)}{2}$$

$$K = H(j\omega) \cdot \frac{A e^{j\phi}}{2}$$

In general 'H' is a complex quantity. So

$$H(j\omega) = H \angle \theta = H e^{j\theta}$$

$$K = |H| e^{j\theta} \cdot \frac{A e^{j\phi}}{2} = |H| e^{j(\theta + \phi)} \cdot \frac{A}{2}$$

$$K = \frac{A}{2} \cdot |H| e^{j(\theta + \phi)}$$

$$K^* = \frac{A}{2} \cdot |H| \cdot e^{-j(\theta + \phi)}$$

Put it in eq (1)



$$Y(s) = \frac{\frac{A}{2} |H| e^{j(\theta+\phi)}}{s-j\omega} + \frac{\frac{A}{2} |H| e^{-j(\theta+\phi)}}{s+j\omega}$$

$$Y(s) = \frac{A}{2} |H| \left[ e^{j(\theta+\phi)} \cdot \frac{1}{(s-j\omega)} + e^{-j(\theta+\phi)} \cdot \frac{1}{(s+j\omega)} \right]$$

Take inverse laplace of both sides.

$$y(t) = \frac{A}{2} \cdot |H| \left[ e^{j(\theta+\phi)} \cdot e^{j\omega t} + e^{-j(\theta+\phi)} \cdot e^{-j\omega t} \right]$$

$$y(t) = \frac{A}{2} \cdot |H| \left[ e^{j(\omega t + \theta + \phi)} + e^{-j(\omega t + \theta + \phi)} \right]$$

$$y(t) = A \cdot |H| \cos(\omega t + \theta + \phi)$$

$$y_{ss}(t) = A \cdot |H| \cos(\omega t + \theta + \phi)$$

Here.

$|H|$  = Amplitude of transfer function


$\theta$  = Phase angle of transfer function

$\phi$  = Phase angle of input

$A$  = Amplitude of input

$\omega$  = Frequency of input in rad/sec

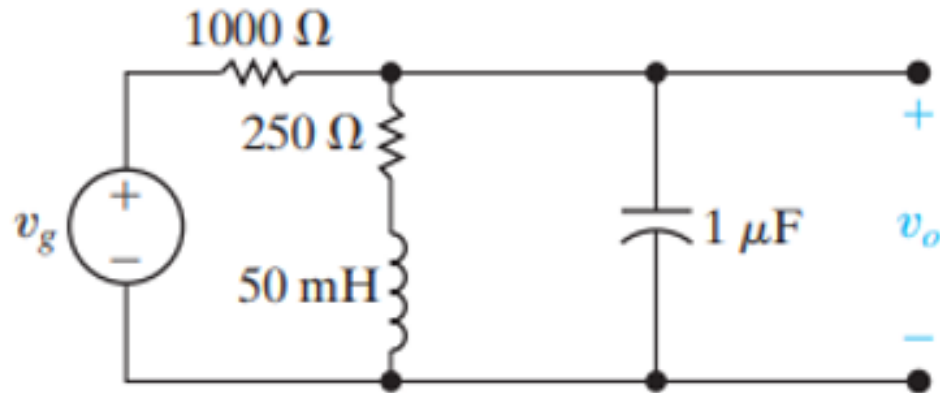
**Ex-2:** For the circuit shown below, the sinusoidal source voltage is  $120 \cos(5000t + 30^\circ)$  V. Find the steady-state expression for  $v_o$ .


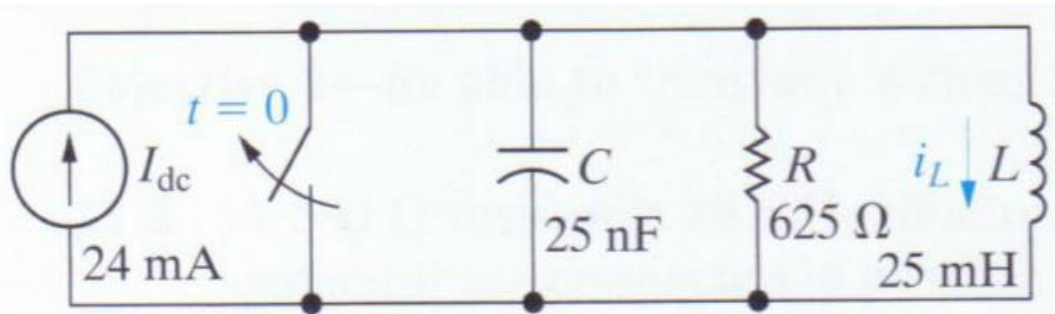
## **The Impulse Function in Circuit Analysis**

- Impulse functions occur in circuit analysis either because of a switching operation or because a circuit is excited by an impulsive source.
- If we create the frequency domain equivalent circuit correctly, these impulse functions are handled as a routine matter in the course of solving the frequency domain circuit equations.

**Ex-3:** Step Response of a Parallel RLC Circuit.




Find the current  $i_L$  through the inductor for  $t > 0$ .

Assume that the switch has been closed for “a long time”.

**Ex-4:** A  $500 \text{ } \Omega$  resistor, a  $16 \text{ mH}$  inductor, and a  $25 \text{ nF}$  capacitor are connected in parallel. Find the zeros and poles.

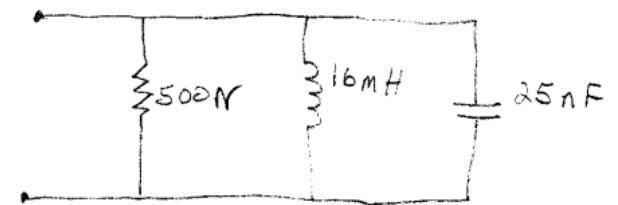
Analyze the circuit and find the zeros and poles.



**Ex-5:** In the circuit above, the capacitor  $C_1$  is charged to an initial voltage  $V_0$  prior to closing the switch at  $t = 0$ .

The capacitor  $C_2$  is discharged so that  $V_{C2} = 0$  prior to closing the switch at  $t = 0$ .

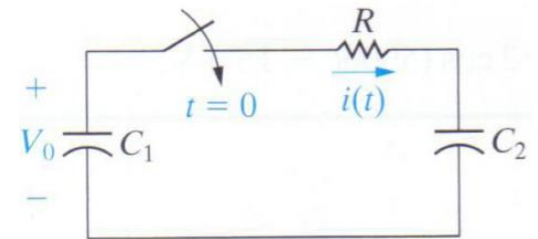
Analyze the circuit and find the current  $i(t)$  expression.


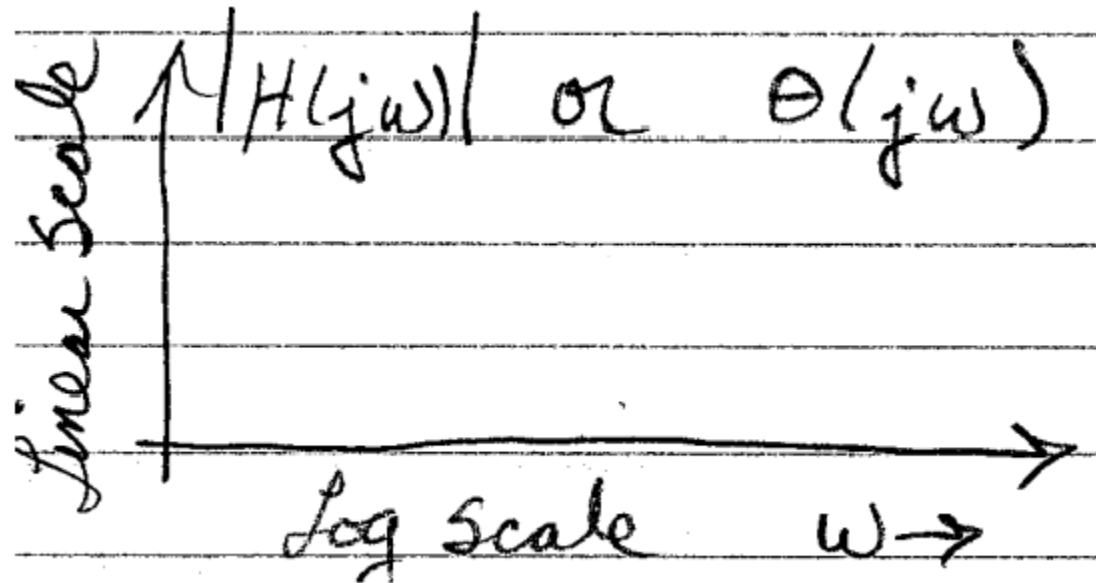
## **Bode Diagram**

- A Bode diagram is a graphical technique that gives a feel for the frequency response of the circuit.
- Diagrams are named after Hendrick W. Bode.
- Dr. Bode was an engineer for Bell Telephone Laboratories. He proposed this approach now known by his name.
- We can approximate the complete frequency response by selecting a few appropriate frequencies. Then we draw a straight-line approximation to the complete response.
- There are many software programs that can plot the frequency response very accurately. But as always, the “hand” analysis confirms the validity of the computer program.
- A Bode diagrams consists of two separate plots. One plot shows how the amplitude of  $H(j\omega)$  varies with frequency. The other plot shows how the phase  $\theta(j\omega)$  varies with frequency.

- The plots are made on semi log paper so that a wide range of frequency values may be plotted.



- The magnitude is given in decibels.

## What is Decibel (dB)

- A unit used to measure the intensity of a sound or the power level of an electrical signal.
- The decibel (symbol: dB) is a relative unit of measurement corresponding to one tenth of a bel (B). It is used to express the ratio of one value of a power quantity to another, on a logarithmic scale.

$$1 \text{ dB} = 10 \log \left[ \frac{P_1}{P_2} \right]$$

- dB for a voltage quantity.

$$\begin{aligned} 10 \log_{10} \left( \frac{P_1}{P_2} \right) &= 10 \log_{10} \left( \frac{\frac{V_1^2}{R_1}}{\frac{V_2^2}{R_2}} \right) = 10 \log_{10} \left( \frac{V_1^2}{V_2^2} \frac{R_2}{R_1} \right) \\ &= 10 \log_{10} \left( \frac{V_1}{V_2} \right)^2 + 10 \log_{10} \left( \frac{R_2}{R_1} \right) \\ &= 20 \log_{10} \left( \frac{V_1}{V_2} \right) + 10 \log_{10} \left( \frac{R_2}{R_1} \right) \end{aligned}$$



If  $R_1 = R_2$  then

$$dB = 20 \log_{10} \left( \frac{V_1}{V_2} \right) + 10 \log_{10} (1) = 20 \log_{10} \left( \frac{V_1}{V_2} \right)$$

- dB for a current quantity.

$$\begin{aligned} 10 \log_{10} \left( \frac{P_1}{P_2} \right) &= 10 \log_{10} \left( \frac{I_1^2 R_1}{I_2^2 R_2} \right) \\ &= 10 \log_{10} \left( \frac{I_1}{I_2} \right)^2 + 10 \log_{10} \left( \frac{R_1}{R_2} \right) \end{aligned}$$

If  $R_1 = R_2$  then

$$dB = 20 \log_{10} \left( \frac{I_1}{I_2} \right) + 10 \log_{10} (1) = 20 \log_{10} \left( \frac{I_1}{I_2} \right)$$

## Magnitude in terms of Linear versus dB

Linear A Voltage or Current	A <sub>dB</sub>
$10^{-6}$	-120
$10^{-5}$	-100
$10^{-4}$	-80
$10^{-3}$	-60
$10^{-2}$	-40
$10^{-1}$	-20
$\frac{1}{2}$	-6
$\frac{1}{\sqrt{2}} = 0.707$	-3
$10^0 = 1$	0
$1.41 = \sqrt{2}$	3
2	6
$10^1$	20
$10^2$	40
$10^3$	60
$10^4$	80
$10^5$	100
$10^6$	120

## Bode Plot for Real, First-Order Poles and Zeros

- As mentioned before, bode diagrams consists of two separate plots; **Amplitude** plot and the **Phase** plot.

### Straight-Line Amplitude Plots:

- The straight-line magnitude plot has the following rules:
- Change the transfer function into standard format which can be one of the following types:



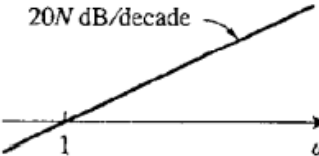

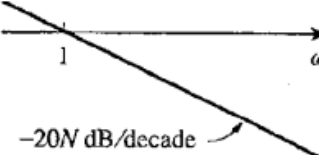

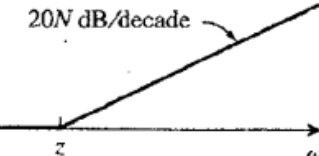
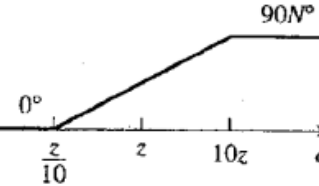
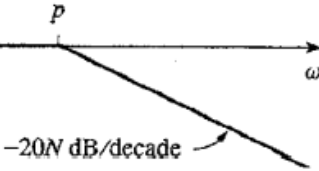
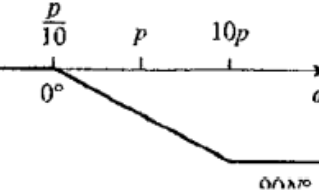
$$H(s) = \frac{K(1+\frac{s}{z_1})(1+\frac{s}{z_2})(1+\frac{s}{z_3})}{(1+\frac{s}{p_1})(1+\frac{s}{p_2})(1+\frac{s}{p_3})} \quad H(s) = \frac{Ks(1+\frac{s}{z_1})(1+\frac{s}{z_2})(1+\frac{s}{z_3})}{(1+\frac{s}{p_1})(1+\frac{s}{p_2})(1+\frac{s}{p_3})} \quad H(s) = \frac{K(1+\frac{s}{z_1})(1+\frac{s}{z_2})(1+\frac{s}{z_3})}{s(1+\frac{s}{p_1})(1+\frac{s}{p_2})(1+\frac{s}{p_3})}$$

- First order Zeros will have a slope = 20 dB / decade
- First order Poles will have a slope = -20 dB / decade
- Slopes will start at the corner frequency.
- “K” will contribute a constant value in the plot = 20 log K

## Straight-Line Phase Plots:

- The phase angle associated with the constant “K” is zero.
- The phase angle associated with a first-order zero or pole at the origin is a constant,  $+90^\circ$  for zeros and  $-90^\circ$  for poles.
- For a first-order zero or pole not at the origin, the straight-line approximations are as follows:
  - For frequencies less than one tenth the corner frequency, the phase angle is assumed to be zero.
  - For frequencies greater than 10 times the corner frequency, the phase angle is assumed to be  $+90^\circ$  and  $-90^\circ$  for zeros and poles respectively.
  - Between one tenth the corner frequency and 10 times the corner frequency, the phase angle plot is a straight line that goes through  $0^\circ$  at one-tenth the corner frequency,  $\pm 45^\circ$  at the corner frequency, and  $\pm 90^\circ$  at 10 times the corner frequency.

# Summary of Bode straight-line magnitude and phase plots.

Factor	Magnitude	Phase
$K$	$20 \log_{10} K$ 	$0^\circ$ 
$(j\omega)^N$	$20N \text{ dB/decade}$ 	$90N^\circ$ 
$\frac{1}{(j\omega)^N}$	$-20N \text{ dB/decade}$ 	$-90N^\circ$ 
$\left(1 + \frac{j\omega}{z}\right)^N$	$20N \text{ dB/decade}$ 	$0^\circ$ to $90N^\circ$ 
$\frac{1}{(1 + j\omega/p)^N}$	$-20N \text{ dB/decade}$ 	$0^\circ$ to $-90N^\circ$ 

**Ex-6:** Draw Bode diagram for the following Transfer function.

$$H(s) = \frac{100(s+1)}{(s+10)(s+100)}$$

**Ex-7:** Draw Bode plot for the following Transfer function.

$$H(s) = \frac{50(s+200)(s+2000)}{(s+20)(s+20000)}$$

**Ex-8:** Draw Bode plot for the following Transfer function.

$$H(s) = \frac{100s}{(s+10)(s+100)}$$

**Ex-9:** Draw Bode plot for the following Transfer function.

$$H(s) = \frac{10000(s+1)}{(s+10)(s+100)^2}$$

## **Bode Plot for Complex Poles and Zeros**

- Complex poles/zeros in the expression for  $H(s)$  require special attention when you make amplitude and phase angle plots.
- The complex poles and zeros of  $H(s)$  always appear in conjugate pairs.
- The first step in making either an amplitude or a phase angle plot of a transfer function that contains complex poles is to combine the conjugate pair into a single quadratic term.
- Express conjugate pair in the form:  $s^2 + 2\zeta\omega_n s + \omega_n^2$
- Then change it into standard form:  $1 + (s/\omega_n)^2 + 2\zeta(s/\omega_n)$

### **Straight-Line Amplitude Plots:**

- For  $\omega < \omega_n$ , the straight line lies along the 0 dB axis.
- For  $\omega = \omega_n$ , the amplitude is 0 dB.
- For  $\omega > \omega_n$ , the straight line has a slope of -40 dB/decade.

## Straight-Line Phase Plots:

- For  $\omega = \omega_n$ , phase is  $\pm 90^\circ$ .
- The straight-line approximations are as follows:
  - For frequencies less than one tenth the corner frequency, the phase angle is assumed to be zero.
  - For frequencies greater than 10 times the corner frequency, the phase angle is assumed to be  $+180^\circ$  and  $-180^\circ$  for zeros and poles respectively.
  - Between one tenth the corner frequency and 10 times the corner frequency, the phase angle plot is a straight line that goes through  $0^\circ$  at one-tenth the corner frequency,  $\pm 90^\circ$  at the corner frequency, and  $\pm 180^\circ$  at 10 times the corner frequency.



**Ex-10:** Draw Bode plot for the following Transfer function.

$$H(s) = \frac{4(s+25)}{(s^2+4s+100)}$$