

**Midterm II EEE 117 Date 04/12/2022 (1:30 - 2:45 p.m.)**



**SOLUTION MUST BE HAND WRITTEN AND SUBMIT THEM BEFORE 3:00 P.M.**

**Q-1** The switch in the circuit shown below has been in position x for a long time. At  $t=0$ , the switch moves instantaneously to position y. **(40 points)**

a) Construct an s-domain circuit for  $t > 0$

b) Find  $I_o$

c) Find  $i_o$

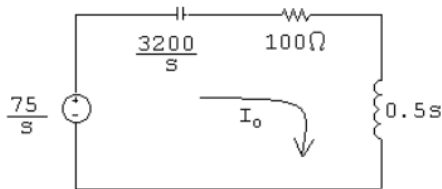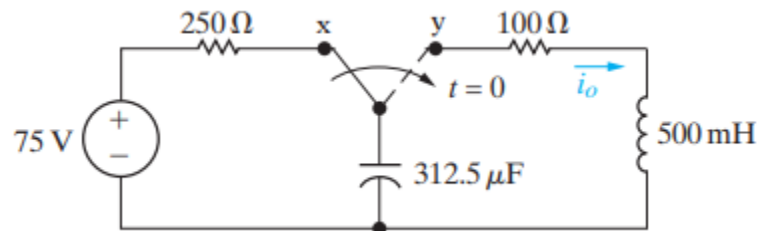

$$\begin{aligned}
 \text{[b]} \quad I_o &= \frac{75/s}{(3200/s) + 100 + 0.5s} \\
 &= \frac{75}{0.5s^2 + 100s + 3200} \\
 &= \frac{150}{(s^2 + 200s + 6400)} = \frac{150}{(s + 40)(s + 160)}
 \end{aligned}$$

$$\text{[c]} \quad I_o = \frac{K_1}{s + 40} + \frac{K_2}{s + 160}$$

$$K_1 = \frac{150}{s + 160} \Big|_{s=-40} = 1.25$$

$$K_2 = \frac{150}{s + 40} \Big|_{s=-160} = -1.25$$


$$I_o = \frac{1.25}{s + 40} - \frac{1.25}{s + 160}$$

$$i_o(t) = (1.25e^{-40t} - 1.25e^{-160t})u(t) \text{ A}$$


**Q-2** There is no energy stored in the circuit shown below at  $t=0^-$  **(20 points)**

a) Construct an s-domain circuit for  $t > 0$

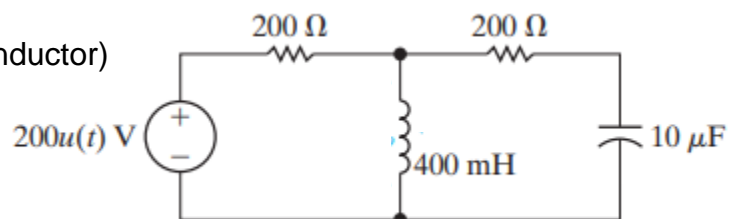b) Find  $V_o(s)$  (Voltage across inductor)



**[a]**

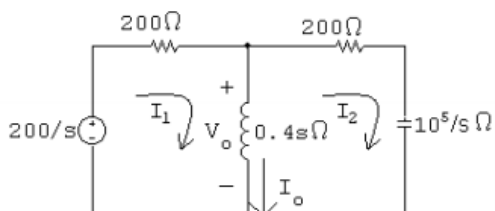


$$\text{[b]} \quad V_o = 0.4sI_o = \frac{100(s + 500)}{s^2 + 500s + 125,000}$$


**Q-3** Draw Straight line Bode diagram for Amplitude and Phase. **(40 points)**

Draw on Semi log sheet and show both individual and combined results.

(Ignore damping effect)
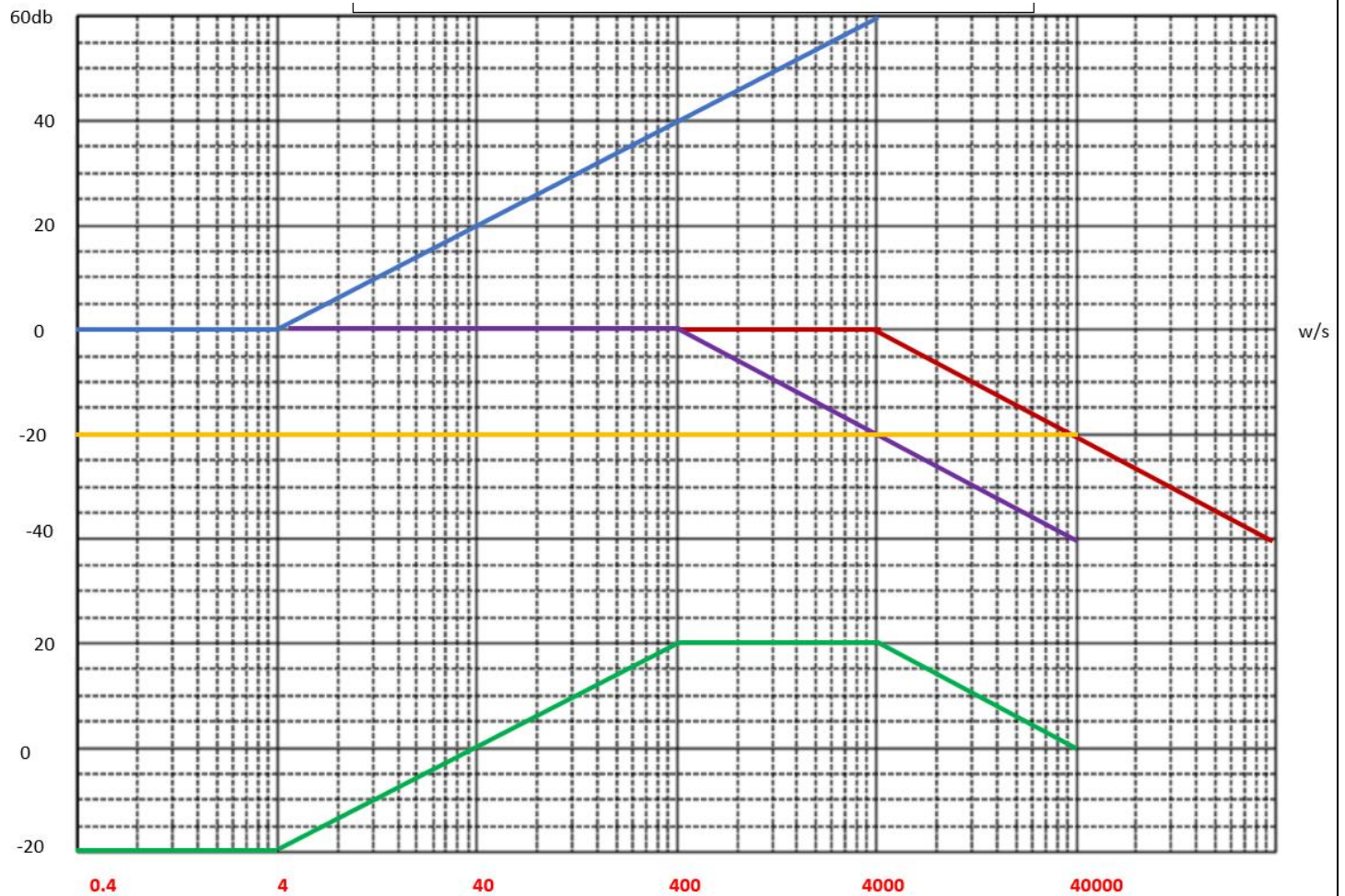
$$a) H(s) = \frac{40000(s+4)}{(s+400)(s+4000)} = \frac{0.1(1+\frac{s}{4})}{(1+\frac{s}{400})(1+\frac{s}{4000})}$$



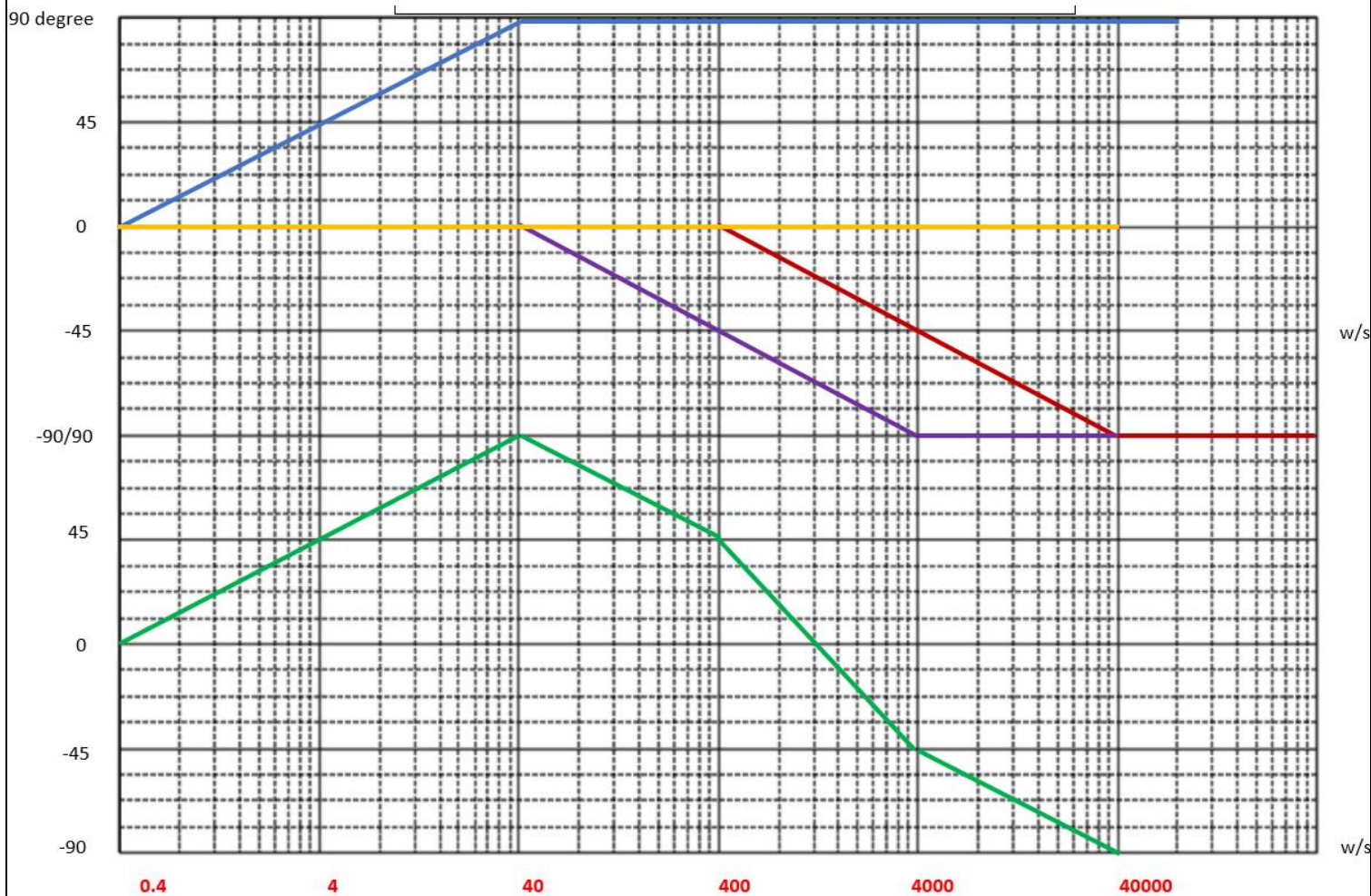



$$\text{b) } H(s) = \frac{10(s^2 + 2s + 1)}{(s^2 + 5s + 100)} = \frac{0.1(1 + \frac{s}{1})^2}{1 + (\frac{s}{10})^2 + 0.5(\frac{s}{10})}$$

