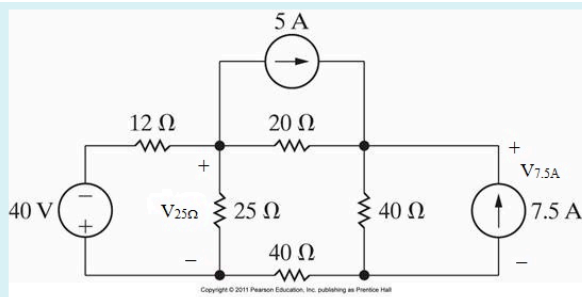


①



Q1d

a) Find the voltage across the 7.5A current source.

$$V_{7.5A} = 216 \text{ Volts}$$

b) Find the voltage across the 25 Ω (Ohm) resistor.

$$V_{25\Omega} = -10 \text{ Volts}$$

$$I_1: -40 - 12I_1 - 25(I_1 - I_2) = 0$$

$$-40 - 12I_1 - 25I_1 + 25I_2 = 0$$

$$-37I_1 + 25I_2 = 40$$

$$I_2: 25(I_1 - I_2) - 20(I_2 - I_4) - 40(I_2 - I_3) - 40I_2 = 0$$

$$25I_1 - 125I_2 + 100 - 300 = 0$$

$$25I_1 - 125I_2 = 200$$

$$I_1 - 5I_2 = 8$$

$$-37I_1 + 25I_2 = 40$$


$$I_1 - 5I_2 = 8$$

$$\begin{aligned} I_1 &= -2.5 \text{ A} \\ I_2 &= -2.1 \text{ A} \end{aligned}$$

$$V_{25} = 25(I_1 - I_2) = 25(-2.5 + 2.1) = -10 \text{ V}$$

$$V_{7.5} = 40(I_2 - I_3) = 40(-2.1 - (-3.5)) = 216 \text{ V}$$

②

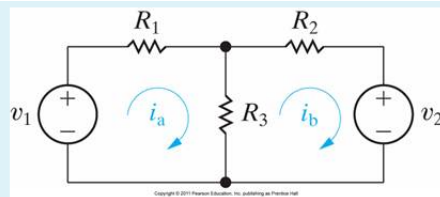

Q2b

Given:

$$v_1 = 14 \text{ Volts}$$

$$v_2 = 7 \text{ Volts}$$

$$R_1 = 10 \Omega \text{ (Ohms)}$$

$$R_2 = 20 \Omega \text{ (Ohms)}$$

$$R_3 = 40 \Omega \text{ (Ohms)}$$

Find the currents i_a and i_b .

$$i_a = 400 \text{ mA (milli Amp)}$$

$$i_b = 150 \text{ mA (milli Amp)}$$

$$i_a: v_1 - R_1 i_a - R_3 (i_a - i_b) = 0$$

$$14 - 10i_a - 40i_a + 40i_b = 0$$

$$-50i_a + 40i_b = -14$$

$$i_b: R_3 (i_a - i_b) - R_2 i_b - v_2 = 0$$

$$40i_a - 40i_b - 20i_b - 7 = 0$$


$$-50i_a + 40i_b = -14$$

$$40i_a - 60i_b = 7$$

$$i_a = 0.40 \text{ A} \approx 400 \text{ mA}$$

$$i_b = 0.150 \text{ A} \approx 150 \text{ mA}$$

③

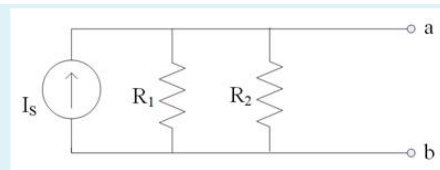

Q3f

Given: $I_s = 10 \text{ A}$ $R_1 = 10 \Omega \text{ (Ohms)}$ $R_2 = 40 \Omega \text{ (Ohms)}$

Perform a source transformation and find the voltage transform equivalent of this circuit.


$$V_{transform} = 80 \text{ V}$$

$$R_{transform} = 8 \Omega \text{ (Ohm)}$$

$$R = R_1 \parallel R_2 = \frac{10(40)}{10+40} = 8 \Omega$$

$$V_s = i_s R = (10 \text{ A})(8 \Omega) = 80 \text{ V}$$

④

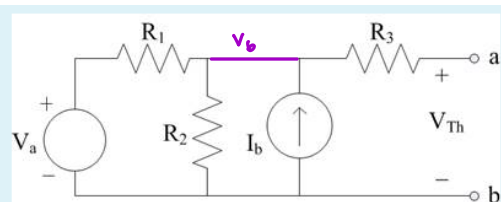

Q4e

Given:

$$V_a = 20 \text{ Volts}$$

$$I_b = 6 \text{ Amps}$$

$$R_1 = 40 \Omega \text{ (Ohm)}$$

$$R_2 = 40 \Omega \text{ (Ohm)}$$

$$R_3 = 10 \Omega \text{ (Ohm)}$$

a) Find the Thévenin equivalent voltage V_{Th} .

$$V_{Th} = 130 \text{ Volts}$$

b) Find the Thévenin equivalent resistance R_{Th} .

$$R_{Th} = 30 \Omega \text{ (Ohms)}$$


$$\text{NODE } V_b: \frac{V_b - 20}{40} + \frac{V_b}{40} - 6 \text{ A} = 0$$

$$V_b - 20 + V_b - 240 = 0$$

$$V_b = 130 \text{ V} = V_{Th}$$

$$R_{Th} = 40 \parallel 40 + 10 = 30 \Omega$$

5


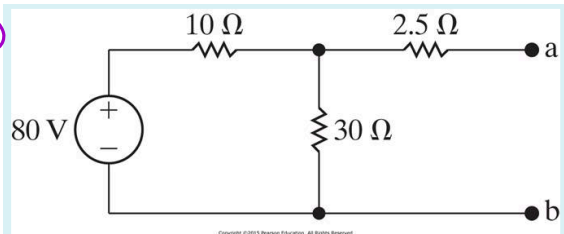


Q5b


Find the Norton equivalent circuit with respect to terminals ab.

$I_N = 6$ ✓ A

$R_{TH} = 10$ ✓ Ω (Ohm)

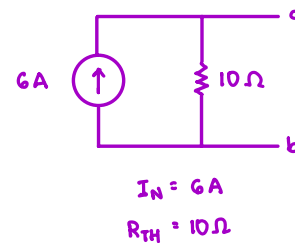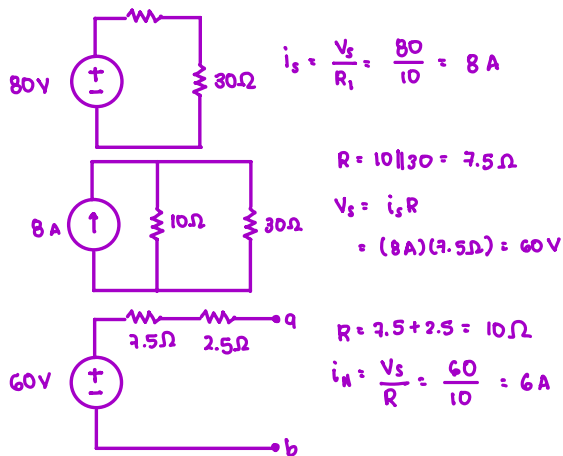

6

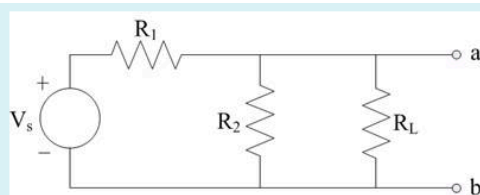

Q6h

Given:


$V_s = 40$ Volts $R_1 = 140$ Ω (Ohm) $R_2 = 56$ Ω (Ohm)

a) Find the value of R_L that results in maximum power being transferred to R_L .


$R_{L,max\ power} = 40$ ✓ Ω (Ohms)

b) Find the maximum power that can be delivered to R_L .

$P_{R_L,max\ power} = 0.8163$ ✓ Watts

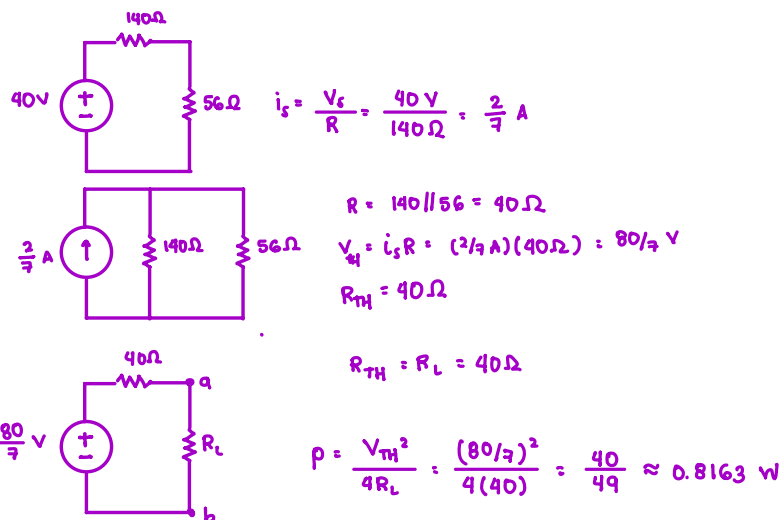

7

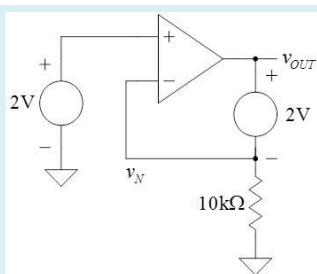

Q7c

Assume that the operational amplifier is ideal.

The opamp has two power inputs (not shown) of $+V_{CC} = +15V$ and $-V_{CC} = -15V$.


Determine the voltage v_{out} .

$v_{out} = 4$ ✓ Volts

$V_N = 2V$

$v_{out} = V_N + 2V = 2V + 2V = 4V$

8.

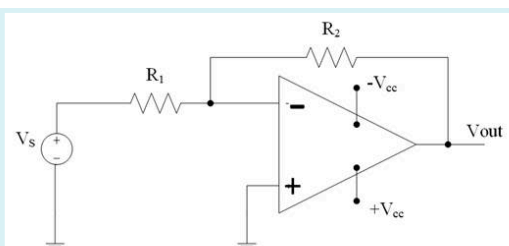

Q8b

Assume that the operational amplifier is ideal.

The opamp has two power inputs $+V_{cc} = +15V$ and $-V_{cc} = -15V$.

Given: $V_s = 4.0$ Volts

$R_1 = 33 \text{ k}\Omega$ (kilo Ohm)

$R_2 = 180 \text{ k}\Omega$ (kilo Ohm)

Determine the voltage V_{out} .

$V_{out} =$ ☒ Volts

$$\text{NODE } v_n : \left[\frac{V_s - v_n}{33 \text{ k}\Omega} + \frac{v_n - v_o}{180 \text{ k}\Omega} = 0 \right]$$


$$-180V_s - 33V_o = 0$$

$$V_o = -\frac{180(4.0)}{33} = -21.82 \text{ V}$$

$$-15 \leq V_{cc} \leq 15$$

$$V_o = -15 \text{ V}$$

9.

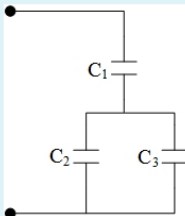

Q9b

Given:

$C_1 = 2 \text{ }\mu\text{F}$ (micro F)

$C_2 = 6 \text{ }\mu\text{F}$ (micro F)

$C_3 = 3 \text{ }\mu\text{F}$ (micro F)

(micro F)


Find the equivalent capacitance C_{Eq} .

$C_{Eq} =$ ☒ μF (micro F)

$$C_2 \parallel C_3 = C_2 + C_3 = 6\mu\text{F} + 3\mu\text{F} = 9\mu\text{F}$$

$$C_{eq} = \frac{(2\mu\text{F})(9\mu\text{F})}{2\mu\text{F} + 9\mu\text{F}} = 1.64 \mu\text{F}$$

10.

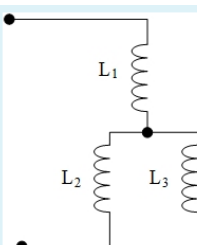

Q10e

Given:

$L_1 = 10 \text{ mH}$ (milli H)

$L_2 = 14 \text{ mH}$ (milli H)

$L_3 = 26 \text{ mH}$ (milli H)

(milli H)

Find the equivalent inductance L_{Eq} .

$L_{Eq} =$ ☒ mH (milli H)

$$L_1 + (L_2 \parallel L_3)$$

$$10\text{mH} + \frac{(14\text{mH})(26\text{mH})}{14\text{mH} + 26\text{mH}} = 19.1 \text{ mH}$$