


Homework-02 ENGR 117 Due date 02/21/2022

5 Questions 20 points each

Q-1 Find the average power delivered by the ideal current source in the circuit

$$i_g = 8 \cos 5000t \text{ A}$$

Here 8 is the max value

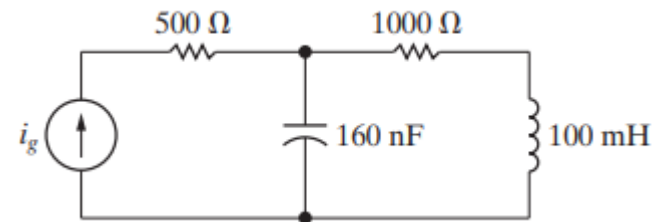


w	5000 rad/s
L	100 mH
C	160 nF

i_g	=	$8 + j 0.0000000$	=	8.0000	L	0	A
R1	=	$500 + j 0.0000000$	=	500.0000	L	0 Deg	Ω
R2	=	$1000 + j 0.0000000$	=	1000.0000	L	0 Deg	Ω
ZL	=	$0 + j 500.0000000$	=	500.0000	L	90 Deg	Ω
ZC	=	$0 + j -1250.0000000$	=	1250.0000	L	-90 Deg	Ω
ZL + R2	=	1000 500.0000000	=	1118.0340	L	26.56505 Deg	Ω
$1/(ZL+R2)$	=	$0.0008 + j -0.0004000$	=	0.0009	L	-26.5651	Ω
$1/ZC$	=	$4.90059E-20 + j 0.0008000$	=	0.0008	L	90 Deg	mho
$1/Zx$	=	$0.0008 + j 0.0004000$	=	0.0009	L	26.56505 Deg	mho
Zx	=	$1000 + j -500.0000000$	=	1118.0340	L	-26.5651 Deg	Ω
Zeq	=	$1500 + j -500.00$	=	1581.1388	L	-18.4349 Deg	Ω

Pavg	48000	Watt
------	-------	------

Q-2 Find the average power dissipated in the $60\ \Omega$ resistor in the circuit
 $i_g = 6 \cos 20,000t\ \text{A}$.

Here 6 is the max value

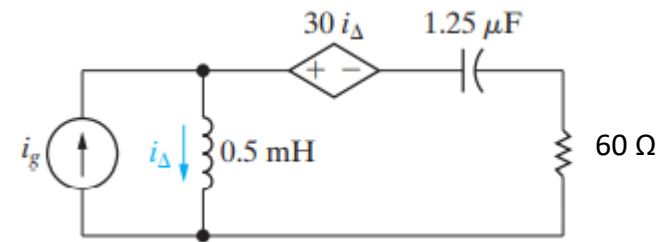

w	20000 rad/s
L	0.5 mH
C	1250 nF

i_g	=	$6 + j\ 0.0000000$	=	6.0000	L	0	A
R	=	$60 + j\ 0.0000000$	=	60.0000	L	$0\ \text{Deg}$	Ω
			=				Ω
Z_L	=	$0 + j\ 10.0000000$	=	10.0000	L	$90\ \text{Deg}$	Ω
Z_C	=	$0 + j\ -40.0000000$	=	40.0000	L	$-90\ \text{Deg}$	Ω
$Z_C + R$	=	$60 + j\ -40.0000000$	=	72.1110	L	$-33.6901\ \text{Deg}$	Ω
$Z_L(Z_C + R)$	=	$400 + j\ 600.0000000$	=	721.1103	L	56.30993	Ω
$1/Z_L$	=	$6.12574\text{E-}18 + j\ -0.1000000$	=	0.1000	L	$-90\ \text{Deg}$	mho
$1/(Z_C + R)$	=	$0.011538462 + j\ 0.0076923$	=	0.0139	L	$33.69007\ \text{Deg}$	mho
$1/(Z_L)(Z_C + R) = \text{XXX}$	=	$0.000769231 + j\ -0.0011538$	=	0.0014	L	$-56.3099\ \text{Deg}$	
$30(\text{XXX})$	=	$0.023076923 + j\ -0.0346154$	=	0.0416	L	$-56.3099\ \text{Deg}$	
cccc	=	$-0.011538462 + j\ -0.057692308$	=	0.0588	L	$258.6901\ \text{Deg}$	


V		101.9804	-258.69
---	--	----------	---------

V	$-20 + j\ 100.0000000$	101.9804	L	$101.3099\ \text{Deg}$
I_{Δ}	$10 + j\ 2.0000000$	10.1980	L	$11.30993\ \text{Deg}$
$I_{60} = I_g - I_{\Delta}$	$-4 + j\ -2$	4.4721	L	$206.5651\ \text{Deg}$

P 60-ohm	=	600	Watt
----------	---	-----	------

Q-3 Find the average power, the reactive power, and the apparent power supplied by the voltage source in the circuit
 $v_g = 40 \cos 10^6 t$ V.

Here 40 is the max value

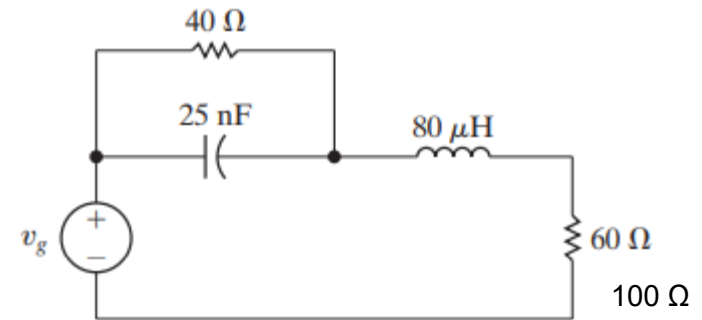

w 1000000 rad/s
 L 0.08 mH
 C 25 nF

Vg	=	40 + j 0.0000000	=	40.0000	L	0	A
R1	=	40 + j 0.0000000	=	40.0000	L	0 Deg	Ω
R2	=	100 + j 0.0000000	=	100.0000	L	0 Deg	Ω
ZL	=	0 + j 80.0000000	=	80.0000	L	90 Deg	Ω
ZC	=	0 + j -40.0000000	=	40.0000	L	-90 Deg	Ω
ZL + R2	=	100 + j 80	=	128.0625	L	38.65981 Deg	Ω
1/ZC	=	1.53144E-18 + j 0.0250000	=	0.0250	L	90 Deg	Ω
1/R1	=	0.025 + j 0.0000000	=	0.0250	L	0 Deg	mho
1/X = (1/R1)+(1/ZC)	=	0.025 + j 0.025	=	0.0354	L	45 Deg	mho
X	=	20 + j -20.0000000	=	28.2843	L	-45 Deg	
Zeq	=	120 + j 60	=	134.1641	L	26.56505 Deg	
Ig = Vg/Zeq	=	0.2667 + j -0.1333	=	0.2981	L	-26.5651 Deg	
Ig (Conj)	=	0.2667 + j 0.1333	=	0.2981	L	26.56505 Deg	
Sg = 1/2 (Vg * Ig(conj))	=	5.3333 + j 2.6667	=	5.9628	L	26.56505 Deg	
P(avg)	=	5.3333 Watts					
Q(reactive)	=	2.6667 VAR					
 S (Apparent)	=	5.9628 VA					

- Q-4** A single-phase source is applied to a two-terminal, passive circuit with equivalent impedance $Z = 2.0 \angle -45^\circ \Omega$ measured from the terminals. The source current is $i(t) = 4\sqrt{2} \cos(\omega t)$ kA. Determine the (a) instantaneous power, (b) real power, and (c) reactive power delivered by the source. (d) Also determine the source power factor.

Here current is max value representation

$$Z = 2 \angle -45^\circ \Omega$$

$$i(t) = 4\sqrt{2} \cos \omega t \text{ kA} \Rightarrow I_{rms} = 4 \text{ kA}$$

$$V(t) = (4\sqrt{2} \cos \omega t)(2 \angle -45^\circ) = (4\sqrt{2} \angle 0^\circ)(2 \angle -45^\circ)$$

$$V(t) = 8\sqrt{2} \angle -45^\circ \text{ kV} \Rightarrow V_{rms} = 8 \text{ kV}$$

$$\theta_v = -45^\circ \quad \theta_i = 0^\circ \Rightarrow \theta_v - \theta_i = \phi = -45^\circ$$

$$\text{a) } p(t) = 22.63 + 32 \cos(2\omega t - 45^\circ) \text{ MW}$$


$$\text{b) } P = V_{rms} I_{rms} \cos \phi = 8 \times 4 \cos(-45^\circ) = 22.62 \text{ MWatt}$$

$$\text{c) } Q = V_{rms} I_{rms} \sin \phi = 8 \times 4 \sin(-45^\circ) = -22.62 \text{ MVAR}$$

$$\text{d) } P.F = \cos \phi = \cos(-45^\circ) = 0.707 \text{ Leading}$$

- Q-5** The real power delivered by a source to two impedances, $Z_1 = 3 + j4 \Omega$ and $Z_2 = 10 \Omega$, connected in parallel, is 1100 W. Determine (a) the real power absorbed by each of the impedances and (b) the source current.

Here V is RMS value representation

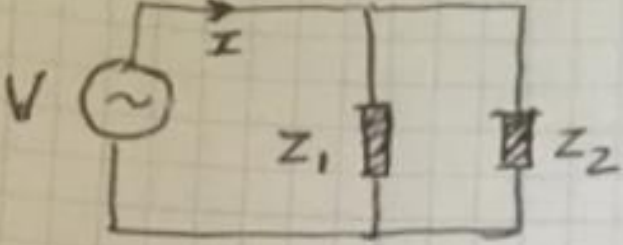
$$\begin{aligned} P &= 1100 \text{ W} \\ Z_1 &= 3 + j4 = 5 \angle 53.13^\circ \Omega \\ Z_2 &= 10 + j0 = 10 \angle 0^\circ \Omega \\ Z_T &= \frac{Z_1 \times Z_2}{Z_1 + Z_2} = 3.676 \angle 36.03^\circ \\ I &= \frac{V}{3.676 \angle 36.03^\circ} \Rightarrow I^* = \frac{V^*}{3.676 \angle 36.03^\circ} \\ \bar{S} &= V I^* = \frac{V \times V^*}{3.676 \angle 36.03^\circ} = V^2 (0.272 \angle +36^\circ) \\ \bar{S} &= V^2 (0.22 - j0.1598) = \underline{0.22 V^2} - j0.1598 V^2 \\ 0.22 V^2 &= 1100 \Rightarrow \boxed{V = 70.71 \text{ V}} \end{aligned}$$

a)

$$I_1 = \frac{V}{Z_1} \Rightarrow \boxed{I_1 = \frac{V}{5 \angle 53.13}} \Rightarrow \boxed{I_1^* = \frac{V^*}{5 \angle -53.13}}$$

$$\bar{S}_1 = V I_1^* = V \times \frac{V^*}{5 \angle -53.13} = V^2 (0.2 \angle 53.13)$$

$$\bar{S}_1 = V^2 (0.12 + 0.16j)$$

$$\boxed{P_1} = 0.12 V^2 = 0.12 \times (70.71)^2 = \boxed{600 \text{ Watt}}$$

$$I_2 = \frac{V}{Z_2} = \frac{V}{10 \angle 0} = 0.1 V \angle 0 \Rightarrow \boxed{I_2^* = 0.1 V^* \angle 0}$$

$$\bar{S}_2 = V I_2^* = V \cdot V^* (0.1 \angle 0) = V^2 (0.1 + 0j)$$

$$\boxed{P_2} = 0.1 V^2 = 0.1 \times (70.71)^2 = \boxed{500 \text{ Watt}}$$

b)

$$I = \frac{V}{Z_T}$$

$$I = 19.23 \angle -36.03^\circ \text{ A}$$