

Lab 3

Part 2: Pseudorandom Number Generator

A linear feedback shift register (LFSR) is a shift register whose input bit is the output of a linear logic function of two or more of its previous states. The LFSR circuit can be used as pseudorandom number generator. This project is a design of a 5-stage LFSR circuit shown below.

 


Figure 1. 5-stage LFSR diagram

Demo Requirement

Make sure that this LFSR design uses a non-zero value as the initial seed value. You need to demonstrate the final simulation waveform of this design to your lab instructor and show that the value of Q_4 (drops to 0) repeats every 31 clock cycles.

Lab Procedure

Step 1. LFSR Design Review

 


Figure 2. 4-stage LFSR diagram

Review the above circuit you have learnt in class with the VHDL design below.

Library ieee;

Use ieee.std_logic_1164.all;

Entity lfsr is

Port (reset, clk: in std_logic;

Q: out std_logic_vector (3 downto 0));

End lfsr;

Architecture beh of lfsr is

Signal m: std_logic_vector (3 downto 0);

Begin

Process(reset, clk)

Begin

If (reset = '1') then

m <= (0 => '1', others => '0'); --- value of "0001"

elsif (rising_edge(clk)) then

m(3 downto 1) <= m(2 downto 0);

m(0) <= m(2) xor m(3);

end if;

end process;

Q <= m;

```
end beh;
```

Step 2. LFSR Testbench Design Review for Fig. 2 Circuit

```
Library ieee;
```

```
Use ieee.std_logic_1164.all;
```

```
Entity lfsr_tb is
```

```
End lfsr_tb;
```

```
Architecture tb of lfsr_tb is
```

```
signal clk, reset: std_logic;
```

```
signal Q: std_logic_vector (3 downto 0);
```

```
component lfsr
```

```
Port ( reset, clk: in std_logic;
```

```
Q: out std_logic_vector (3 downto 0) );
```

```
End component;
```

```
Begin
```

```
uut: lfsr port map(reset, clk, Q);
```

```
Process
```

```
Begin
```

```
Clk <= '0';
```

```
Wait for 5 ns;
```

```
Clk <= '1';
```

```
Wait for 5 ns;
```

```
End process;
```

```
Process
```

```
Begin
```

```
Reset <= '1';
```

```
Wait for 2 ns;
```

CPE166 Lab 3 Part 2

By: Prof. Pang

```

Reset <= '0';


Wait for 200 ns;

Wait;

End process;

End tb;

```

 Step 3. LFSR Design and Testbench Simulation of Fig. 1 Circuit

Steps 1 and 2 are for optional exercise purposes.

Step 3 is a required task for this laboratory experiment.

You need to write a VHDL design and testbench for this 5-stage LFSR, and run simulations to verify that the value of Q (4 downto 0) repeats every 31 clock cycles.