

FINAL EEE 117 Date 05/19/2022 (12:45 - 2:45 p.m.)

SOLUTION MUST BE HAND WRITTEN AND SUBMIT THEM BEFORE 3:00 P.M.

5 Questions Each 20 points

Q-1: True or False

- a) A relative motion of magnetic field and a conductor outside the field induced emf.
- b) Sinusoidal signal is represented only by Sine function.
- c) Phasor is a complex number that represents the only the amplitude at $t=0$ of a sinusoidal function.
- d) RMS voltage can be calculated as: $V_{rms} = V_m/2$
- e) In a purely capacitive circuit, voltage lags the current by 90 degrees.
- f) The phenomenon of mutual inductance occurs when one circuit is physically connected with other circuit.
- g) An ideal transformer gives output power exactly equal to the input power.
- h) Complex power is the complex sum of real and reactive power measured in watts.
- i) Power factor is the fraction of system capability that can be actually utilized.
- j) An ideal capacitor does not dissipate real power.


- k)** The roots of the denominator of a polynomial are called the poles and the roots of the numerator are called the zeros of $F(s)$.
- l)** Complex poles and zeros always appear in conjugate pairs.
- m)** A straight line Bode diagrams consists of two separate plots. One for amplitude and other for phase.
- n)** The Bode plots are drawn on semi log paper so that a wide range of amplitude values may be plotted.
- o)** $1 \text{ dB} = 20 \log \left[\frac{P_1}{P_2} \right]$ where P represents power
- p)** First order Zeros will have a slope = 20 dB / decade and Poles will have a slope = -20 dB / decade.
- q)** The phase angle associated with the constant “K” is zero.
- r)** Phase angle of an active low pass filter is -45 degree.
- s)** In delta connection, phase voltage = Line voltage.
- t)** Center frequency is the geometric mean of two corner frequencies.

Q-2: Design a series RLC bandpass filter. The center frequency of the filter is 12 kHz, and the quality factor is 4. Use a 7 μF capacitor. (Show your circuit)

- a) Specify the values of R and L.
- b) What is the lower cutoff frequency in kilohertz?
- c) What is the upper cutoff frequency in kilohertz?
- d) What is the bandwidth of the filter in kilohertz?

Q-3: For the circuit shown below:

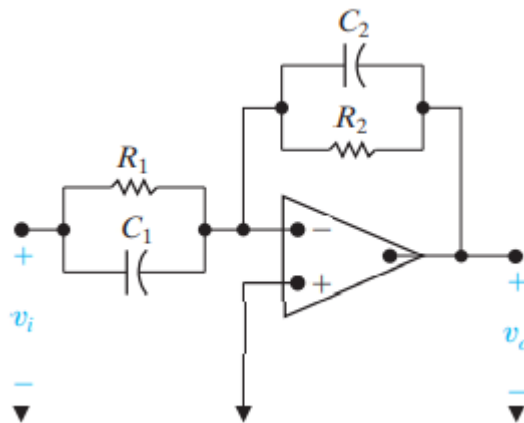- a) Find the transfer function of the circuit.
- b) What is the $H(j\omega)$ of the circuit as $\omega \rightarrow 0$?
- c) What is the $H(j\omega)$ of the circuit as $\omega \rightarrow \infty$?
- d) Find the expression of corner frequency.



Q-4: A balanced three-phase Y-connected generator with negative sequence has an impedance of $0.3 + j0.7 \Omega/\phi$ and an internal voltage of $140 \text{ V}/\phi$. The generator feeds a balanced three-phase Y-connected load having an impedance of $48 + j32 \Omega/\phi$. The impedance of the line connecting the generator to the load is $1.1 + j1.8 \Omega/\phi$. The a-phase internal voltage of the generator is specified as the reference phasor.

- a)** Construct the a-phase equivalent circuit of the system.
- b)** Find the three-line currents I_{aA} , I_{bB} and I_{cC}
- c)** Find the three phase voltages at the load V_{AN} , V_{BN} and V_{CN}
- d)** Find the line voltages V_{AB} , V_{BC} and V_{CA} at the terminals of the load.
- e)** Find the phase voltages at the terminals of the generator V_{an} , V_{bn} and V_{cn} .
- f)** Find the line voltages V_{ab} , V_{bc} and V_{ca} at the terminals of the generator.

Q-5: The **b**-phase voltage of a balanced three-phase Y-Y connected system is $350 \angle -35^\circ$. If the phase sequence is positive, what is the value of V_{CA} ?