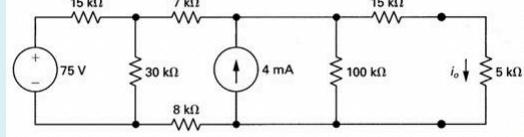


①



P4.51_6ed

Use source transformations to:


a) Find the current i_o through the $5\text{k}\Omega$ (kilo Ohm) resistor.

$$i_o = 3 \text{ mA} \quad (\text{milli Amp})$$


b) Find the power absorbed/delivered by the 75V voltage source.

$$P_{75V} = -105 \text{ mW} \quad (\text{milli Watt})$$

PART A:

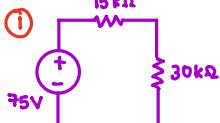

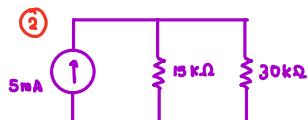
$$i_s = \frac{V_s}{R} = \frac{75V}{15000\Omega} = 0.005 \text{ A} \\ \approx 5 \text{ mA}$$




$$R = 15 \parallel 30 = \frac{15 \cdot 30}{15 + 30} = 10\text{k}\Omega$$
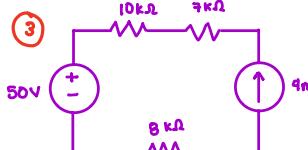
$$V_s = i_s R = (0.005 \text{ A})(10\text{k}\Omega) = 50 \text{ V}$$




$$R = 10 + 7 + 8 = 25\text{k}\Omega$$
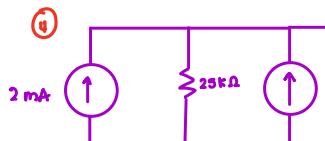
$$i_s = \frac{V_s}{R} = \frac{50V}{25\text{k}\Omega} = 2 \text{ mA}$$




$$R = 25 \parallel 100 = 20\text{k}\Omega$$

$$i_s = 2 \parallel 9 = 6 \text{ mA}$$

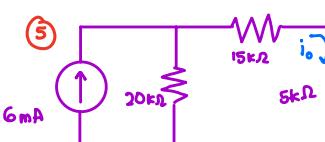

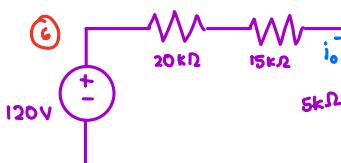
$$V_s = i_s R = (6 \text{ mA})(20\text{k}\Omega) = 120 \text{ V}$$



$$R = 20 + 15 + 5 = 40\text{k}\Omega$$

$$i_o = \frac{V_s}{R} = \frac{120 \text{ V}}{40\text{k}\Omega} = 3 \text{ mA}$$


②

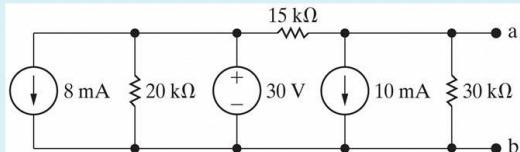

P4.66_8ed

Find the Norton equivalent with respect to the terminals a,b.
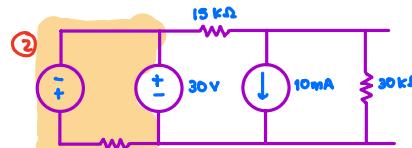
$$I_N = -8 \text{ mA} \quad (\text{milli Amp}) \quad R_{TH} = 10 \text{ k}\Omega \quad (\text{kilo Ohm})$$




NOT INCLUDED




$$R_{TH} = 15 \parallel 30 = 10\text{k}\Omega$$


PART B:

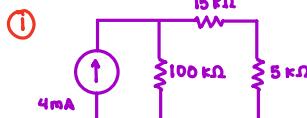

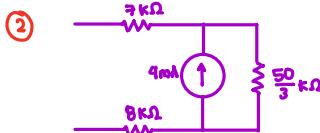
$$R = (15 + 5) \parallel 100 \\ = 50/3 \text{ k}\Omega$$


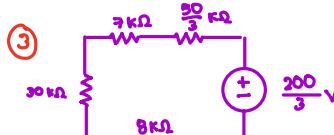
$$V_s = i_s R = (4 \text{ mA})(\frac{50}{3} \text{ k}\Omega) = \frac{200}{3} \text{ V}$$


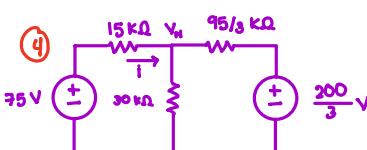
$$R = 7 + \frac{50}{3}/8 + 8 = \frac{95}{3} \text{ k}\Omega$$



$$\text{NODE } V_N: \left[\frac{75 - V_N}{15\text{k}} - \frac{V_N}{30\text{k}} + \frac{200/3 - V_N}{95/3\text{k}} = 0 \right] \text{ K}$$

$$\frac{75}{15} + V_N \left[-\frac{1}{15} - \frac{1}{30} - \frac{3}{95} \right] + \frac{200}{95} = 0$$

$$\frac{5}{28} V_N = \frac{135}{19}$$


$$V_N = 54 \text{ V}$$

$$i = \frac{75 - V_N}{15\text{k}} = \frac{75 - 54}{15\text{k}} = 1.4 \text{ mA}$$


$$P_{75V} = iV = (1.4 \text{ mA})(75\text{V}) = 0.105 \text{ W}$$

≈ 105 mW (-) DELIVERED

①

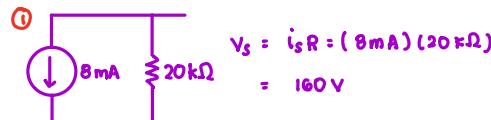
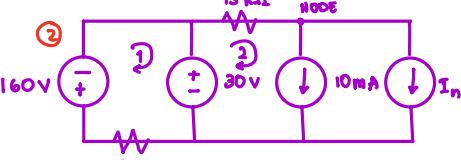
$$V_s = i_s R = (8 \text{ mA})(20\text{k}\Omega) \\ = 160 \text{ V}$$



$$\text{LOOP 2: } 30 - (15\text{k})i_2 = 0$$


$$i_2 = 2 \text{ mA}$$

$$\text{NODE: } \begin{array}{c} 2 \text{ mA} \\ \downarrow \\ 10 \text{ mA} \end{array}$$

$$2 - 10 - I_n = 0$$

$$I_n = -8 \text{ mA}$$

③

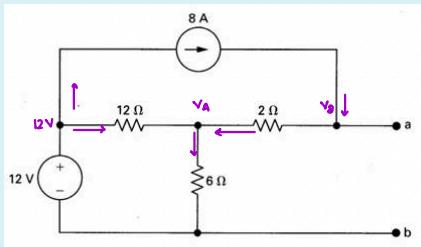

P4.59_6ed

Find the Thévenin equivalent circuit with respect to the terminals a,b for this circuit.

$$V_{Th} = 52 \text{ V}$$

$$R_{Th} = 6 \Omega \text{ (Ohm)}$$

$$\text{NODE } V_A : \left[\frac{12 - V_A}{12} - \frac{V_A}{6} + \frac{V_B - V_A}{2} = 0 \right] 12$$

$$12 - V_A - 2V_A + 6V_B - 6V_A = 0$$

$$-9V_A + 6V_B + 12 = 0$$

$$9V_A - 6V_B = 12$$

$$3V_A - 2V_B = 4$$

$$\begin{aligned} 3V_A - 2V_B &= 4 \\ [-V_A + V_B &= 16] 3 \end{aligned}$$

$$V_B = 52 \text{ V} \leftarrow V_{Th}$$


$$\text{NODE } V_B : \left[-\frac{V_B - V_A}{2} + 8 = 0 \right] 2$$

$$-V_B + V_A + 16 = 0$$

$$-V_A + V_B = 16$$

$$\begin{aligned} R_{Th} &= 12 \parallel 6 + 2 \\ &= 4 + 2 = 6 \Omega \end{aligned}$$

④

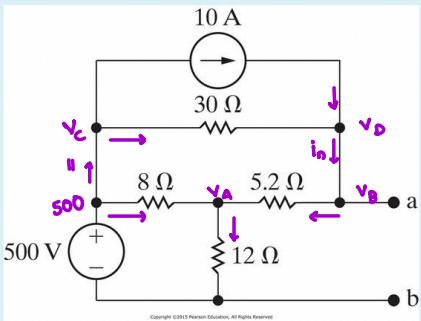

P4.67_10ed

Find the Thévenin equivalent circuit with respect to the terminals a,b for this circuit.

$$V_{Th} = 425 \text{ V}$$

$$R_{Th} = 7.5 \Omega \text{ (Ohm)}$$

$$\begin{aligned} i_n &= 10 + \frac{500 - V_B}{30} \\ V_D &= V_B \end{aligned}$$

$$\begin{aligned} \text{NODE } V_A : \frac{500 - V_A}{8} - \frac{V_A}{12} + \frac{V_B - V_A}{5.2} &= 0 \\ \left[\frac{500 - V_A}{8} - \frac{V_A}{12} + \frac{5(V_B - V_A)}{26} \right] 312 &= 0 \end{aligned}$$

$$\begin{aligned} \text{NODE } V_B : -\frac{V_B - V_A}{5.2} + i_n &= 0 \\ \left[-\frac{V_B - V_A}{26/5} + 10 + \frac{500 - V_B}{30} \right] 780 &= 0 \end{aligned}$$

$$39(500 - V_A) - 26V_A + (12)(5)(V_B - V_A) = 0$$

$$19500 - 39V_A - 26V_A + 60V_B - 60V_A = 0$$

$$[-125V_A + 60V_B + 19500 = 0] / 5$$

$$25V_A - 12V_B = 3900$$

$$-150V_B + 150V_A + 7800 + 13000 - 26V_B = 0$$

$$[150V_A - 176V_B + 20800 = 0] / 2$$

$$75V_A - 88V_B = -10400$$

$$[25V_A - 12V_B = 3900] / 3$$

$$-52V_B = -22100$$

$$V_B = 425 \text{ V}$$

$$\begin{aligned} R_{Th} &= (8 \parallel 12 + 5.2) \parallel 30 \\ &= (4.8 + 5.2) \parallel 30 \\ &= 10 \parallel 30 \\ R_{Th} &= 7.5 \Omega \end{aligned}$$

$$\text{NODE } V_A : \left[\frac{72 - V_A}{5} - \frac{V_A}{20} + \frac{V_{Th} - V_A}{8} = 0 \right] 40$$

$$\begin{aligned} (-3V_A + 5V_{Th} = 144) 5 \\ 15V_A - 5V_{Th} = 576 \end{aligned}$$

$$576 - 8V_A - 2V_A + 5V_{Th} - 5V_A = 0$$

$$15V_A - 5V_{Th} = 576$$

$$20V_{Th} = 1296$$


$$V_{Th} = 64.8 \text{ V}$$

$$\text{NODE } V_{Th} : \left[\frac{72 - V_{Th}}{12} - \frac{V_{Th} - V_A}{8} = 0 \right] 24$$

$$\begin{aligned} R_{Th} &= (5 \parallel 20 + 8) \parallel 12 \\ &= (4 + 8) \parallel 12 \\ &= 12 \parallel 12 \\ R_{Th} &= 6 \Omega \end{aligned}$$

$$144 - 2V_{Th} - 3V_{Th} + 3V_A = 0$$

$$-3V_A + 5V_{Th} = 144$$

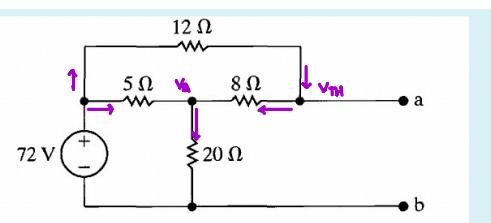


AP4.16_9ed

Find the Thévenin equivalent circuit with respect to the terminals a,b for the circuit shown


$$V_{Th} = 64.8 \text{ V}$$

$$R_{Th} = 6 \Omega \text{ (Ohms)}$$

$$V_S = (15A)(8\Omega) = 120 \text{ V}$$

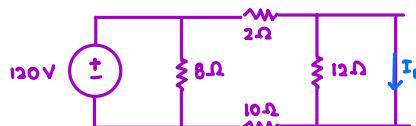

⑥

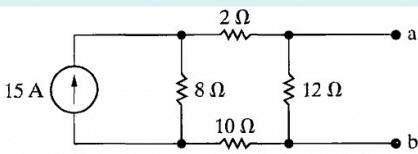

AP4.17_9ed

Find the Norton equivalent circuit with respect to the terminals a,b for the circuit.

$$I_N = 6 \text{ A (current directed toward terminal a)}$$


$$R_N = R_{Th} = 7.5 \Omega \text{ (Ohm)}$$

$$R_{Th} = (2 + 8 + 10) \parallel 12$$

$$= 20 \parallel 12$$

$$= 7.5 \Omega$$

7

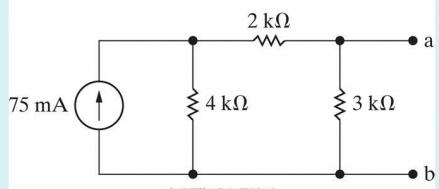


Copyright ©2013 Pearson Education, All Rights Reserved

Find the Norton equivalent circuit with respect to the terminals a,b for this circuit.


$I_N = 50 \text{ mA}$

$R_{Th} = 2000 \Omega$

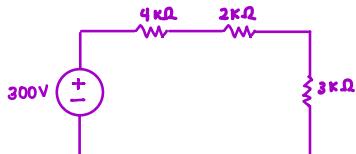
$V_S = (75 \text{ mA})(4 \text{ k}\Omega) = 300 \text{ V}$



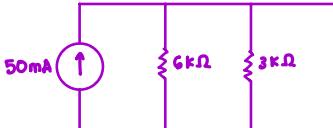$R = 4 + 2 = 6 \text{ k}\Omega$
 $i_S = 300 / 6 \text{ k}\Omega = 50 \text{ mA}$




$R = 6 \parallel 3 = 2 \text{ k}\Omega$

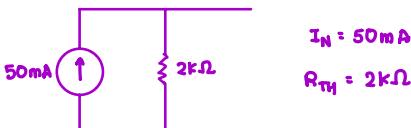


$I_N = 50 \text{ mA}$

$R_{Th} = 2 \text{ k}\Omega$

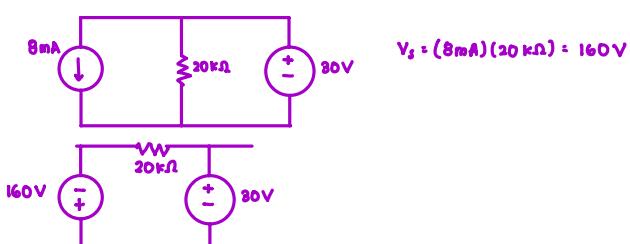

$V_S = (8 \text{ mA})(20 \text{ k}\Omega) = 160 \text{ V}$

8

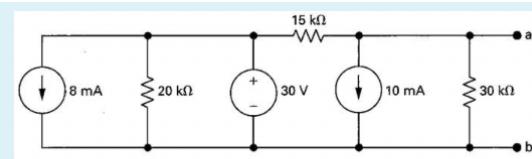


P4.62_6ed

Find the Norton equivalent circuit with respect to the terminals a,b for this circuit. The Norton equivalent current should "point up".

$I_N = -8 \text{ mA}$

$R_{Th} = 10 \text{ k}\Omega$

9

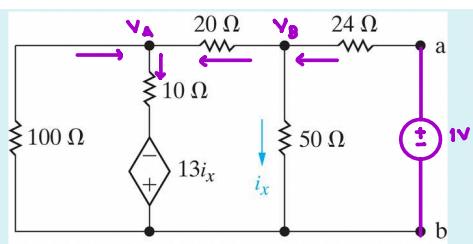

P4.80_10ed

Find the Thévenin equivalent circuit with respect to the terminals a,b for the circuit shown.

Hint: Note that there are no independent sources in this circuit! You will have to provide an excitation to get a response.

$V_{Th} = 0.049 \text{ V}$

$R_{Th} = 40.12 \Omega$

$\text{NODE } V_A: \left[\frac{V_A}{100} - \frac{V_A - 13i_x}{10} - \frac{V_B - V_A}{20} = 0 \right] 100$

$V_A - 10V_A + 130i_x - 5V_B + 5V_A = 0$

$-4V_A - 5V_B + 130i_x = 0 \quad \bullet i_x = \frac{V_B}{50}$

$-4V_A - 5V_B + 130(V_B/50) = 0$

$[-4V_A + 5V_B + 13V_B/5 = 0] 5$

$-20V_A + 38V_B = 0$

$\text{NODE } V_B: \left[\frac{V_B - V_A}{20} - \frac{V_B}{50} + \frac{1 - V_B}{24} = 0 \right] 1200$

$[-20V_A + 38V_B = 0] 67$

$[67V_A - 30V_B = 25] 20$

$1946V_B = 500$


$60V_B - 60V_A - 24V_B + 50 - 50V_B = 0$

$60V_B - 134V_A + 50 = 0$

$67V_A - 30V_B = 25$

$V_B =$

10.

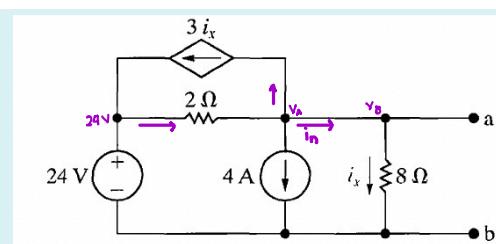

AP4.19_9ed

Find the Thévenin equivalent circuit with respect to the terminals a,b for the circuit shown

$V_{Th} = 8 \text{ V}$

$R_{Th} = 1 \Omega$

$\text{NODE } V_A: \frac{24 - V_A}{2} - 3i_x - 4 - i_n = 0$

$\left[\frac{24 - V_A}{2} - 3\left[\frac{V_B}{8} \right] - 4 - \frac{V_B}{8} = 0 \right] 8$

$96 - 4V_A - 3V_B - 32 - V_B = 0$

$-4V_A - 4V_B + 64 = 0$


$\text{NODE } V_B: i_n = \frac{V_B}{8}$

$i_x = \frac{V_B}{8}$

$8V_A + 8V_B = 64$

$V_A = 8 = V_{Th}$

(11)

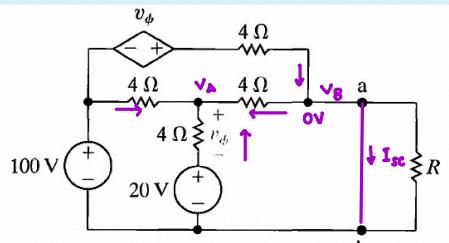

AP4.21_9ed

a) Find the value of R that enable the circuit to deliver maximum power to the terminals a,b

$$R = \boxed{3} \quad \checkmark \quad \Omega \text{ (Ohm)}$$

b) Find the maximum power delivered to R

$$P_R = \boxed{1200} \quad \checkmark \quad \text{W}$$

$$\text{Node } V_A: \frac{V_A - 100}{4} + \frac{V_A - 20}{4} + \frac{V_A - V_B}{4} = 0$$

$$V_A - 100 + V_A - 20 + V_A - V_B = 0$$

$$3V_A - V_B = 120$$

$$(3V_A - V_B = 120) \cdot 2$$

$$(-2V_A + 2V_B = 80) \cdot 3$$

$$4V_B = 480$$

$$V_B = 120 = V_{TH}$$

$$\text{NODE } V_B: \frac{V_B - V_\phi - 100}{4} - \frac{V_A - V_B}{4} = 0$$

$$V_B - V_\phi - 100 - V_A + V_B = 0$$

$$-V_A + 2V_B - V_\phi = 100$$

$$-V_A + 2V_B - (V_A - 20) = 100$$

$$-2V_A + 2V_B = 80$$

WHEN $V_B = 0$:

$$\text{NODE } V_A: \frac{V_A - 100}{4} + \frac{V_A - 20}{4} + \frac{V_A}{4} = 0$$

$$3V_A = 120 \rightarrow V_A = 40$$

$$V_\phi = V_A - 20V = 40V - 20V \\ = 20V$$

$$\text{NODE } V_B: \left[\frac{0 - 100 - V_\phi}{4} + \frac{0 - V_A}{4} + I_{sc} = 0 \right] 4$$



$$-100 - 20 - V_A + 4I_{sc} = 0$$

$$I_{sc} = \frac{100 + 20 + 40}{4} = 40 \text{ A}$$

$$R_{TH} = \frac{V_{TH}}{I_{sc}} = \frac{120 \text{ V}}{40 \text{ A}} = 3 \Omega$$

$$P_{R\max} = I^2 R = \left(\frac{V_{TH}}{R_{TH} + R_L} \right)^2 R_L = \left(\frac{120 \text{ V}}{3\Omega + 3\Omega} \right)^2 (3\Omega) = 1200 \text{ W}$$

(12)

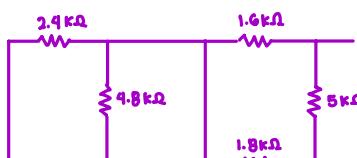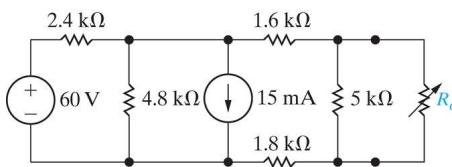

$$60 \text{ V} \quad \begin{matrix} 2.4 \text{ k}\Omega \\ \parallel \\ 4.8 \text{ k}\Omega \end{matrix} \quad i_s = V_s/R = 60/2.4 \text{ k}\Omega = 25 \text{ mA}$$

$$R_{TH} = [(2.4 \parallel 4.8) + 1.6 + 1.8] \parallel 5 \\ = (1.6 + 1.6 + 1.8) \parallel 5 \\ = 5 \parallel 5 = 2.5 \text{ k}\Omega$$

$$25 \text{ mA} \quad \begin{matrix} 2.4 \text{ k}\Omega \\ \parallel \\ 4.8 \text{ k}\Omega \end{matrix} \quad R = 2.4 + 4.8 = 7.2 \text{ k}\Omega$$

$$V_s = i_s R = (25 \text{ mA})(7.2 \text{ k}\Omega) = 180 \text{ V}$$

$$180 \text{ V} \quad \begin{matrix} 1.6 \text{ k}\Omega \\ \parallel \\ 7.2 \text{ k}\Omega \end{matrix} \quad i_n = \frac{180}{7.2 \text{ k}\Omega} - 15 \text{ mA} = 10 \text{ mA}$$

$$10 \text{ mA} \quad \begin{matrix} 1.6 \text{ k}\Omega \\ \parallel \\ 7.2 \text{ k}\Omega \end{matrix} \quad V_s = (10 \text{ mA})(7.2 \text{ k}\Omega) = 72 \text{ V}$$

$$V_s = (10 \text{ mA})(7.2 \text{ k}\Omega) = 72 \text{ V}$$

$$25 \text{ mA} \quad \begin{matrix} 1.6 \text{ k}\Omega \\ \parallel \\ 7.2 \text{ k}\Omega \end{matrix} \quad 15 \text{ mA} \quad \begin{matrix} 1.6 \text{ k}\Omega \\ \parallel \\ 7.2 \text{ k}\Omega \end{matrix} \quad 15.6$$