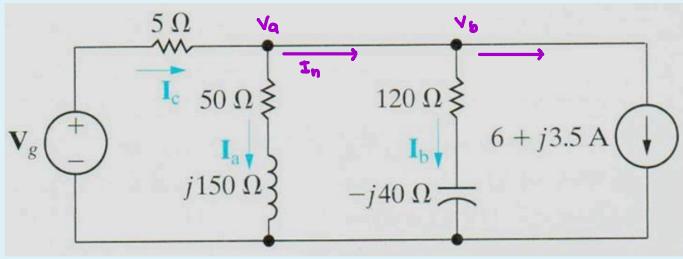


①



P9.40_7ed

Given the phasor current $I_a = 2$ at angle 0° A (magnitude 2 with angle 0 degrees Amps).

Find the following phasor values:

$$I_b = \text{Magnitude } 2.5 \quad \checkmark \quad \text{with Angle } 90^\circ \quad \checkmark \quad (\text{Degrees}) \quad \text{Amps}$$

$$I_c = \text{Magnitude } 10 \quad \checkmark \quad \text{with Angle } 36.87^\circ \quad \checkmark \quad (\text{Degrees}) \quad \text{Amps}$$

$$V_g = \text{Magnitude } 358.47 \quad \checkmark \quad \text{with Angle } 67.01^\circ \quad \checkmark \quad (\text{Degrees}) \quad \text{Volts}$$

$$I_a = 2 < 0^\circ \text{ A} \approx 2 + j0$$

$$V_q = I_a (50 + j150) \quad V_b = V_q = 100 + j300$$

$$= 2 (50 + j150)$$

$$= 100 + j300$$

$$(a) V_b = I_b (120 - j40)$$

$$I_b = \frac{100 + j300}{120 - j40} + \frac{j120 + j40}{120 + j40} = \frac{12k + j40k - 12k}{14.4k + 1.6k}$$

$$= \frac{j40k}{16k} = j2.5 \approx 2.5 < 90^\circ \text{ A}$$

$$(b) I_n = I_b + (6 + j3.5)$$

$$I_c = I_a + I_n = I_a + I_b + (6 + j3.5)$$

$$= (2 + j0) + (j2.5) + (6 + j3.5)$$


$$I_c = 8 + j6 \approx 10 < 36.87^\circ$$

$$(c) I_c = \frac{V_g - V_q}{5} \rightarrow V_g = 5I_c + V_q$$

$$V_g = 5(8 + j6) + (100 + j300)$$

$$= 140 + j330 \approx 358.47 < 67.01^\circ$$

②

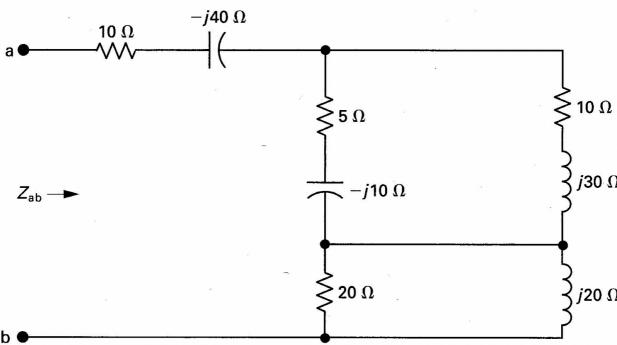


P9.23_6ed

Find the impedance Z_{ab} in this circuit.


$$Z_{ab} = 30 + j -40 \quad \checkmark \quad \Omega \text{ (Ohms)} \text{ in rectangular form}$$
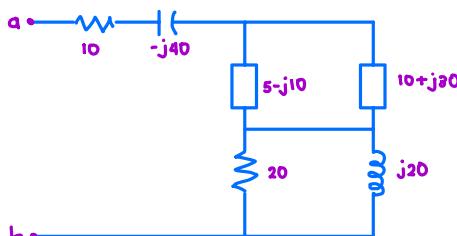
$$Z_{ab} = \text{Mag } 50 \quad \checkmark \quad \text{and Angle } -53.13^\circ \quad \checkmark \quad (\text{Degrees}) \Omega \text{ (Ohms)} \text{ in polar form}$$



$$5 - j10 // 10 + j30 = \frac{(5 - j10)(10 + j30)}{(5 - j10) + (10 + j30)} = \frac{50 + j50 + 300}{15 + j20} = \frac{350 + j50}{15 + j20} \cdot \frac{15 - j20}{15 - j20} = \frac{5250 - j6250 + 1000}{225 + 400} = \frac{6250 - j6250}{625} = 10 - j10$$
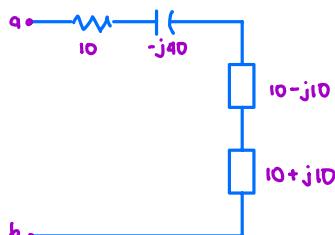
$$20 // j20 = \frac{(20)(j20)}{20 + j20} = \frac{j400}{20 + j20} \cdot \frac{20 - j20}{20 - j20} = \frac{j8000 + 8000}{400 + 400} = 10 + j10$$




$$Z_{ab} = 10 - j40 + (10 - j10) + (10 + j10)$$

$$\Rightarrow 30 - j40$$

$$\text{polar form: } Z_{ab} = 50 < -53.13^\circ$$


(3)

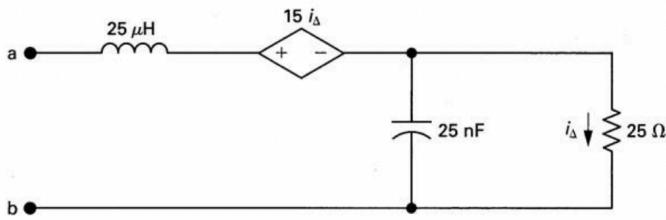

P9.18_6ed

Given: ω (omega) = 1.6×10^6 rad/sec

Find the circuits impedance at the terminals ab.

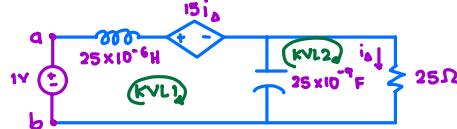 Z_{ab} = Magnitude ✓ with Angle ✓ ° (Degrees) Ω (Ohm)

$$\omega = 1.6 \times 10^6 \text{ rad/s}$$

$$Z_L = j\omega L = j(1.6 \times 10^6)(25 \times 10^{-6})$$

$$= j40$$

$$Z_C = -\frac{j}{\omega C} = -\frac{-j}{(1.6 \times 10^6)(25 \times 10^{-9})} = -j25$$

$$V = ZI$$

$$\begin{aligned} \text{KVL1: } & -1 + j40I_1 + 15I_\Delta - j25(I_1 - I_2) = 0 & I_\Delta = I_2 \\ & -1 + j40I_1 + 15I_2 - j25I_1 + j25I_2 = 0 \\ & [j15I_1 + (15+j25)I_2 = 1] \sqrt{5} \\ & j3I_1 + (3+j5)I_2 = \sqrt{5} \end{aligned}$$

$$\begin{aligned} \text{KVL2: } & -(-j25)(I_1 - I_2) + 25I_2 = 0 \\ & j25I_1 - j25I_2 + 25I_2 = 0 \\ & 25[jI_1 + (1-j)I_2] = 0 \\ & jI_1 + (1-j)I_2 = 0 \end{aligned}$$

$$[jI_1 + (1-j)I_2 = 0] 3$$

$$(-j3I_1 + (3+j5)I_2 = \sqrt{5})$$

$$-8jI_2 = -1/\sqrt{5}$$

$$I_2 = \frac{1}{j40}$$


$$I_1 = -\frac{(1-j)(1/j40)}{j} = \frac{1-j}{40} = 0.025 - j0.025$$

$$Z_{ab} = \frac{V}{I_1} = \frac{1}{0.025 - j0.025} = \frac{0.025 + j0.025}{\frac{1}{1600} + \frac{1}{1600}} \approx 20 + j20$$

$$Z_{ab} = 20\sqrt{2} < 45^\circ$$

$$\approx 28.28 < 45^\circ$$

(4)

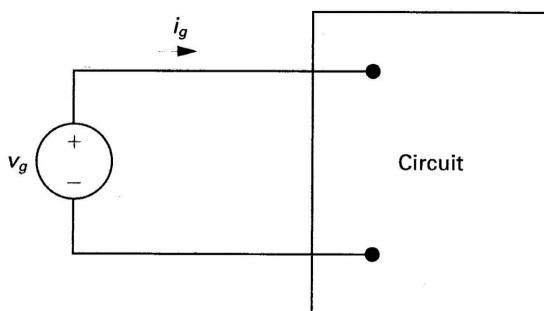

P9.29_6ed

Given:

$$V_g = 150 \cos(8000\pi t + 20^\circ) \text{ V}$$

$$i_g = 30 \sin(8000\pi t + 38^\circ) \text{ A}$$

a) What is the impedance seen by the source?

 $Z_{circuit} = \text{Mag } 5 \text{ with Angle } 72 \text{ }^\circ \text{ (Degrees) } \Omega \text{ (Ohm)}$

b) By how many microseconds is the current out of phase with the voltage?

 $t_{phase} = 50 \text{ } \mu\text{s (micro sec)}$

$$(a) V_g = 150 \cos(8000\pi t + 20^\circ) \text{ V}$$

$$V = 150 < 20^\circ$$

$$i_g = 30 \sin(8000\pi t + 38^\circ) \text{ A}$$

$$I = 30 < -52^\circ$$

$$= 30 \cos[90 - (8000\pi t + 38^\circ)]$$

$$V = ZI$$


$$= 30 \cos(-8000\pi t + 52^\circ)$$

$$Z = \frac{V}{I} = \frac{150 < 20^\circ}{30 < -52^\circ} = 5 < 92^\circ$$

$$(b) \omega = 8000\pi \quad T = \frac{2\pi}{\omega} = \frac{2\pi}{8000\pi} = 2.5 \times 10^{-4} \text{ s}$$

$$\frac{2.5 \times 10^{-4} \text{ s}}{t} \rightarrow 360^\circ \quad \frac{t}{72^\circ} \rightarrow 360^\circ$$
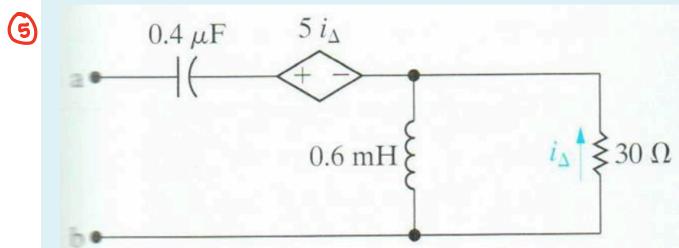
$$t = 5 \times 10^{-5} \text{ s} \approx 50 \text{ } \mu\text{s}$$




P9.29_7ed

Find the Thévenin impedance seen looking into the terminals ab of this circuit.

The frequency of operation is 100 krad/sec (kilo rad/sec).
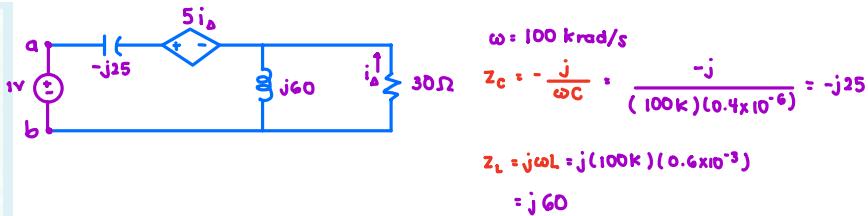
$$Z_{Th} = \boxed{20 \quad \checkmark \quad +j \quad -15 \quad \checkmark \quad \Omega \text{ (Ohm)}}$$



CURRENT DIVISION RULE:

$$I_2 = \frac{R_1}{R_1 + R_2} I \quad I_A = -I_2$$

$$I_A = -\frac{j60}{j60 + 30} I = \frac{-j1800 - 3600}{4500} I = -(0.8 + j0.4)I$$

$$V = ZI$$

$$\text{KVL: } -1 - j25I + 5I_\Delta + (j60 \parallel 30)I = 0 \\ -1 - j25I - 5(0.8 + j0.4)I + (24 + j12)I = 0$$

$$(20 - j15)I = 1$$


$$I = \frac{1}{20 - j15} = \frac{20 + j15}{625} = \frac{4 + j3}{125}$$

$$Z_{Th} = \frac{V}{I} = \frac{1}{\frac{4 + j3}{125}} = \frac{125}{4 + j3} \cdot \frac{4 - j3}{4 - j3} = \frac{500 - j875}{25} = \boxed{20 - j15}$$

$$j60 \parallel 30 = \frac{(j60)(30)}{j60 + 30}$$

$$= \frac{j1800}{30 + j60} \cdot \frac{30 - j60}{30 - j60}$$
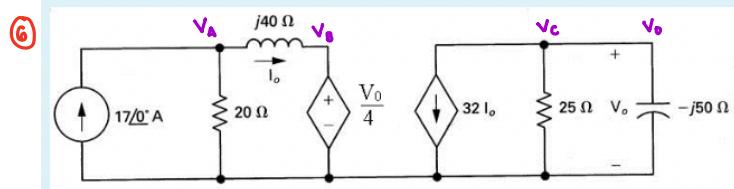
$$= \frac{j54k + 108k}{4.5k} = 24 + j12$$



P9.56_6ed

Use the node-voltage method to find the follow phasor values.

$$V_0 = \boxed{1280 \quad \checkmark \quad +j \quad 320 \quad \checkmark \quad \text{Volts}}$$

$$I_0 = \boxed{-1.4 \quad \checkmark \quad +j \quad -1.2 \quad \checkmark \quad \text{Amps}}$$

$$\text{NODE } V_A: \left[\frac{V_A}{20} + \frac{V_A - V_B}{j40} = 17 \right] j40$$

$$j2V_A + V_A - V_B = j680$$

$$(1+j2)V_A - V_B = j680$$

$$\left[(1+j2)V_A - \frac{V_0}{4} = j680 \right] 4$$

$$(4+j8)V_A - V_0 = j2720$$

$$\text{NODE } V_C: \left[32I_0 + \frac{V_C}{25} - \frac{V_C}{j50} = 0 \right] j50$$

$$j1600I_0 + j2V_C - V_C = 0$$

$$j1600I_0 + (-1+j2)V_C = 0$$

$$j1600 \left[\frac{V_A - V_B}{j40} \right] + (-1+j2)V_C = 0$$

$$40V_A - 40V_B + (-1+j2)V_C = 0$$

$$40V_A - 40 \left(\frac{V_0}{4} \right) + (-1+j2)V_C = 0$$

$$40V_A - 10V_0 + (-1+j2)V_C = 0$$

$$V_A = \frac{11-j2}{40} V_0$$

$$= \left(\frac{11}{40} - j0.05 \right) (1280 + j320)$$

$$= 352 + j24 + 16 = 368 + j24$$


$$I_0 = \frac{V_A - V_B}{j40} = \frac{\frac{11-j2}{40} V_0 - \frac{V_0}{4}}{j40} = \frac{(11-j2)V_0 - 10V_0}{j40 \cdot 40} = \frac{1-j2}{j40 \cdot 40} V_0$$

$$I_0 = \left(\frac{1}{j40 \cdot 40} - \frac{1}{20 \cdot 40} \right) V_0$$

$$= (-1.25 \times 10^{-3} - j6.25 \times 10^{-4}) (1280 + j320)$$

$$= -1.6 - j1.2 + 0.2 = -1.4 - j1.2$$

⑦

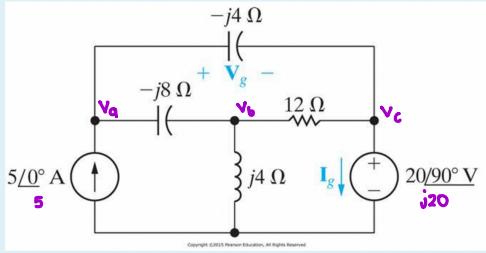

P9.55_10ed

Use the node-voltage method to find V_g .

$$V_g = -2.665 \quad + j \quad -18.668 \quad \text{Volts}$$

$$\begin{aligned} V_g &= V_a - V_c = -\frac{8}{3} + j\frac{4}{3} - j20 \\ &= -\frac{8}{3} - j\frac{56}{3} \approx -2.67 - j18.67 \end{aligned}$$

$$\text{NODE } V_a: \left[\frac{V_a - V_c}{-j4} + \frac{V_a - V_b}{-j8} = 5 \right] -j8$$

$$2V_a - 2V_c + V_a - V_b = -j40$$

$$3V_a - 2(j20) - V_b = -j40$$

$$3V_a - V_b = 0$$

$$V_b = 3V_a$$

$$\text{NODE } V_b: \left[\frac{V_b - V_a}{-j8} + \frac{V_b}{j4} + \frac{V_b - V_c}{12} = 0 \right] j24$$

$$-3V_b + 3V_a + 6V_b + j2V_b - j2V_c = 0$$

$$3V_a + (3+j2)V_b = j2(j20)$$


$$3V_a + (3+j2)V_b = -40$$

$$3V_a + (3+j2)(2V_a) = -40$$

$$[(12+j6)V_a = -40] \frac{1}{2}$$

$$V_a = \frac{-20}{6+j3} \cdot \frac{6-j3}{6+j3} = \frac{-120+j60}{45} = -\frac{8}{3} + j\frac{4}{3}$$

⑧

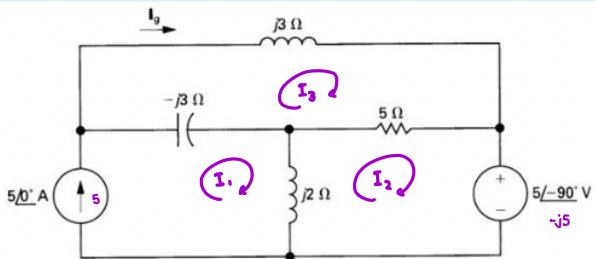

P9.45_6ed

Use the mesh-current method to find I_g .

$$I_g = 0 \quad + j \quad -3 \quad \text{A}$$

$$I_1 = 5 \text{ A}$$

$$I_2: -j2(I_2 - I_1) - 5(I_2 - I_3) + j5 = 0$$

$$-j2I_2 + j2(5) - 5I_2 + 5I_3 + j5 = 0$$

$$(-5-j2)I_2 + 5I_3 = -j15$$

$$I_3: -j3I_3 - 5(I_3 - I_2) + j3(I_3 - I_1) = 0$$

$$-j2I_3 - 5I_3 + 5I_2 + j3I_3 - j3(5) = 0$$

$$5I_2 - 5I_3 = j15$$

$$5I_2 - 5I_3 = j15$$

$$(+) (-5-j2)I_2 + 5I_3 = -j15$$


$$-j2I_2 + 0 = 0$$

$$I_2 = 0$$

$$I_3 = (-j15 + 5I_2) \frac{1}{5} = -j3 + 0 = -j3$$

$$I_g = I_3 = -j3 \text{ A}$$

⑨

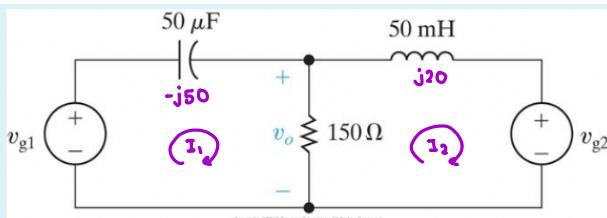

P9.61_10ed

Given: $v_{g1} = 25 \sin(400t + 143.12^\circ) \text{ V}$ and $v_{g2} = 18.03 \cos(400t + 33.69^\circ) \text{ V}$ Use the mesh-current method to find the steady-state voltage of $v_0(t)$.

$$v_0(t) = 15 \quad + \cos(400t + 0.005) \quad \text{Degrees} \text{ V}$$

$$\begin{aligned} I_1: -v_{g1} - j50I_1 + 150(I_1 - I_2) &= 0 \\ -(15+j20) - j50I_1 + 150I_1 - 150I_2 &= 0 \\ (150-j50)I_1 - 150I_2 &= 15+j20 \end{aligned}$$

$$\begin{aligned} I_2: 150(I_2 - I_1) + j20I_2 + v_{g1} &= 0 \\ 150I_2 - 150I_1 + j20I_2 &= -(15+j20) \\ -150I_1 + (150+j20)I_2 &= -15-j10 \end{aligned}$$

$$v_{g1} = 25 \sin(400t + 143.12^\circ) \text{ V}$$

$$= 25 \cos(400t + 53.12^\circ) \text{ V}$$

$$= 25 \angle 53.12^\circ \approx 15 + j20$$

$$v_{g2} = 18.03 \cos(400t + 33.69^\circ) \text{ V}$$

$$= 18.03 \angle 33.69^\circ \approx 15 + j10$$

$$Z_L = j\omega L = j(400)(50 \times 10^{-3})$$

$$= j20$$

$$Z_C = \frac{-j}{\omega C} = \frac{-j}{(400)(50 \times 10^{-6})} = -j50$$

$$\begin{aligned} (150-j50)I_1 - 150I_2 &= 15+j20 \\ -150I_1 + (150+j20)I_2 &= -15-j10 \end{aligned} \quad \left. \begin{aligned} I_1 &= -0.4 \\ I_2 &= -0.5 \end{aligned} \right.$$


$$V_0 = 150(I_1 - I_2)$$

$$= 150(-0.4 + 0.5)$$

$$= 15 + j0$$

$$\approx 15 \angle 0^\circ$$

10.

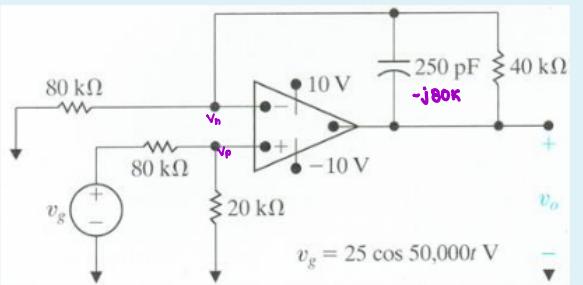

P9.81_7ed


The operational amplifier is ideal.

Given $v_g(t) = 25 \cos(50,000t)$ Va) Find the steady-state output $v_o(t)$.

$$v_o(t) = 7.07 \quad \checkmark \quad \cos(50,000t + -8.13 \quad \checkmark \quad ^\circ) \text{ (Degrees) Volts}$$

b) How large can the amplitude of $v_g(t)$ be before the amplifier saturates?

$$|v_o(t)_{\max}| \leq 35.35 \quad \checkmark \text{ Volts}$$

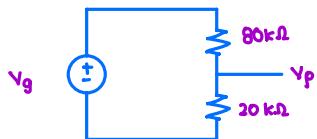

VOLTAGE DIVISION:

$$v_p = \frac{v_g(20k)}{20k + 80k}$$

$$\approx 0.2v_g = 5V = v_n$$

$$Z_C = \frac{-j}{\omega C} = \frac{-j}{(50k)(250 \times 10^{-12})} = -j80k$$

$$\begin{aligned} -j80k // 40k &= \frac{(-j80k)(40k)}{-j80k + 40k} = \frac{-j3200k^2}{40k(1-j2)} = \frac{-j80k}{1-j2} \cdot \frac{1+j2}{1+j2} \\ &= \frac{-j80k + 160k}{5} = 32k - j16k \end{aligned}$$

$$(a) \text{ NODE } V_n: \frac{V_n}{80k} + \frac{V_n - V_o}{32k - j16k} = 0$$

$$\frac{5}{80k} + \frac{5 - V_o}{32k - j16k} = 0$$

$$5 - V_o = -\frac{5}{80k} (32k - j16k)$$

$$V_o = \frac{j16k(2-j1)}{16k} + 5 = 2-j1 + 5 = 7-j1$$

$$V_o = 7 \angle -8.13^\circ$$

$$(b) |v_o(t)| \leq 10V$$

$$|(0.28 - j0.04)v_g| \leq 10$$

$$|\sqrt{2}/2 v_g| \leq 10$$

$$v_g \leq 25\sqrt{2} \approx 35.35$$

$$\frac{V_n}{80k} + \frac{V_n - V_o}{32k - j16k} = 0$$

$$\frac{0.2V_g}{80k} + \frac{0.2V_g - V_o}{32k - j16k} = 0$$

$$\left(\frac{1}{80k} + \frac{1}{32k - j16k} \right) 0.2V_g = \frac{V_o}{32k - j16k}$$

$$\frac{0.2}{16k} \left[\frac{1}{5} + \frac{1}{2-j1} \right] V_g = \frac{V_o}{16k(2-j1)}$$

$$0.2 \left[\frac{5+2-j1}{5(2-j1)} \right] V_g = \frac{V_o}{2-j1}$$

$$\frac{(0.2)(7-j1)(2-j1)}{5(2-j1)^2} V_g = V_o$$

$$0.04(7-j1)V_g = V_o$$

$$0.28 - j0.04V_g = V_o$$