

Solution Homework-06 ENGR 117

5 Questions 20 points each


Q-1 Design an op amp-based low-pass filter with a cutoff frequency of 2500 Hz and a passband gain of 5 using a 10 nF capacitor. The input to the low-pass filter is $3.5 \cos \omega t$ V.

- a) Draw your circuit, labeling the component values and output voltage.
- b) If the value of the feedback resistor in the filter is changed but the value of the resistor in the forward path is unchanged, what characteristic of the filter is changed?
- c) Find the output voltage when $\omega = \omega_c$.
- d) Find the output voltage when $\omega = 0.125 \omega_c$.
- e) Find the output voltage when $\omega = 8 \omega_c$.

Note: $v_i = 3.5 \angle 0$ $\implies V_i(j\omega) = 3.5 \angle 0$

$$[a] \quad \omega_c = \frac{1}{R_2 C} \quad \text{so} \quad R_2 = \frac{1}{\omega_c C} = \frac{1}{2\pi(2500)(10 \times 10^{-9})} = 6366 \, \Omega$$
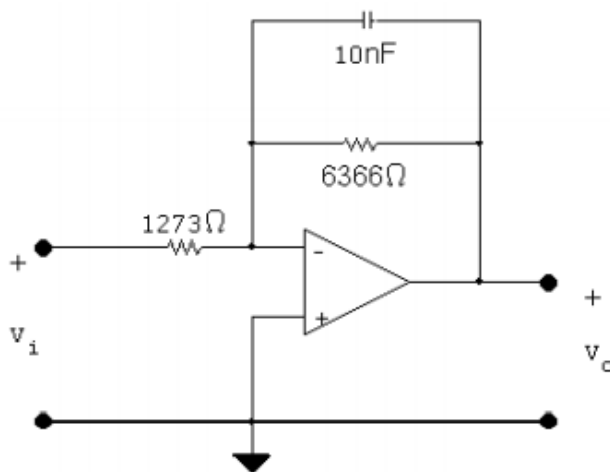
$$K = \frac{R_2}{R_1} \quad \text{so} \quad R_1 = \frac{R_2}{K} = \frac{6366}{5} = 1273 \, \Omega$$



[b] Both the cutoff frequency and the passband gain are changed.

$$[c] \quad H(j\omega) = \frac{-5(2\pi)(2500)}{j\omega + 2\pi(2500)}$$

$$H(j5000\pi) = \frac{-5(5000\pi)}{5000\pi + j5000\pi} = \frac{5}{\sqrt{2}} \angle 135^\circ = \frac{Vo}{Vi}$$

$$Vo = \frac{17.5}{\sqrt{2}} \angle 135^\circ \quad \text{so} \quad v_o(t) = 12.37 \cos(5000\pi t + 135^\circ) \text{ V}$$

$$[d] \quad H(j625\pi) = \frac{-5(5000\pi)}{5000\pi + j625\pi} = 4.96 \angle 172.9^\circ = \frac{Vo}{Vi}$$

$$Vo = 17.36 \angle 172.9^\circ \quad \text{so} \quad v_o(t) = 17.36 \cos(625\pi t + 172.9^\circ) \text{ V}$$

$$[e] \quad H(j40,000\pi) = \frac{-5(5000\pi)}{5000\pi + j40,000\pi} = 0.62 \angle 97.1^\circ = \frac{Vo}{Vi}$$

$$Vo = 2.2 \angle 97.1^\circ \quad \text{so} \quad v_o(t) = 2.2 \cos(40,000\pi t + 97.1^\circ) \text{ V}$$

Q-2 Write the relationship and draw phasor between phase and line quantities for a balanced 3 phase system if:

- Star Connection (phasor diagram for phase voltages and Line voltages).
- Delta Connection (phasor diagram for phase currents and Line currents).


[a] **STAR: (Positive sequence)**

I(phase) = I(Line) It means:

$$\begin{aligned} I_{an} &= I_{\phi} \angle 0 & I_a &= I_{\phi} \angle 0 \\ I_{bn} &= I_{\phi} \angle -120 & I_b &= I_{\phi} \angle -120 \\ I_{cn} &= I_{\phi} \angle +120 & I_c &= I_{\phi} \angle +120 \end{aligned}$$

V(Line) = ($\sqrt{3} \angle +30^\circ$) V(phase) It means:


$$\begin{aligned} V_{an} &= V_{\phi} \angle 0^\circ & \text{then} & & V_{ab} &= (\sqrt{3} \angle +30^\circ) (V_{\phi} \angle 0) = \sqrt{3} V_{\phi} \angle 30^\circ \\ V_{bn} &= V_{\phi} \angle -120^\circ & \text{then} & & V_{bc} &= (\sqrt{3} \angle +30^\circ) (V_{\phi} \angle -120) = \sqrt{3} V_{\phi} \angle -90^\circ \\ V_{cn} &= V_{\phi} \angle +120^\circ & \text{then} & & V_{ca} &= (\sqrt{3} \angle +30^\circ) (V_{\phi} \angle +120) = \sqrt{3} V_{\phi} \angle 150^\circ \end{aligned}$$

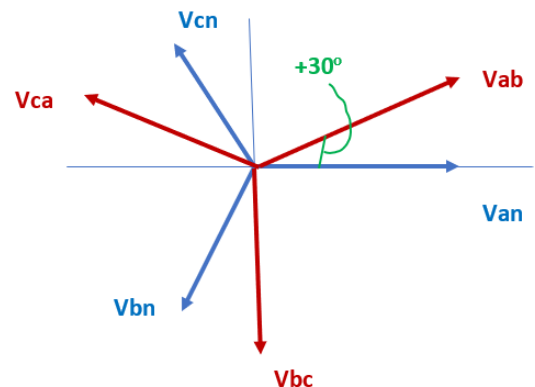

[b] **DELTA: (Positive sequence)**

V(phase) = V(Line) It means:
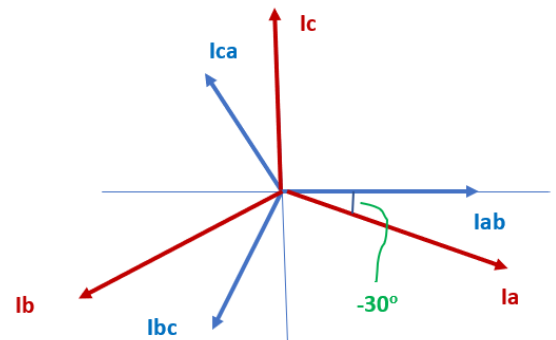
$$\begin{aligned} V_{ab} &= V_{\phi} \angle 0 & V_{ab} &= I_{\phi} \angle 0 \\ V_{bc} &= V_{\phi} \angle -120 & V_{bc} &= V_{\phi} \angle -120 \\ V_{ca} &= V_{\phi} \angle +120 & V_{ca} &= V_{\phi} \angle +120 \end{aligned}$$



I(Line) = ($\sqrt{3} \angle -30^\circ$) I(phase) It means:

$$\begin{aligned} I_{ab} &= I_{\phi} \angle 0^\circ & \text{then} & & I_a &= (\sqrt{3} \angle -30^\circ) (I_{\phi} \angle 0) = \sqrt{3} I_{\phi} \angle -30^\circ \\ I_{bc} &= I_{\phi} \angle -120^\circ & \text{then} & & I_b &= (\sqrt{3} \angle -30^\circ) (I_{\phi} \angle -120) = \sqrt{3} I_{\phi} \angle -150^\circ \\ I_{ca} &= I_{\phi} \angle +120^\circ & \text{then} & & I_c &= (\sqrt{3} \angle -30^\circ) (I_{\phi} \angle +120) = \sqrt{3} I_{\phi} \angle 90^\circ \end{aligned}$$

Q-3 For each set of voltages, state whether or not the voltages form a balanced three-phase set. If the set is balanced, state whether the phase sequence is positive or negative. If the set is not balanced, explain why?

a) $v_a = 48 \cos(314t - 45^\circ) \text{ V},$
 $v_b = 48 \cos(314t - 165^\circ) \text{ V},$
 $v_c = 48 \cos(314t + 75^\circ) \text{ V}.$

b) $v_a = 188 \cos(250t + 60^\circ) \text{ V},$
 $v_b = -188 \cos 250t \text{ V},$
 $v_c = 188 \cos(250t - 60^\circ) \text{ V}.$

c) $v_a = 426 \cos 100t \text{ V},$
 $v_b = 462 \cos(100t + 120^\circ) \text{ V},$
 $v_c = 426 \cos(100t - 120^\circ) \text{ V}.$

d) $v_a = 1121 \cos(2000t - 20^\circ) \text{ V},$
 $v_b = 1121 \sin(2000t - 50^\circ) \text{ V},$
 $v_c = 1121 \cos(2000t + 100^\circ) \text{ V}.$

e) $v_a = 540 \sin 630t \text{ V},$
 $v_b = 540 \cos(630t - 120^\circ) \text{ V},$
 $v_c = 540 \cos(630t + 120^\circ) \text{ V}.$

f) $v_a = 144 \cos(800t + 80^\circ) \text{ V},$
 $v_b = 144 \sin(800t - 70^\circ) \text{ V},$
 $v_c = 144 \sin(800t + 50^\circ) \text{ V}.$

[a] $V_a = 48/\underline{-45^\circ} \text{ V}$

$$V_b = 48/\underline{-165^\circ} \text{ V}$$

$$V_c = 48/\underline{75^\circ} \text{ V}$$

Balanced, positive phase sequence

[b] $V_a = 188/\underline{60^\circ} \text{ V}$

$$V_b = -188/\underline{0^\circ} \text{ V} = 188/\underline{180^\circ} \text{ V}$$

$$V_c = 188/\underline{-60^\circ} \text{ V}$$

Balanced, negative phase sequence

[c] $V_a = 426/\underline{0^\circ} \text{ V}$

$$V_b = 462/\underline{120^\circ} \text{ V}$$

$$V_c = 426/\underline{-120^\circ} \text{ V}$$

Unbalanced due to unequal amplitudes

[d] $V_a = 1121/\underline{-20^\circ} \text{ V}$

$$V_b = 1121/\underline{-140^\circ} \text{ V}$$

$$V_c = 1121/\underline{100^\circ} \text{ V}$$

Balanced, positive phase sequence

[e] $V_a = 540/\underline{-90^\circ} \text{ V}$

$$V_b = 540/\underline{-120^\circ} \text{ V}$$

$$V_c = 540/\underline{120^\circ} \text{ V}$$

Unbalanced due to unequal phase separation

[f] $V_a = 144/\underline{80^\circ} \text{ V}$

$$V_b = 144/\underline{-160^\circ} \text{ V}$$

$$V_c = 144/\underline{-40^\circ} \text{ V}$$

Balanced, negative phase sequence


Q-4 A balanced three-phase circuit has the following characteristics.

- Y-Y connected;
- The line voltage at the source, V_{ab} , is $110\sqrt{3} \angle -60^\circ$ V;
- The phase sequence is positive;
- The line impedance is $3 + j2 \Omega/\phi$;
- The load impedance is $37 + j28 \Omega/\phi$;

- Draw the single-phase equivalent circuit for the a-phase.
- Calculated the line currents for each phase.
- Calculated the line voltages at the load in each phase.

[a] $V_{an} = 1/\sqrt{3} \angle -30^\circ V_{ab} = 110 \angle -90^\circ$ V

The a-phase circuit is

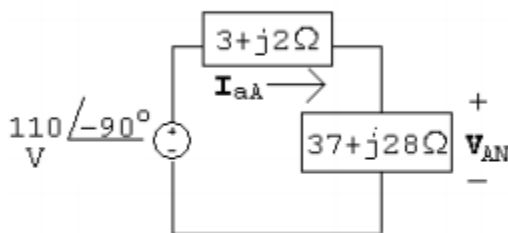

[b] $I_{aA} = \frac{110 \angle -90^\circ}{40 + j30} = 2.2 \angle -126.87^\circ$ A

[c] $V_{AN} = (37 + j28)I_{aA} = 102.08 \angle -89.75^\circ$ V

$V_{AB} = \sqrt{3} \angle 30^\circ V_{AN} = 176.81 \angle -59.75^\circ$ V

$I_{bB} = 2.2 \angle -246.87^\circ$ A

$I_{cC} = 2.2 \angle -6.87^\circ$ A

$V_{BC} = 176.81 \angle -179.75^\circ$ V

$V_{CA} = 176.81 \angle +60.25^\circ$ V

Q-5 A balanced, three-phase circuit is characterized as follows:


- Y- Δ connected;
- Source voltage in the b-phase is $150/\underline{135^\circ}$ V;
- Source phase sequence is acb;
- Line impedance is $2 + j3 \Omega/\phi$;
- Load impedance is $129 + j171 \Omega/\phi$.

- Draw the single phase equivalent for the a-phase.
- Calculate the a-phase line current.
- Calculate the a-phase line voltage for the three-phase load.

$$[a] \ V_{an} = V_{bn} - 1/\underline{120^\circ} = 150/\underline{15^\circ} \text{ V}$$

$$Z_y = Z_{\Delta}/3 = 43 + j57 \Omega$$

The a-phase circuit is

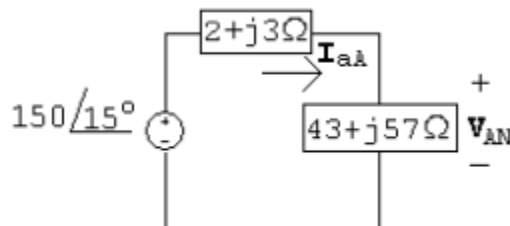

$$[b] \ I_{aA} = \frac{150/\underline{15^\circ}}{45 + j60} = 2/\underline{-38.13^\circ} \text{ A}$$

$$[c] \ V_{AN} = (43 + j57)I_{aA} = 142.8/\underline{14.84^\circ} \text{ V}$$

$$V_{AB} = \sqrt{3}/\underline{-30^\circ} V_{AN} = 247.34/\underline{-15.16^\circ} \text{ V}$$

$$V_{BC} = 247.34 \angle +104.84^\circ \text{ V}$$

$$V_{CA} = 247.34 \angle -135.16^\circ \text{ V}$$