


## Homework-02      ENGR 117      Due date 02/21/2022

5 Questions    20 points each

- Q-1** Find the average power delivered by the ideal current source in the circuit

$$i_g = 8 \cos 5000t \text{ A}$$


Here 8 is max value

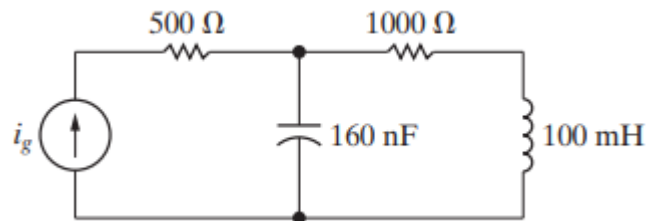

- Q-2** Find the average power dissipated in the  $60 \Omega$  resistor in the circuit

$$i_g = 6 \cos 20,000t \text{ A.}$$


Here 6 is max value

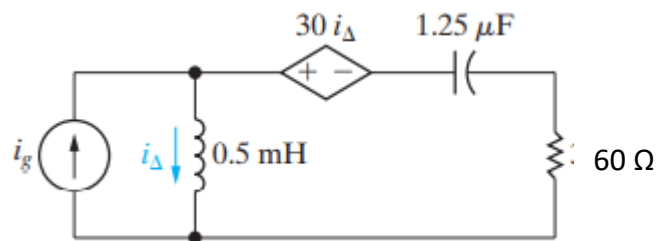

- Q-3** Find the average power, the reactive power, and the apparent power supplied by the voltage source in the circuit

$$v_g = 40 \cos 10^6 t \text{ V.}$$

Here 40 is max value

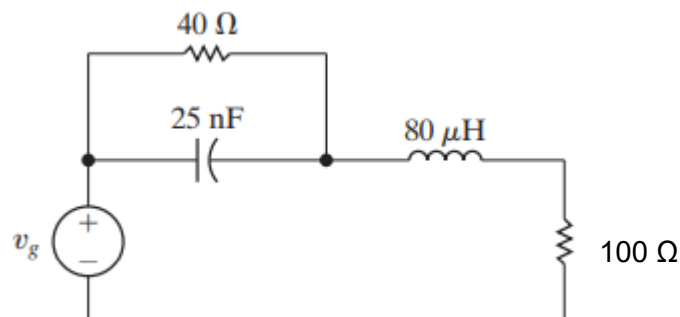

**Q- 4** A single-phase source is applied to a two-terminal, passive circuit with equivalent impedance  $Z = 2.0 \angle -45^\circ \Omega$  measured from the terminals. The source current is  $i(t) = 4\sqrt{2} \cos(\omega t)$  kA. Determine the (a) instantaneous power, (b) real power, and (c) reactive power delivered by the source. (d) Also determine the source power factor.

Here current is max value representation.

**Q-5** The real power delivered by a source to two impedances,  $Z_1 = 3 + j4 \Omega$  and  $Z_2 = 10 \Omega$ , connected in parallel, is 1100 W. Determine (a) the real power absorbed by each of the impedances and (b) the source current.

Here V is RMS value representation

Q1.

$$Z_L = j\omega L = j(5000)(100 \times 10^{-3}) = j500 \Omega$$

$$Z_C = \frac{-j}{\omega C} = \frac{-j}{(5000)(160 \times 10^{-9})} = -j1250 \Omega$$

$$R_{eq1} = 1000 + j500$$

$$\frac{1}{R_{eq2}} = \frac{1}{1000 + j500} + \frac{1}{-j1250}$$

$$R_{eq2} = 1000 - j500$$

$$Z = 500 + R_{eq2}$$

$$= 500 + (1000 - j500)$$

$$= 1500 - j500$$


$$= 1581.13 \angle -18.43^\circ$$

$$V = IZ = (8 \angle 0^\circ)(1581.13 \angle -18.43^\circ)$$

$$= 12649.04 \angle -18.43^\circ$$

$$i_g = 8 \cos 5000t \text{ A}$$

Here 8 is max value

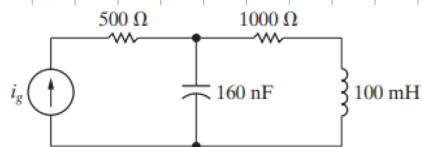

$$6324.52 \angle -18.43^\circ$$

$$P_{avg} = \frac{V_m I_m}{2} \cos(\theta_v - \theta_i) = \frac{(12649.04)(8)}{2} \cos(-18.43 - 0) = 48001.11 \text{ W} \approx 48 \text{ kW}$$

Q2

$$Z_L = j\omega L = j(20000)(0.5 \times 10^{-3}) = j10 \Omega$$

$$Z_C = \frac{-j}{\omega C} = \frac{-j}{(20000)(1.25 \times 10^{-6})} = -j40 \Omega$$


$$i_g = 6 \angle 0^\circ \approx 6 \text{ A}$$

$$R_{eq1} = -j40 \Omega + 60 \Omega = 60 - j40 \Omega$$

Find the average power dissipated in the 60  $\Omega$  resistor in the circuit

$$i_g = 6 \cos 20,000t \text{ A.}$$

Here 6 is max value

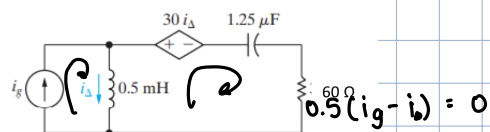

$$\text{KCL: } j10(I - i_g) + 30i_\Delta - j40I + 60I = 0$$

$$I(j10 - j40 + 60) = j10(6) - 30i_\Delta$$

$$I(60 - j30) = j60 - 30(6 - I)$$

$$I(60 - j30 - 30) = j60 - 180$$

$$I = \frac{-180 + j60}{30 - j30} = -4 - j2$$

$$= 2\sqrt{5} \angle -153.43^\circ$$

$$\begin{aligned} i_g &= I \\ i_\Delta &= I \\ 6 &= i_\Delta + I \\ i_\Delta &= 6 - I \end{aligned}$$

$$P_{60} =$$

$$V = (I \angle \theta_i)(R \angle \theta_r)$$


$$\frac{VI}{2} \cos(\theta_v - \theta_i)$$

$$\frac{I^2 R (\theta_i + \theta_r)}{2} \cos(\theta_v - \theta_i)$$

Find the average power, the reactive power, and the apparent power supplied by the voltage source in the circuit

$$v_g = 40 \cos 10^6 t \text{ V.}$$

Here 40 is max value

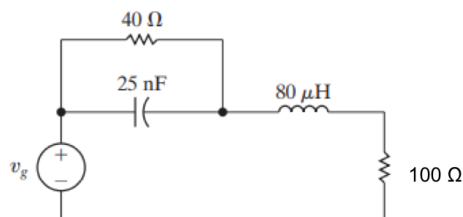

$$Q3. Z_L = j\omega L = j(10^6)(80 \times 10^{-6}) = j80 \Omega$$

$$Z_C = \frac{-j}{\omega C} = \frac{-j}{(10^6)(25 \times 10^{-9})} = -j40 \Omega$$

$$Z_{eq1} = 40 \Omega // 25 nF = \frac{1}{\frac{1}{40} + \frac{1}{-j40}} = 20 - j20$$

$$Z_{eq} = R_{eq1} + j80 \Omega + 100 \Omega = (20 - j20) + j80 + 100$$

$$= 120 + j60 \Omega \approx 60\sqrt{5} \angle 26.57^\circ$$

$$V = IZ \rightarrow I = \frac{V}{Z} = \frac{40 \angle 0^\circ}{60\sqrt{5} \angle 26.57^\circ} = 0.298 \angle -26.57^\circ$$

$$P_{ave} = \frac{(40)(0.298)}{2} \cos(0 + 26.57^\circ) = 5.33 \text{ W}$$

$$Q = \frac{(40)(0.298)}{2} \sin(0 + 26.57^\circ) = 2.67 \text{ W}$$

$$|S| = \sqrt{P^2 + Q^2} \quad \theta = \tan^{-1}(Q/P)$$

$$= \sqrt{(5.33)^2 + (2.67)^2} = 5.96 \quad = \tan^{-1}(2.67/5.33) = 26.61^\circ$$

$$\text{Apparent Power: } |S| = 5.96 \text{ W}$$

Q4

**Q-5** The real power delivered by a source to two impedances,  $Z_1 = 3 + j4 \Omega$  and  $Z_2 = 10 \Omega$ , connected in parallel, is 1100 W. Determine (a) the real power absorbed by each of the impedances and (b) the source current.

Here V is RMS value representation

$$P = VI \cos \theta_i$$

$$P_1 = V(V/Z_1) \cos \theta_{i1}$$

$$= \frac{V^2}{5} \cos(-53.13^\circ)$$

$$= 0.12 V^2$$

$$P_2 = V(V/Z_2) \cos \theta_{i2}$$

$$= \frac{V^2}{10} \cos 0^\circ$$

$$= 0.1 V^2$$

$$I_1 = \frac{50\sqrt{2}}{5} \angle -53.13^\circ$$

$$= 10\sqrt{2} \angle -53.13^\circ$$

$$I_2 = \frac{50\sqrt{2}}{10} \angle 0^\circ = 5\sqrt{2} \angle 0^\circ$$

$$V = IZ$$

$$I_1 = \frac{V}{Z_1} = \frac{V}{5 \angle -53.13^\circ} = \frac{V}{5} \angle -53.13^\circ$$

$$I_2 = \frac{V}{Z_2} = \frac{V}{10 \angle 0^\circ} = \frac{V}{10} \angle 0^\circ$$

$$P = P_1 + P_2$$

$$1100 = 0.12 V^2 + 0.1 V^2$$

$$V^2 = 5000$$

$$V = 50\sqrt{2}$$

$$P_1 = 0.12 V^2$$

$$= 0.12(5000)$$

$$= 600 \text{ W}$$

$$P_2 = 0.1 V^2$$

$$= 0.1(5000)$$

$$= 500 \text{ W}$$