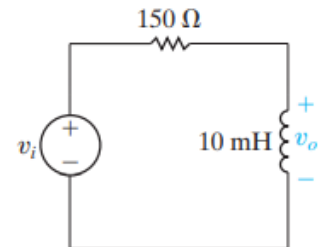


Homework-05 ENGR 117 Due date 04/25/2022

5 Questions 20 points each


Q-1 Consider the circuit shown below.

- a) This circuit behaves like what type of filter?
- b) What is the transfer function, of this filter?
- c) What is the cutoff frequency of this filter?
- d) Find the magnitude and phase of the transfer function at $s=j\omega_c$?




Q-2 For the bandpass filter shown. Find:

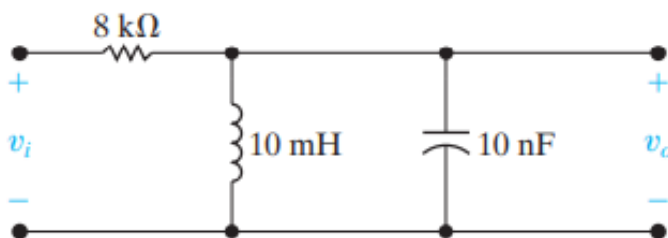(a) ω_o , (b) f_o , (c) Q , (d) ω_{c1} , (e) f_{c1} , (f) ω_{c2} , (g) f_{c2} , and (h) β .



Q-3 Verify the following for the bandpass filter: (show your work)
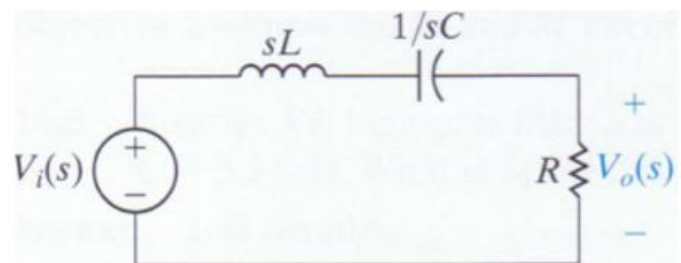
$$\omega_{c1} = \frac{-R}{2L} + \sqrt{\left(\frac{R}{2L}\right)^2 + \frac{1}{LC}}$$
$$\omega_{c2} = \frac{+R}{2L} + \sqrt{\left(\frac{R}{2L}\right)^2 + \frac{1}{LC}}$$



Q-4 Use a 5 nF capacitor to design a series RLC bandpass filter. The center frequency of the filter is 8 kHz, and the quality factor is 2. (Show your circuit)

- a) Specify the values of R and L.
- b) What is the lower cutoff frequency in kilohertz?
- c) What is the upper cutoff frequency in kilohertz?
- d) What is the bandwidth of the filter in kilohertz?

Q-5 Design the component values for the series RLC band reject filter so that the center frequency is 4 kHz and the quality factor is 5. Use a 500 nF capacitor. (Show your circuit)

- a) Specify the values of R and L.
- b) Find quality factor Q.