

Q1e

A 12 V battery supplies 130 mA (milli A) to a portable music system.

a) Determine the power delivered/absorbed by the music system

$P_{\text{music_system}} = 1.56$ ✓ W

b) Determine how much energy the battery delivers/absorbs in 5 minutes?

Energy $w = -468$ ✓ Joules

"+" = absorbed "-" = delivered

$$V = 12 \text{ V}$$


$$i = 130 \text{ mA} = 0.13 \text{ A}$$

$$P = vi$$

$$= (12)(0.13) = 1.56$$

$$P = w/t$$

$$w = Pt = 468 \text{ J}$$

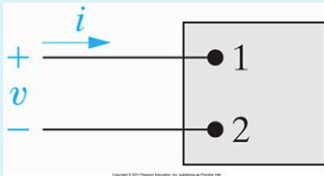

Q2c

The voltage and current at the terminals of this circuit are zero for $t < 0$.

For $t \geq 0$ $v = 40 e^{-1.750t}$ Volts $i = 8 e^{-1.750t}$ Amps

a) Find the power absorbed/delivered by the circuit element at $t = 500 \mu\text{s}$ (micro seconds).

$P_{500\mu\text{s}} = 55.6$ ✓ Watts

b) How much energy is absorbed/delivered by the circuit element between zero and $500 \mu\text{s}$ (micro seconds)?

$w = 75.54$ ✓ mJ (milli J)

$$P = vi$$

$$= 320 e^{-3500t}$$

$$= 320 e^{-1.75}$$

$$w = \int_0^{500\mu\text{s}} P(t) dt = \int_0^{500\mu\text{s}} 320 e^{-3500t} dt = -\frac{16}{175} e^{-3500t} \Big|_0^{500\mu\text{s}} = -\frac{16}{175} (e^{-1.75} - 1)$$

$$w = 0.07554 \text{ J} \approx 75.54 \text{ mJ}$$



Q3c

Given:

A student measured the voltage and current for the resistor as shown in the figure.

$v = 44.3$ Volts $i = -6.7$ Amps


The instructor verified that the voltage was measured correctly.

a) Was the current measured correctly?

Correct? = No ✗

b) Find the power absorbed/delivered by the resistor. If needed, correct any measuring mistake (sign not magnitude). "+" = absorbed and "-" = delivered

$P_R = 296.81$ ✓ Watts

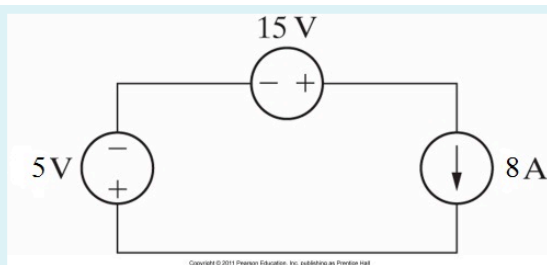

Q4b

Calculate the power in each circuit element.

"+" = absorbed and "-" = delivered

$P_{5V} = 40$ ✓ Watts

$P_{15V} = -120$ ✓ Watts

$P_{8A} = 80$ ✓ Watts


$$\text{KVL: } 5V - 15V - v = 0$$


$$v = -10V$$

$$P_{5V} = (5)(8) = 40 \text{ (ABS)}$$

$$P_{15V} = -(15)(8) = 120 \text{ (DELIVER)}$$

$$P_{8A} = (10)(8) = 80 \text{ (ABS)}$$

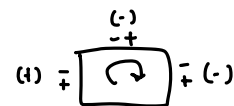

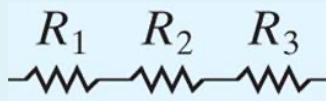

Q5

Given:


$$R_1 = 239 \, \Omega \text{ (Ohm)} \quad R_2 = 139 \, \Omega \text{ (Ohm)} \quad R_3 = 1553 \, \Omega \text{ (Ohm)}$$

Find the equivalent resistance R_{Eq} .

$$R_{Eq} = ??? \, \Omega \text{ (Ohm)}$$

Answer: ✓

$$R = 239 + 139 + 1553 = 1931$$

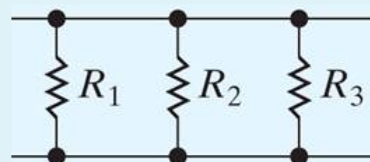

Q6

Given:

$$R_1 = 149 \, \Omega \text{ (Ohm)} \quad R_2 = 280 \, \Omega \text{ (Ohm)} \quad R_3 = 1699 \, \Omega \text{ (Ohm)}$$


Find the equivalent resistance R_{Eq} .

$$R_{Eq} = ?? \, \Omega \text{ (Ohm)}$$

Answer:

$$\frac{1}{R} = \frac{1}{149} + \frac{1}{280} + \frac{1}{1699}$$

$$R = 91.98$$

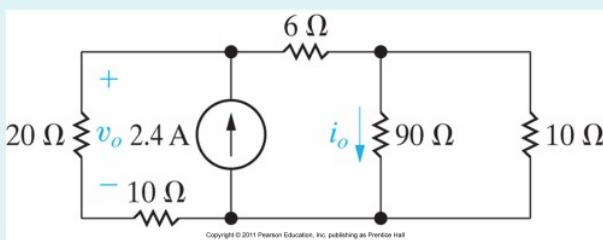

Q7b

Find the current through the 10 Ω (Ohm) resistor on the far right side of the circuit.

$i_{10\Omega} =$ ✓ A

$$\frac{i_1}{2.4A} = \frac{i_n}{i_o}$$


$$V = iR$$

$$i_1 = \frac{V_1}{20+10}$$

$$i_n = \frac{V_n}{15}$$

$$i_1 - 2.4 + i_n = 0$$

$$i_n = 2.4 - i_1$$

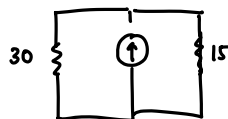

$$V_{30} = V_{2.4} = V_{15}$$