

①

AP9.02_9ed

Find the time-domain expression for each phasor below.

The time domain form is assumed to be similar to $x(t) = \cos(\omega t + \phi^\circ)$ a) $V = 18.6$ at angle -54° Volts

$$v(t) = 18.6 \cos(\omega t + -54^\circ) \text{ V}$$

b) $I = (20$ at angle $45^\circ) - (50$ at angle $-30^\circ)$ mA

$$i(t) = 48.809 \cos(\omega t + 126.684^\circ) \text{ mA}$$

c) $V = (20 + j 80) - (30$ at angle $15^\circ)$ Volts

$$v(t) = 72.790 \cos(\omega t + 97.085^\circ) \text{ V}$$

$$(a) \quad 18.6 \angle -54^\circ \quad V_m \angle \phi$$

$$V = 18 \cos(\omega t - 54^\circ) \text{ V}$$

$$(b) \quad 20 \angle 45^\circ \rightarrow 20 \cos(45^\circ) + j 20 \sin(45^\circ) \\ \rightarrow 10\sqrt{2} + 10j\sqrt{2}$$

$$50 \angle -30^\circ \rightarrow 50 \cos(-30^\circ) - j 50 \sin(30^\circ) \\ 25\sqrt{3} - 25j$$

$$(20 \angle 45^\circ) - (50 \angle -30^\circ) \\ (10\sqrt{2} + 10j\sqrt{2}) - (25\sqrt{3} - 25j) \\ -29.159 + 39.142j \quad -x + y$$

$$A = \sqrt{(-29.159)^2 + (39.142)^2} \\ = 48.809$$

$$\phi = \tan^{-1} \left[\frac{39.142}{-29.159} \right] = -53.315^\circ \quad \text{QUADRANT II} \\ +180^\circ \\ = 126.684^\circ$$

$$A \angle \phi = 48.809 \angle 126.684^\circ$$

$$i(t) = 48.809 \cos(\omega t + 126.684^\circ) \text{ mA}$$

$$(c) \quad 30 \angle 15^\circ \rightarrow 30 \cos(15^\circ) + j 30 \sin(15^\circ) \\ \rightarrow 28.978 + 7.766j$$

$$(20 + j 80) - (28.978 + 7.766j) \\ -8.978 + 72.234j$$

$$A = \sqrt{(8.978)^2 + (72.234)^2} = 72.790$$

$$\phi = \tan^{-1} \left[\frac{72.234}{-8.978} \right] = -82.916^\circ \quad \text{Q II} \\ +180^\circ = 97.085^\circ$$

$$A \angle \phi = 72.790 \angle 97.085^\circ$$

$$v(t) = 72.790 \cos(\omega t + 97.085^\circ) \text{ V}$$

②

P9.06_6ed

Use the concept of the phasor to combine the following sinusoidal functions into a single trigonometric express.

The time domain form is assumed to be similar to $x(t) = \cos(\omega t + \phi^\circ)$ a) $x(t) = 100 \cos(300t + 45^\circ) + 500 \cos(300t - 60^\circ)$

$$x(t) = 483.856 \cos(300t + -48.485^\circ)$$

b) $y(t) = 250 \cos(377t + 30^\circ) - 150 \sin(377t + 140^\circ)$

$$y(t) = 120.511 \cos(377t + 4.804^\circ)$$

c) $v(t) = 60 \cos(100t + 60^\circ) - 120 \sin(100t - 125^\circ) + 100 \cos(100t + 90^\circ)$

$$v(t) = 152.877 \cos(100t + 32.942^\circ)$$

d) $w(t) = 100 \cos(\omega t + 40^\circ) + 100 \cos(\omega t + 160^\circ) + 100 \cos(\omega t - 80^\circ)$

$$w(t) = 0 \cos(\omega t + 0^\circ)$$

$$(a) \quad 100 \angle 45^\circ + 500 \angle -60^\circ \\ (50\sqrt{2} + 50j\sqrt{2}) + (250 - 250j\sqrt{3}) \\ 320.711 - 362.302j$$

$$A \angle \phi = 483.856 \angle -48.485^\circ \rightarrow 483.856 \angle 311.515^\circ$$

$$(b) \quad 150 \sin(377t + 140^\circ) \rightarrow 155 \cos[90^\circ - (377t + 140^\circ)] \\ 155 \cos(-377t - 50^\circ) \\ 155 \cos(377t + 50^\circ)$$

$$250 \angle 30^\circ - 150 \angle 50^\circ$$

$$120.088 + j10.093$$

$$A \angle \phi = 120.511 \angle 4.804^\circ$$

$$(c) \quad 120 \sin(100t - 125^\circ) \rightarrow 120 \cos(-100t + 215^\circ) \\ 120 \cos(100t - 215^\circ)$$

$$60 \angle 60^\circ - 120 \angle -215^\circ + 100 \angle 90^\circ$$

$$128.298 + 83.132j$$


$$A \angle \phi = 152.877 \angle 32.942^\circ$$

$$(d) \quad 100 \angle 40^\circ + 100 \angle 160^\circ + 100 \angle -80^\circ$$

$$(76.604 + j 64.279) + (-93.969 + j 39.202) + (17.365 - j 98.481) \\ 0 + j 0$$

$$A \angle \phi = 0 \angle 0^\circ$$

3

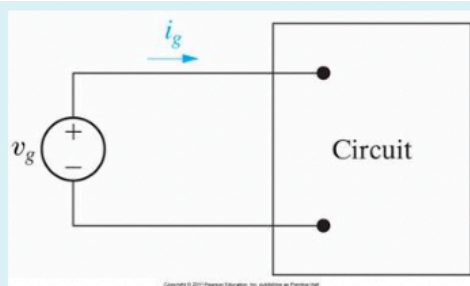

P9.12_9ed

The expressions for the steady-state voltage and current at the terminals of the circuit are

$$v_g = 300 \cos(5,000 \pi t + 78^\circ) \text{ V}$$

$$i_g = 6 \sin(5,000 \pi t + 123^\circ) \text{ A}$$

a) What is the impedance seen by the source? Write in rectangular form.

$$Z = 35.35 + j 35.35 \, \Omega \text{ (Ohm)}$$

b) By how much time t in microseconds is the current out of phase with the voltage?

$$i_g \text{ lags } v_g \text{ by } 50 \, \mu\text{s (micro sec)}$$

$$(a) \, v_g : 300 \angle 78^\circ$$

$$i_g : 6 \angle 33^\circ$$

$$V = 1Z$$

$$Z = \frac{V}{I} = \frac{300 \angle 78^\circ}{6 \angle 33^\circ} = 50 \angle 45^\circ$$

$$\rightarrow 35.35 + j35.35j$$

$$i_g = 6 \sin(5000\pi + 123^\circ) \text{ A}$$

$$= 6 \cos(-5000\pi - 33^\circ) \text{ A}$$

$$= 6 \cos(5000\pi + 33^\circ) \text{ A}$$

$$(b) \, \omega = 5000\pi$$

$$\omega = 2\pi/T \rightarrow T = 2\pi/5000\pi = 4 \times 10^{-4} \text{ s} \approx 400 \mu\text{s}$$

$$t = \frac{45^\circ}{360^\circ} \cdot 400 \mu\text{s} = 50 \mu\text{s}$$

4

AP9.01_9ed

Find the phasor (based on cosine) transform of each trigonometric function:

a) $v = 170 \cos(377t - 40^\circ)$ Volts

$$V_{\text{phasor}} \text{ Magnitude} = 170 \text{ V}$$

$$\text{Angle} = -40^\circ \text{ (Degrees)}$$

b) $i = 10 \sin(1,000t + 20^\circ)$ Amps

$$I_{\text{phasor}} \text{ Magnitude} = 10 \text{ A}$$

$$\text{Angle} = -70^\circ \text{ (Degrees)}$$

c) $i = 5 \cos(\omega t + 36.87^\circ) + 10 \cos(\omega t - 53.13^\circ)$ Amps

$$I_{\text{phasor}} \text{ Magnitude} = 11.18 \text{ A}$$


$$\text{Angle} = -26.57^\circ \text{ (Degrees)}$$

d) $v = 300 \cos(20,000\pi t + 45^\circ) - 100 \sin(20,000\pi t + 30^\circ)$ mV

$$V_{\text{phasor}} \text{ Magnitude} = 339.89 \text{ mV}$$

$$\text{Angle} = 61.51^\circ \text{ (Degrees)}$$

5

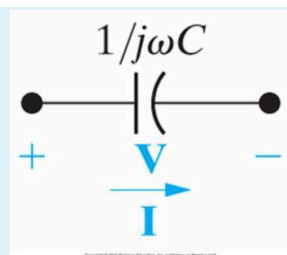

AP9.04_9ed

The voltage across the terminals of the $5 \, \mu\text{F}$ (micro F) capacitor is $30 \cos(4,000t + 25^\circ)$ V.

a) Calculate the capacitive reactance.

$$X_C = -50 \, \Omega$$

b) Calculate the impedance of the capacitor.

$$Z_C = j -50 \, \Omega$$

c) Calculate the phasor current I .

$$I = \text{Magnitude } 0.60 \text{ with Angle } 114.84^\circ \text{ Degrees Amps}$$

d) Write the steady-state expression for $i(t)$.

$$i(t) = 0.6 \cos(4000t + 114.84^\circ) \text{ Amps}$$

$$V = 30 \cos(4000t + 25^\circ) \text{ V}$$

$$C = 5 \mu\text{F} = 5 \times 10^{-6} \text{ F}$$

$$\omega = 4000$$

$$(a) \, X_C = \frac{1}{\omega C} = \frac{1}{(4000)(5 \times 10^{-6})} = -50 \, \Omega$$

$$(b) \, Z_C = \frac{1}{j\omega C} = \frac{1}{j(4000)(5 \times 10^{-6})} = -j50 \, \Omega$$

$$(c) \, V = 30 \cos(4000t + 25^\circ) \text{ V}$$

$$V = 30 \angle 25^\circ \rightarrow 27.189 + j12.679$$

$$V = ZI \rightarrow I = \frac{V}{Z} = \frac{27.189 + j12.679}{-j50} =$$

$$I = -\frac{0.54378}{j} - 0.25358$$

$$= j0.54 - 0.25 \approx -0.25 + j0.54$$

$$I = 0.60 \angle 114.84^\circ$$

$$(d) \, i = \frac{30}{-j50} \cos(4000t + 25^\circ)$$

$$i = 0.6 \cos(4000t + 114.84^\circ)$$

6

P9.12_8ed

A 50 Hz sinusoidal voltage with a maximum amplitude of 340 V at $t = 0$ is applied across the terminals of an inductor. The maximum amplitude of the steady-state current in the inductor is 8.5 A.

a) What is the frequency of the inductor current?

$\omega =$ ✓ rad/sec

b) If the phase angle of the voltage is zero, what is the phase angle of the current?

$\phi_I =$ ✓ ° (Degree)

c) What is the reactance of the inductor?

$X_L =$ ✓ Ω (Ohm)

d) What is the inductance of the inductor?

$L =$ ✓ mH (milli H)

(a) $f = 50 \text{ Hz}$

$\omega = 2\pi f = 2\pi(50) = 100\pi \approx 314.16 \text{ rad/s}$

(b) $\phi_V = 0$

(b)

The phase angle of inductor voltage, $\phi_V = 0^\circ$

$\phi_I = -90^\circ$

Since the current through the inductor lags behind the voltage by exactly 90° , the phase angle of the current, ϕ_I is -90° .

(c) $V = 340 \angle 0^\circ \text{ V}$

$I = 8.5 \angle -90^\circ \text{ A}$


$Z_L = \frac{V}{I} = \frac{340 \angle 0^\circ}{8.5 \angle -90^\circ} = 40 \angle 90^\circ \approx 0 + j40 \Omega$

$Z_L = jX_L \rightarrow X_L = 40$

(d) $jX_L = j\omega L$

$L = X_L / \omega = 40 / 100\pi \approx 0.12732 \approx 127.32 \text{ mH}$

3

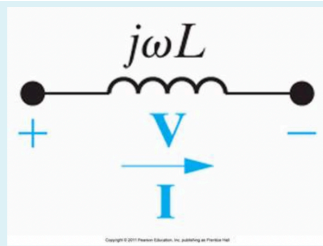

AP9.03_9ed

The current in the inductor is $10 \cos(10,000t + 30^\circ) \text{ mA}$.

Given: $L = 20 \text{ mH}$

a) Calculate the inductance reactance.

$X_L =$ ✓ Ω (Ohm)

b) Calculate the impedance of the inductor.

$Z_L = j$ ✓ Ω (Ohm)

c) Calculate the phasor voltage V .

$V =$ Magnitude ✓ with Angle ✓ ° (Degrees) Volts

d) Write the steady-state expression for $v(t)$.

$v(t) =$ ✓ $\cos($ ✓ $t +$ ✓ °) Volts

(a) $X_L = \omega L = (10,000)(20 \times 10^{-3})$
 $= 200$

(b) $Z_L = j\omega L = jX_L = j200$

(c) $V = ZI$

$= (j200)[(10 \angle 30^\circ) \times 10^{-3}]$

$= (j200)[(5\sqrt{3} + j5) \times 10^{-3}] = (j1000\sqrt{3} + 1000) \times 10^{-3}$

$= 1 + j\sqrt{3} \approx 2 \angle 60^\circ$

(d) $v(t) = 1000 \cos(10000t + 89.50^\circ)$