

①

P6.03\_6ed

The current in a 2 mH (milli Henry) inductor is  $i_L = 50 t e^{-10t}$  Amps for  $t \geq 0$ .

a) Find the voltage across the inductor for  $t = 0^+$ .

$$v_L(t=0^+) = 100 \text{ mV (milli Volt)}$$

b) Find the power absorbed/delivered by the inductor at  $t = 50$  ms (milli sec).

$$P_L(t=50 \text{ ms}) = 45.98 \text{ mW (milli Watt)}$$

c) Find the power absorbed/delivered by the inductor at  $t = 200$  ms (milli sec).

$$P_L(t=200 \text{ ms}) = -18.31 \text{ mW (milli Watt)}$$

$$i_L = 50te^{-10t}$$

$$v_L = L \frac{di}{dt}$$

$$v_L = L \frac{d}{dt}(50te^{-10t})$$

$$v_L = 50L \frac{d}{dt}(te^{-10t})$$

$$= 50L [e^{-10t} - 10te^{-10t}]$$

$$v_L(t) = 50(2 \times 10^{-3}) [e^{-10t}(1-10t)]$$

when  $t=0$ :

$$v_L(t) = 0.1[(1-10t)e^{-10t}]$$

$$v_L(0) = 0.1(1-0)e^0$$

$$= 0.1 \text{ V} \approx 100 \text{ mV}$$

$$b.) P_L = Li \frac{di}{dt}$$

$$P_L(t) = (2 \times 10^{-3})(50te^{-10t}) \frac{d}{dt}(50te^{-10t})$$

$$= 5te^{-10t} [e^{-10t}(1-10t)]$$

$$= 5te^{-20t}(1-10t)$$

$$P_L(0.05) = 5(0.05)e^{-20(0.05)} [1-10(0.05)]$$

$$= 0.04598 \text{ W} \approx 45.98 \text{ mW}$$

$$c.) P_L = Li \frac{di}{dt}$$

$$P_L(t) = (2 \times 10^{-3})(50te^{-10t}) \frac{d}{dt}(50te^{-10t})$$


$$= 5te^{-10t} [e^{-10t}(1-10t)]$$

$$= 5te^{-20t}(1-10t)$$

$$P_L(0.2) = 5(0.2)e^{-20(0.2)} [1-10(0.2)]$$

$$= -0.01831 \text{ W} \approx -18.31 \text{ mW}$$

②

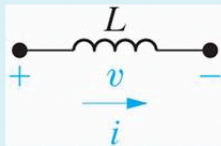

CQ6.09

Given:

$L = 18 \text{ mH}$  (milli Henry)

At an instant of time the inductor has a current of 4.8 Amps which is increasing by 10.4 Amps/ms.

What is the power absorbed/delivered by the inductor at that instant of time?


$P_L = ??$  Watts

Answer: 898.56

$$P_L = Li \frac{di}{dt}$$

$$= \left( 18 \text{ mH} \times \frac{1 \text{ H}}{1000 \text{ mH}} \right) (4.8 \text{ A}) \left( \frac{10.4 \text{ A}}{\text{ms}} \times \frac{1000 \text{ ms}}{1 \text{ s}} \right) = 898.56 \text{ W}$$

③

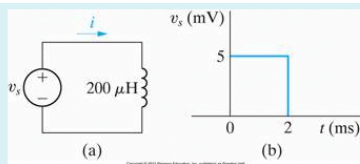

P6.03\_9ed

The voltage at the terminals of the  $200 \mu\text{H}$  (micro Henry) inductor is shown in the figure.

The inductor current  $i$  is known to be zero for  $t \leq 0$ .

Derive an expression for  $i$  for  $0 \leq t \leq 2$  ms (milli sec).

Select one:

☒ a.  $i = 25 t \text{ A}$   $0 \leq t \leq 2 \text{ ms}$  (milli sec)

☐ b.  $i = -25 t \text{ A}$   $0 \leq t \leq 2 \text{ ms}$  (milli sec)

☐ c.  $i = 5 t \text{ A}$   $0 \leq t \leq 2 \text{ ms}$  (milli sec)

☐ d.  $i = 25 \text{ A}$   $0 \leq t \leq 2 \text{ ms}$  (milli sec)

$$V_s = 5 \times 10^{-3} \text{ V} \quad 0 \leq t \leq 2 \text{ ms}$$

$$L = 200 \times 10^{-6} \text{ H}$$

$$\text{for } 0 \leq t \leq 2 \text{ ms} : i = 25t$$

$$t \geq 2 \text{ ms} : i = 0.05 \text{ A}$$

$$i = \frac{1}{L} \int_{t_0}^t v_L dt + i_L(t_0)$$

$$= \frac{1}{200 \times 10^{-6}} \int_0^{2 \times 10^{-3}} (5 \times 10^{-3}) dt + 0$$

$$= \frac{5 \times 10^{-3}}{200 \times 10^{-6}} \int_0^{2 \times 10^{-3}} dt$$

$$= 25 [t]_0^{2 \times 10^{-3}} = 25 (2 \times 10^{-3}) = 0.05 \text{ A}$$

4

P6.17\_6ed

The voltage across the terminals of a  $0.40 \mu\text{F}$  (micro F) capacitor is:

$$V_C(t) = 25 \text{ V for } t \leq 0;$$

$$V_C(t) = A_1 t e^{-1500t} + A_2 e^{-1500t} \text{ V for } t \geq 0.$$

The initial current in the capacitor is  $90 \text{ mA}$  (milli Amp).

Assume the passive sign convention (current is in the direction of voltage drop).

a) What is the initial energy stored in the capacitor?

$$w(t=0) = 125 \text{ mJ (micro J)}$$

b) Find the coefficients  $A_1$  and  $A_2$ .

$$A_1 = 262500 \text{ Volts/Sec}$$

$$A_2 = 25 \text{ Volts/Sec}$$

c) Find the capacitor current at  $t = 0.4 \text{ ms}$  (milli sec).

$$i(t = 0.4 \text{ ms}) = 14.82 \text{ mA (milli Amp)}$$

d) Find the capacitor current at  $t = 2 \text{ ms}$  (milli sec).

$$i(t = 2 \text{ ms}) = -11.20 \text{ mA (milli Amp)}$$

$$C = 0.40 \times 10^{-6} \text{ F}$$

$$V_C(t) = 25 \text{ V } t \leq 0$$

$$V_C(t) = A_1 t e^{-1500t} + A_2 e^{-1500t} \text{ V } t \geq 0$$

$$i_C(0) = 0.09 \text{ A}$$

$$(a) \quad w = \frac{1}{2} C V^2$$

$$= \frac{1}{2} (0.40 \times 10^{-6}) (25)^2$$

$$= 1.25 \times 10^{-4} \text{ J} \approx 125 \mu\text{J}$$

$$(b) \quad V_C(t) = A_1 t e^{-1500t} + A_2 e^{-1500t}$$

$$@ t = 0: V_C(t) = 25 \text{ V}$$

$$25 = A_2 \text{ V/s}$$

$$i_C = C \frac{dV}{dt}$$

$$= (0.40 \times 10^{-6}) \frac{d}{dt} (A_1 t e^{-1500t} + A_2 e^{-1500t})$$

$$= 0.40 \times 10^{-6} [A_1 (e^{-1500t} - 1500t e^{-1500t}) - 1500 A_2 e^{-1500t}]$$

$$@ t = 0:$$

$$0.09 = 0.40 \times 10^{-6} (A_1 - 1500 A_2)$$

$$225000 = A_1 - 1500 A_2$$

$$A_1 = 225000 + 1500(25) = 262500 \text{ V/s}$$

$$(c) \quad V_C(t) = 262500 t e^{-1500t} + 25 e^{-1500t}$$

$$i_C = C \frac{dV}{dt}$$

$$= (0.40 \times 10^{-6}) \frac{d}{dt} (262500 t e^{-1500t} + 25 e^{-1500t})$$

$$= (0.40 \times 10^{-6}) [262500 (e^{-1500t} - 1500t e^{-1500t}) - 37500 e^{-1500t}]$$

$$(0.40 \times 10^{-6}) [e^{-1500t} [225000 - (393.75 \times 10^6)t]]$$

$$@ t = 0.4 \text{ ms} \approx 4 \times 10^{-4} \text{ s}$$

$$i_C = 0.014818 \text{ A} \approx 14.82 \text{ mA}$$

$$@ t = 2 \text{ ms} \approx 2 \times 10^{-3} \text{ s}$$

$$i_C = -0.01120 \text{ A} \approx -11.20 \text{ mA}$$

$$C = 5 \times 10^{-6} \text{ F}$$

$$V_C = 500t e^{-2500t} \text{ V}$$

$$i_C = C \frac{dV}{dt}$$

$$i_C = (5 \times 10^{-6}) \frac{d}{dt} (500t e^{-2500t})$$

$$= (2.5 \times 10^{-3}) [e^{-2500t} - 2500t e^{-2500t}]$$

$$= (2.5 \times 10^{-3}) e^{-2500t} (1 - 2500t) \text{ V}$$

$$i_C = 2.5 e^{-2500t} (1 - 2500t) \text{ mV}$$

$$P_C = V i_C$$

$$= (500t e^{-2500t}) (2.5 \times 10^{-3}) e^{-2500t} (1 - 2500t)$$

$$= 1.25 t e^{-5000t} (1 - 2500t)$$

$$@ t = 80 \mu\text{s} \approx 80 \times 10^{-6} \text{ s}$$

$$P_C(t = 80 \mu\text{s}) = 5.3626 \times 10^{-6} \text{ W} \approx 5.3626 \mu\text{W}$$

5

P6.13\_10ed

The voltage across a  $5 \mu\text{F}$  (micro F) capacitor is  $v_C = 500 t e^{-2500t} \text{ V}$  for  $t \geq 0$ .

Find the current "through" the capacitor for  $t > 0$ .

Find the power at the terminals of the capacitor when  $t = 80 \mu\text{s}$  (micro sec).

Select one:

- ☒ a.  $i_C = 2.5 e^{-2500t}$  (1-2500 t) mV (milli Volts)  $p_C = 53.626 \mu\text{W}$  (micro Watts) absorbing

- ☐ b.  $i_C = 2.5 e^{-2500t}$  (1-2500 t) V  $p_C = 53.626 \text{ W}$  absorbing

- ☐ c.  $i_C = 5.3 e^{-5000t}$  (1-2500 t) mV (milli Volts)  $p_C = -53.626 \mu\text{W}$  (micro Watts) delivering

- ☐ d.  $i_C = 0.5 e^{-2500t}$  (1-2500 t) mV (milli Volts)  $p_C = 13.626 \text{ mW}$  (milli Watts) absorbing

6

P6.18\_9ed

The initial current in a  $0.2 \mu\text{F}$  (micro F) capacitor is  $250 \text{ mA}$  (milli Amp) with an initial voltage of  $150 \text{ V}$ .

What is the initial energy stored in the capacitor?

$$w(t=0) = \boxed{2.25} \text{ mJ (milli J)}$$


$$C = 0.2 \times 10^{-6} \text{ F}$$

$$\text{At } t=0: i = 0.25 \text{ A}$$

$$V = 150 \text{ V}$$

$$w = \frac{1}{2} CV^2 = \frac{1}{2} (0.2 \times 10^{-6}) (150)^2 \\ = 2.25 \times 10^{-3} \text{ J} \approx 2.25 \text{ mJ}$$

7

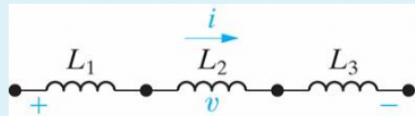

CQ6.04

Given:

$$L_1 = 1.8 \text{ mH (milli Henry)} \quad L_2 = 6.7 \text{ mH (milli Henry)}$$

$$L_3 = 4.4 \text{ mH (milli Henry)}$$

Find the equivalent inductance  $L_{\text{Eq}}$ .


$$L_{\text{Eq}} = ?? \text{ mH (milli Henry)}$$

Answer:

$$\boxed{12.9}$$

$$L_{\text{eq}} = L_1 + L_2 + L_3 \\ = 1.8 \text{ mH} + 6.7 \text{ mH} + 4.4 \text{ mH} \\ = 12.9 \text{ mH}$$


8

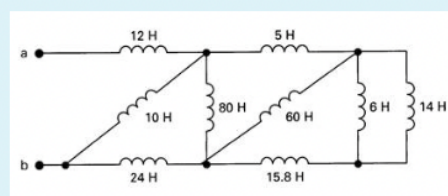

P6.21\_6ed


Find the equivalent inductance with respect to the terminals a,b.

$$L_{\text{Eq}} = \boxed{20} \text{ H}$$

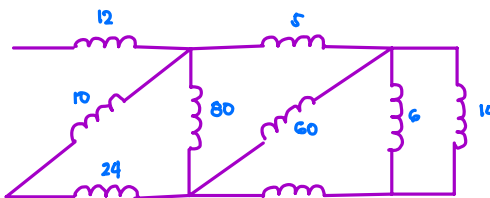


$$L_{\text{parallel}} = \frac{(6)(14)}{6+14} = 4.2 \text{ H}$$
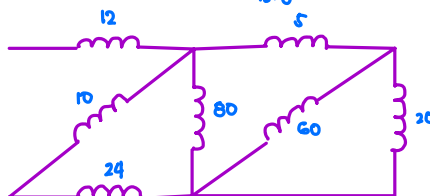
$$L_{\text{series}} = 4.2 + 15.8 = 20 \text{ H}$$



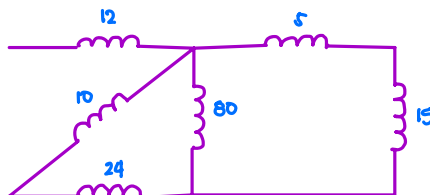
$$L_{\text{parallel}} = \frac{(60)(20)}{60+20} = 15 \text{ H}$$



$$L_{\text{series}} = 5 + 15 = 20 \text{ H}$$
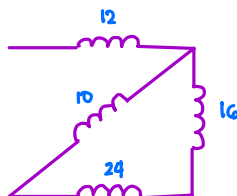
$$L_{\text{parallel}} = \frac{(80)(20)}{80+20} = 16 \text{ H}$$




$$L_{\text{series}} = 16 + 24 = 40 \text{ H}$$

$$L_{\text{parallel}} = \frac{(10)(40)}{10+40} = 8 \text{ H}$$

$$L_{\text{series}} = 12 + 8 = 20 \text{ H}$$

9

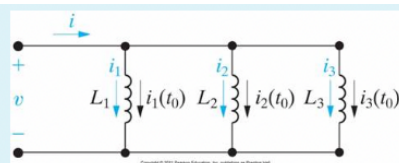

CQ6.05

Given:

$$L_1 = 2.7 \text{ mH (milli Henry)} \quad L_2 = 7.5 \text{ mH (milli Henry)}$$

$$L_3 = 8.0 \text{ mH (milli Henry)}$$

Find the equivalent inductance  $L_{\text{Eq}}$ .

$$L_{\text{Eq}} = ?? \text{ mH (milli Henry)}$$

Answer:


$$\boxed{1.5906}$$

$$\frac{1}{L_{\text{eq}}} = \frac{1}{L_1} + \frac{1}{L_2} + \frac{1}{L_3}$$

$$= \frac{1}{2.7} + \frac{1}{7.5} + \frac{1}{8.0}$$

$$L_{\text{eq}} = \frac{1}{\frac{1}{2.7} + \frac{1}{7.5} + \frac{1}{8.0}} = 1.5906 \text{ mH}$$

10

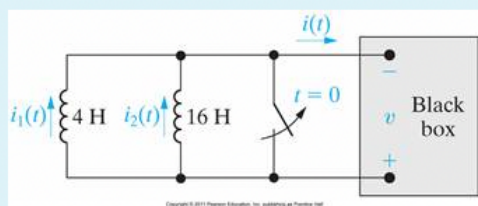

P6.25\_9ed

Given: The voltage  $v$  (across all the parallel elements) is  $64e^{-4t}$  Volts for  $t > 0$ .

And at  $t = 0^-$   $i_1 = -10$  A and  $i_2 = 5$  A

a) Find the equivalent inductance of the two inductors in the figure.

$$L_{Eq} = 3.2 \text{ H}$$

b) Find  $i(t)$  at  $t = 1$  sec.

$$i(t = 1 \text{ s}) = -91.58 \text{ mA (milli Amp)}$$


$$(a) \quad L_{eq} = \frac{(4)(16)}{4+16} = 3.2 \text{ H}$$

$$\begin{aligned} (b) \quad i_1(t) &= \frac{1}{L} \int_{t_0}^t v_L dt + i_L(t_0) \\ &= \frac{1}{4} \int_0^1 64e^{-4t} dt + (-10) \\ &= 16 \left[ -\frac{1}{4} e^{-4t} \right]_0^1 - 10 \\ &= 16 \left[ -\frac{1}{4} e^{-4} + \frac{1}{4} \right] - 10 \\ &= -4e^{-4} + 4 - 10 = -4e^{-4} - 6 \end{aligned}$$

$$\begin{aligned} i_2(t) &= \frac{1}{16} \int_0^1 64e^{-4t} dt + 5 \\ &= 4 \left[ -\frac{1}{4} e^{-4t} \right]_0^1 + 5 \\ &= -e^{-4} + 1 + 5 = -e^{-4} + 6 \end{aligned}$$

$$\begin{aligned} i &= i_1 + i_2 = -4e^{-4} - 6 - e^{-4} + 6 = -5e^{-4} \\ &= -0.09158 \text{ A} \approx -91.58 \text{ mA} \end{aligned}$$

11

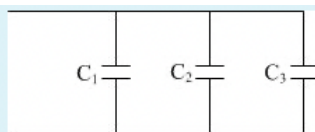

Given:

$$C_1 = 1.7 \text{ } \mu\text{F (micro F)} \quad C_2 = 7.7 \text{ } \mu\text{F (micro F)}$$

$$C_3 = 1.2 \text{ } \mu\text{F (micro F)}$$

Find the equivalent capacitance  $C_{Eq}$ .

$$C_{Eq} = ?? \text{ } \mu\text{F (micro F)}$$


Answer:

$$10.6$$

PARALLEL:

$$\begin{aligned} C_{eq} &= C_1 + C_2 + C_3 \\ &= 1.7 + 7.7 + 1.2 \\ &= 10.6 \text{ } \mu\text{F} \end{aligned}$$

12

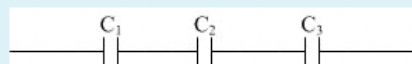

CQ6.01

Given:

$$C_1 = 2.6 \text{ } \mu\text{F (micro Farad)} \quad C_2 = 7.2 \text{ } \mu\text{F (micro Farad)}$$

$$C_3 = 7.1 \text{ } \mu\text{F (micro Farad)}$$

Find the equivalent capacitance  $C_{Eq}$ .

$$C_{Eq} = ?? \text{ } \mu\text{F (micro Farad)}$$

Answer:

$$1.505$$

SERIES:

$$\frac{1}{C_{eq}} = \frac{1}{C_1} + \frac{1}{C_2} + \frac{1}{C_3}$$

$$\frac{1}{C_{eq}} = \frac{1}{2.6} + \frac{1}{7.2} + \frac{1}{7.1}$$

$$C_{eq} = 1.505 \text{ } \mu\text{F}$$

$$C_{series} = \frac{(48)(16)}{48+16} = 12 \text{ } \mu\text{F}$$

$$C_{parallel} = 12 + 3 = 15 \text{ } \mu\text{F}$$

$$C_{series} = \frac{(30)(15)}{30+15} = 10 \text{ } \mu\text{F}$$


$$C_{parallel} = 10 + 10 = 20 \text{ } \mu\text{F}$$

$$C_{series} = \frac{1}{C_{eq}} = \frac{1}{5} + \frac{1}{20} + \frac{1}{4}$$

$$C_{eq} = 2 \text{ } \mu\text{F}$$

$$\begin{aligned} -V + 5 + 10 - 20 + 30 &= 0 \\ V &= 25 \text{ V} \end{aligned}$$

13

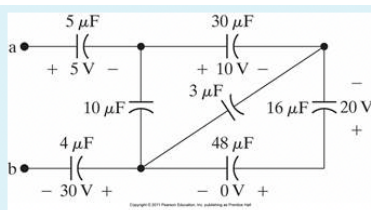

P6.26\_9ed


Find the equivalent capacitance with respect to the terminals a,b.

$$C_{Eq} = 2 \text{ } \mu\text{F (micro F)}$$

And find the initial voltage across the equivalent capacitance.

$$V_{Ceq} = 25 \text{ V}$$

19

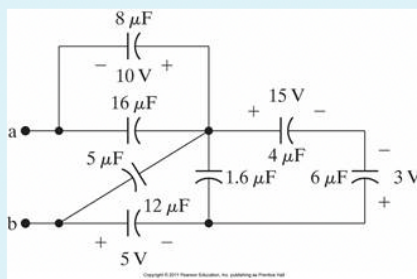

P6.27\_9ed

Find the equivalent capacitance with respect to the terminals a,b.

$C_{Eq} = 6.03 \mu\text{F}$  (micro F)

Find the initial voltage across the equivalent capacitance.

$V_{Ceq} = -3 \text{ V}$

$$C_{series} : \frac{(15)(3)}{15+3} = 2.5 \mu\text{F}$$

$$C_{parallel} : 8+16 = 24 \mu\text{F}$$

$$C_{parallel} : 1.6+2.5 = 4.1 \mu\text{F}$$

$$C_{series} : \frac{(12)(4.1)}{12+4.1} = \frac{492}{161}$$

$$-V - 10 + 15 - 3 - 5 = 0 \\ V = -3 \text{ V}$$

$$C_{parallel} : 5 + \frac{492}{161} = \frac{1297}{161}$$

$$C_{series} : \frac{(24)(\frac{1297}{161})}{24 + \frac{1297}{161}} = 6.03 \mu\text{F}$$