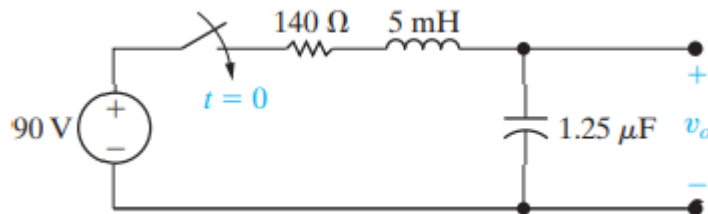


## Homework-04      ENGR 117      Due date 04/06/2022

5 Questions    20 points each

**Q-1** Find  $V_o$  and  $v_o$  in the circuit shown below if the initial energy is zero and the switch is closed at  $t=0$ . Also find the transfer function and identify the poles and zeros for this circuit. (Use circuit transform method)




**Q-2** There is no energy stored in the circuit shown below at the time the voltage source is turned on. (Use circuit transform method)

$$v_g = 325u(t) \text{ V.}$$

a) Find  $V_o$  and  $I_o$

b) Find  $v_o$  and  $i_o$

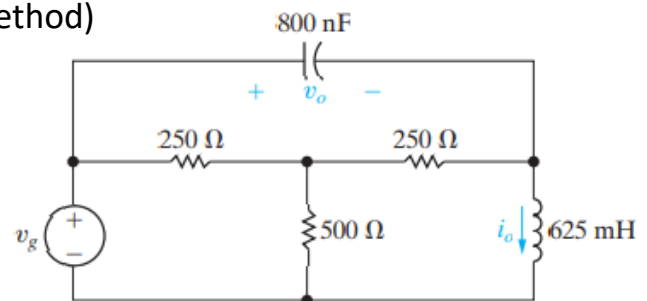

**Q-3** Draw the magnitude and phase Bode diagram for the following transfer function.

$$H(s) = \frac{s(s+100)(s+1000)}{(s+10)(s+10000)}$$



**Q-4** Draw the magnitude and phase Bode diagram for the following transfer function.

$$H(s) = \frac{(s+3)}{(s+30)(s+300)}$$

**Q-5** Draw the magnitude and phase Bode diagram for the following transfer function.

$$H(s) = \frac{(s+1)(s+10)}{s(s+10)^2}$$

Q-1

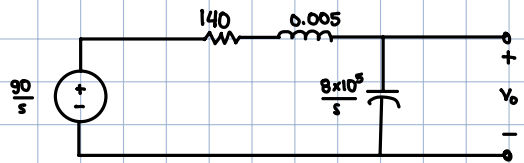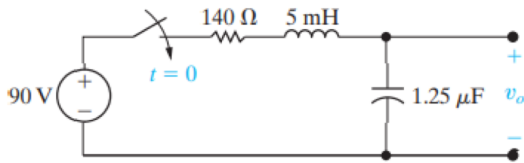

$$V_o = \frac{1.44 \times 10^{10}}{s(s^2 + 28 \times 10^3 s + 16 \times 10^6)}$$

$$= \frac{1.44 \times 10^{10}}{s(s + 8000)(s + 20000)} = \frac{A}{s} + \frac{B}{s + 8000} + \frac{C}{s + 20000}$$

$$1.44 \times 10^{10} = A(s + 8000)(s + 20000) + B(s)(s + 20000) + C(s)(s + 8000)$$

$$s = 0: 1.44 \times 10^{10} = A(160 \times 10^6) \quad A = 90$$


$$s = -8000: 1.44 \times 10^{10} = B(-96 \times 10^6) \quad B = -150$$

$$s = -20000: 1.44 \times 10^{10} = C(240 \times 10^6) \quad C = 60$$

$$V_o(s) = \frac{90}{s} - \frac{150}{s + 8000} + \frac{60}{s + 20000}$$

$$v_o(t) = [90 - 150e^{-8000t} + 60e^{-20000t}] u(t)$$

Q-2

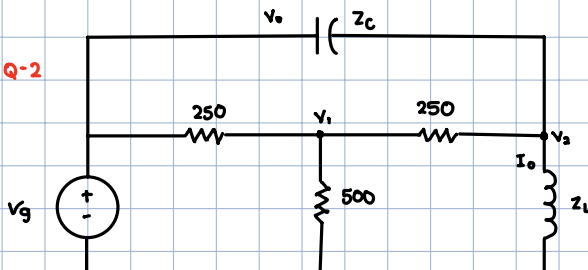

$$V_g(s) = 325/s$$

$$Z_C = \frac{1}{sC} = \frac{1}{s(800 \times 10^{-9})} = \frac{1.25 \times 10^6}{s}$$

$$Z_L = sL = s(625 \times 10^{-3}) = 0.625s$$

$$\text{NODE } V_1: \frac{V_1 - V_g}{250} + \frac{V_1}{500} + \frac{V_1 - V_2}{250} = 0$$

$$V_1 \left[ \frac{1}{250} + \frac{1}{500} + \frac{1}{250} \right] = \frac{V_g}{250} + \frac{V_2}{250}$$

$$V_1 \left( \frac{1}{100} \right) = \frac{325/s}{250} + \frac{V_2}{250}$$

$$V_1 = (1.3/s + V_2/250) 100$$

$$= 130/s + 0.4V_2$$

$$(a) V_o = V_g - V_2 = \frac{325}{s} - \frac{325}{s + 1000}$$

$$= \frac{325 \times 10^3}{s(s + 1000)}$$

$$I_o = V_2 / 0.625s$$

$$= \frac{325}{0.625s(s + 1000)} = \frac{520}{s(s + 1000)}$$

$$\text{NODE } V_2: \frac{V_2 - V_g}{Z_C} + \frac{V_2 - V_1}{250} + \frac{V_2}{Z_L} = 0$$

$$V_2 \left[ \frac{1}{Z_C} + \frac{1}{250} + \frac{1}{Z_L} \right] - \frac{V_1}{250} = \frac{V_g}{Z_C}$$

$$V_2 \left[ \frac{1}{\frac{1.25 \times 10^6}{s}} + \frac{1}{250} + \frac{1}{0.625s} \right] - \frac{V_1}{250} = \frac{325/s}{\frac{1.25 \times 10^6}{s}}$$

$$V_2 \left[ \frac{s}{1.25 \times 10^6} + \frac{1}{250} + \frac{1}{0.625s} \right] - \frac{130/s + 0.4V_2}{250} = \frac{2.6 \times 10^{-4}}{s}$$

$$V_2 \left[ \frac{s}{1.25 \times 10^6} + \frac{1}{250} + \frac{1}{0.625s} - \frac{1}{625} \right] = 2.6 \times 10^{-4} + 0.52/s$$

$$V_2 \left[ \frac{s}{1.25 \times 10^6} + \frac{1}{0.625s} + \frac{3}{1250} \right] = 2.6 \times 10^{-4} + 0.52/s$$

$$V_2 \left[ \frac{781.25s^2 + 1.5625 \times 10^9 + 2343750s}{(1.25 \times 10^6)(781.25s)} \right] = 2.6 \times 10^{-4} + 0.52/s$$

$$V_2 \left[ \frac{s^2 + 3000s + 2 \times 10^6}{1.25 \times 10^6 s} \right] = 2.6 \times 10^{-4} + 0.52/s$$

$$V_2 = \frac{325s + 0.65 \times 10^6}{s^2 + 3000s + 2 \times 10^6} = \frac{325}{s + 1000}$$

$$(b) V_o = \frac{325 \times 10^3}{s(s+1000)} = \frac{A}{s} + \frac{B}{s+1000}$$

$$325 \times 10^3 = A(s+1000) + B(s)$$

$$s=0: 325 \times 10^3 = A(1000) \quad A = 325$$

$$s=-1000: 325 \times 10^3 = B(-1000) \quad B = -325$$

$$V_o = \frac{325}{s} - \frac{325}{s+1000}$$

$$V_o = 325 (1 - e^{-1000t}) u(t) \text{ V}$$

$$I_o = \frac{520}{s(s+1000)} = \frac{A}{s} + \frac{B}{s+1000}$$

$$520 = A(s+1000) + B(s)$$

$$s=0: 520 = A(1000) \quad A = 0.52$$

$$s=-1000: 520 = B(-1000) \quad B = -0.52$$

$$I_o = \frac{0.52}{s} - \frac{0.52}{s+1000}$$

$$i_o = 0.52 (1 - e^{-1000t}) u(t) \text{ A}$$

Q-3

$$H(s) = \frac{s(s+100)(s+1000)}{(s+10)(s+10000)}$$

$$H(s) = \frac{s \left( \frac{s}{100} + 1 \right) \left( \frac{s}{1000} + 1 \right) \times 10^5}{\left( \frac{s}{10} + 1 \right) \left( \frac{s}{10000} + 1 \right) \times 10^5}$$

$$= \frac{s \left( 1 + \frac{s}{100} \right) \left( 1 + \frac{s}{1000} \right)}{\left( 1 + \frac{s}{10} \right) \left( 1 + \frac{s}{10000} \right)}$$

$$\omega_1 = \frac{1}{1/10} = 10 \text{ rad/sec}$$


$$\omega_2 = \frac{1}{1/100} = 100 \text{ rad/sec}$$

$$\omega_3 = \frac{1}{1/1000} = 1000 \text{ rad/sec}$$


$$\omega_4 = \frac{1}{1/10000} = 10000 \text{ rad/sec}$$

starting magnitude:  $20 \log(K) + 20 \log(0.1)$

Magnitude plot:

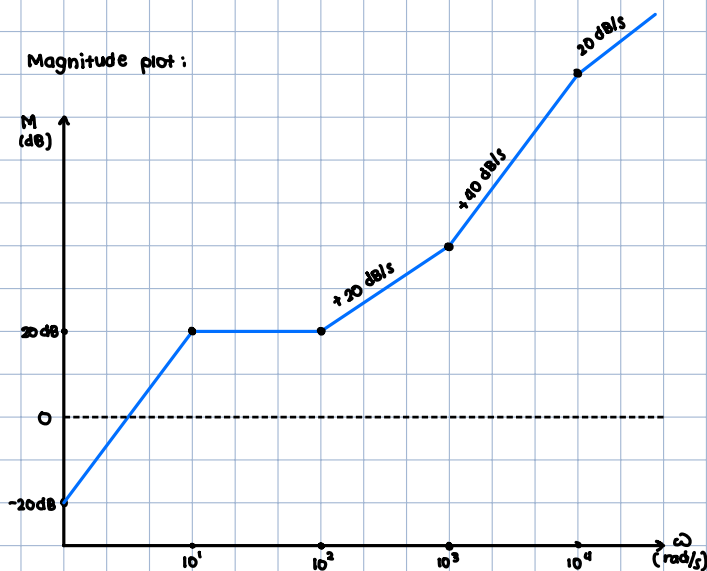

Phase plot:

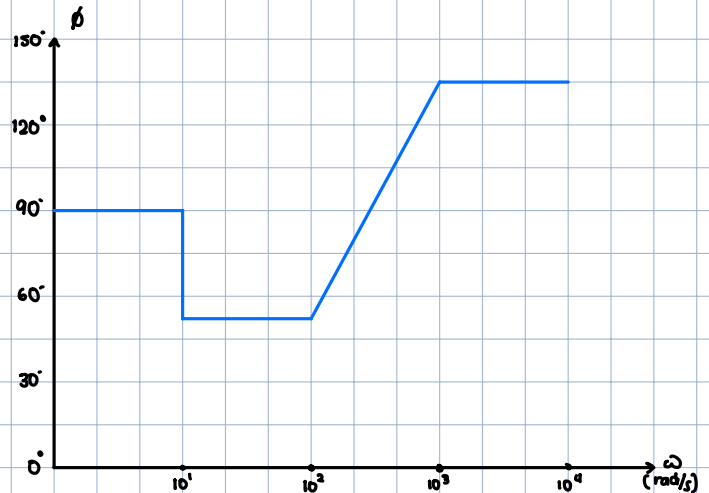


Q-4

$$H(s) = \frac{(s+3)}{(s+30)(s+300)}$$


$$= \frac{(1 + s/3)}{(1 + s/30)(1 + s/300)} \cdot \frac{1}{3000}$$

$$\text{starting point: } 20 \log(1) - 20 \log(3000) = -69.54$$

Magnitude plot:

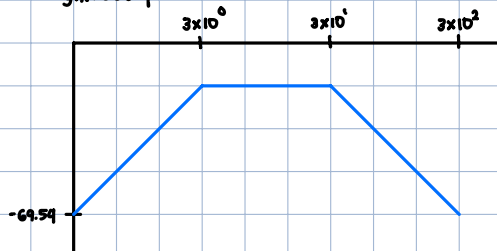

phase plot:

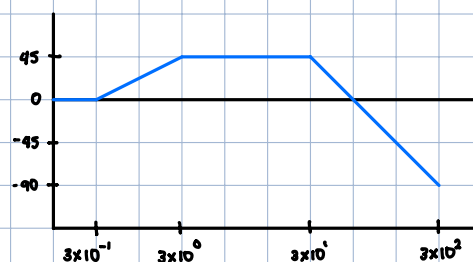


Q-5

$$H(s) = \frac{(s+1)(s+10)}{s(s+10)^2}$$

$$= \frac{(s+1)}{s(s+10)} = \frac{(s+1)}{s(\frac{s}{10}+1)} \cdot \frac{1}{10}$$

Magnitude plot :

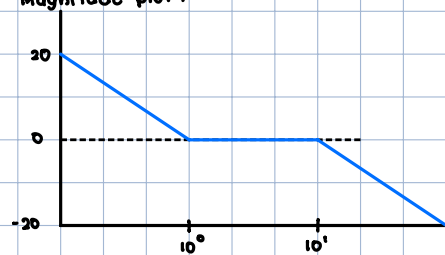

Phase plot :

