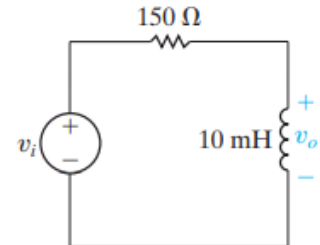


## Solution of Homework-05      ENGR 117

### 5 Questions    20 points each

**Q-1** Consider the circuit shown below.



- a) This circuit behaves like what type of filter?
- b) What is the transfer function, of this filter?
- c) What is the cutoff frequency of this filter?
- d) Find the magnitude and phase of the transfer function at  $s=j\omega_c$ ?

[a] For  $\omega = 0$ , the inductor behaves as a short circuit, so  $V_o = 0$ .  
For  $\omega = \infty$ , the inductor behaves as an open circuit, so  $V_o = V_i$ .  
Thus, the circuit is a high-pass filter.

$$[b] \ H(s) = \frac{sL}{R + sL} = \frac{s}{s + R/L} = \frac{s}{s + 15,000}$$


$$[c] \ \omega_c = \frac{R}{L} = 15,000 \text{ rad/s}$$

$$[d] \ |H(jR/L)| = \left| \frac{jR/L}{jR/L + R/L} \right| = \left| \frac{j}{j + 1} \right| = \frac{1}{\sqrt{2}}$$

$$\Theta = 90 - 45 = +45 \text{ degree}$$

**Q-2** For the bandpass filter shown. Find:

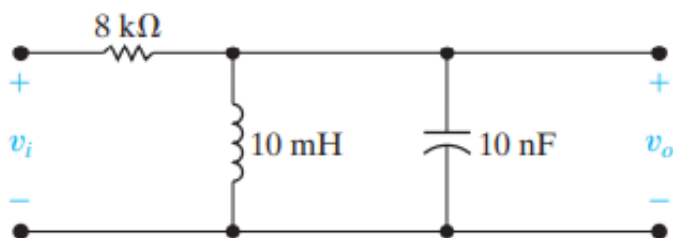(a)  $\omega_o$ , (b)  $f_o$ , (c)  $Q$ , (d)  $\omega_{c1}$ , (e)  $f_{c1}$ , (f)  $\omega_{c2}$ , (g)  $f_{c2}$ , and (h)  $\beta$ .



$$[a] \quad \omega_o^2 = \frac{1}{LC} = \frac{1}{(10 \times 10^{-3})(10 \times 10^{-9})} = 10^{10}$$

$$\omega_o = 10^5 \text{ rad/s} = 100 \text{ krad/s}$$

$$[b] \quad f_o = \frac{\omega_o}{2\pi} = \frac{10^5}{2\pi} = 15.9 \text{ kHz}$$

$$[c] \quad Q = \omega_o RC = (100 \times 10^3)(8000)(10 \times 10^{-9}) = 8$$

$$[d] \quad \omega_{c1} = \omega_o \left[ -\frac{1}{2Q} + \sqrt{1 + \left( \frac{1}{2Q} \right)^2} \right] = 10^5 \left[ -\frac{1}{16} + \sqrt{1 + \frac{1}{256}} \right] = 93.95 \text{ krad/s}$$

$$[e] \quad \therefore f_{c1} = \frac{\omega_{c1}}{2\pi} = 14.95 \text{ kHz}$$

$$[f] \quad \omega_{c2} = \omega_o \left[ \frac{1}{2Q} + \sqrt{1 + \left( \frac{1}{2Q} \right)^2} \right] = 10^5 \left[ \frac{1}{16} + \sqrt{1 + \frac{1}{256}} \right] = 106.45 \text{ krad/s}$$


$$[g] \quad \therefore f_{c2} = \frac{\omega_{c2}}{2\pi} = 16.94 \text{ kHz}$$

$$[h] \quad \beta = \frac{\omega_o}{Q} = \frac{10^5}{8} = 12.5 \text{ krad/s or } 1.99 \text{ kHz}$$

**Q-3** Verify the following for the bandpass filter: (show your work)

$$\omega_{c1} = \frac{-R}{2L} + \sqrt{\left(\frac{R}{2L}\right)^2 + \frac{1}{LC}}$$
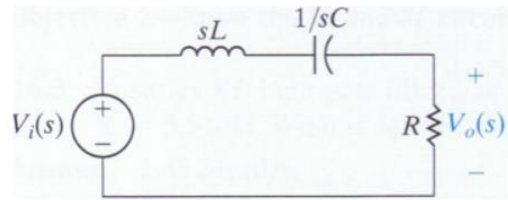
$$\omega_{c2} = \frac{+R}{2L} + \sqrt{\left(\frac{R}{2L}\right)^2 + \frac{1}{LC}}$$



At Corner frequency

$$|H(j\omega)| = \frac{\frac{R}{L} \omega}{\sqrt{\left(\frac{1}{LC} - \omega^2\right)^2 + \left(\frac{R}{L} \omega\right)^2}} = \frac{1}{\sqrt{2}} \Rightarrow$$

$$2 \left(\frac{R}{L} \omega\right)^2 = \left(\frac{1}{LC} - \omega^2\right)^2 + \left(\frac{R}{L} \omega\right)^2$$

$$\left(\frac{R}{L} \omega\right)^2 = \left(\frac{1}{LC} - \omega^2\right)^2$$

$$\pm \left(\frac{R}{L} \omega\right) = \pm \left(\frac{1}{LC} - \omega^2\right) \Rightarrow \text{This gives 4 combinations}$$

$$\omega^2 + \frac{R}{L} \omega - \frac{1}{LC} = 0$$

$$\omega^2 - \frac{R}{L} \omega - \frac{1}{LC} = 0$$

$$\omega^2 - \frac{R}{L} \omega - \frac{1}{LC} = 0$$

$$\omega^2 + \frac{R}{L} \omega - \frac{1}{LC} = 0$$

These 4 reduce to 2 equations.

$$\omega^2 + \frac{R}{L} \omega - \frac{1}{LC} = 0 \quad \text{--- (1)}$$

$$\omega_1 = \frac{-\frac{R}{L}}{2} + \sqrt{\left(\frac{R}{2L}\right)^2 + \frac{1}{LC}} \quad \leftarrow +ve$$

$$\omega_2 = \frac{-\frac{R}{L}}{2} - \sqrt{\left(\frac{R}{2L}\right)^2 + \frac{1}{LC}} \quad \leftarrow -ve \quad \leftarrow \text{ignore}$$

$$\omega^2 - \frac{R}{L} \omega - \frac{1}{LC} = 0 \quad \text{--- (2)}$$

$$\omega_1 = \frac{+\frac{R}{L}}{2} + \sqrt{\left(\frac{R}{2L}\right)^2 + \frac{1}{LC}} \quad \leftarrow +ve$$

$$\omega_2 = \frac{+\frac{R}{L}}{2} - \sqrt{\left(\frac{R}{2L}\right)^2 + \frac{1}{LC}} \quad \leftarrow -ve \quad \leftarrow \text{ignore}$$

So

$$\omega_{c1} = \frac{-R}{2L} + \sqrt{\left(\frac{R}{2L}\right)^2 + \frac{1}{LC}}$$

$$\omega_{c2} = \frac{+R}{2L} + \sqrt{\left(\frac{R}{2L}\right)^2 + \frac{1}{LC}}$$

Proved

**Q-4** Use a 5 nF capacitor to design a series RLC bandpass filter. The center frequency of the filter is 8 kHz, and the quality factor is 2. (Show your circuit)

- a) Specify the values of R and L.
- b) What is the lower cutoff frequency in kilohertz?
- c) What is the upper cutoff frequency in kilohertz?
- d) What is the bandwidth of the filter in kilohertz?

$$[a] \quad \omega_o^2 = \frac{1}{LC} \quad \text{so} \quad L = \frac{1}{[8000(2\pi)]^2(5 \times 10^{-9})} = 79.16 \text{ mH}$$

$$R = \frac{\omega_o L}{Q} = \frac{8000(2\pi)(79.16 \times 10^{-3})}{2} = 1.99 \text{ k}\Omega$$

$$[b] \quad f_{c1} = 8000 \left[ -\frac{1}{4} + \sqrt{1 + \frac{1}{16}} \right] = 6.25 \text{ kHz}$$

$$[c] \quad f_{c2} = 8000 \left[ \frac{1}{4} + \sqrt{1 + \frac{1}{16}} \right] = 10.25 \text{ kHz}$$

$$[d] \quad \beta = f_{c2} - f_{c1} = 4 \text{ kHz}$$

or

$$\beta = \frac{f_o}{Q} = \frac{8000}{2} = 4 \text{ kHz}$$

**Q-5** Design the component values for the series RLC band reject filter so that the center frequency is 4 kHz and the quality factor is 500. Use a 500 nF capacitor. (Show your circuit)

a) Find the values of R and L.

$$\omega_o = 8000\pi \text{ rad/s}$$

$$C = 500 \text{ nF}$$

$$\omega_o^2 = \frac{1}{LC} \quad \text{so} \quad L = \frac{1}{\omega_o^2 C} = 3.17 \text{ mH}$$

$$Q = \frac{\omega_o}{\beta} = \frac{\omega_o L}{R} = \frac{1}{\omega_o C R}$$

$$\therefore R = \frac{1}{\omega_o C Q} = \frac{1}{(8000\pi)(500)(5 \times 10^{-9})} = 15.92 \Omega$$

[a]    R=15.92  $\Omega$             L= 3.17 mH