

P2.10. 10ed

Given that $v_o = 5$ Volts.

Find the total power developed in the circuit. $P_{\text{developed}} = 77$ W

+ = absorbed and -* = delivered

Answer:

$$\begin{aligned} P_{del} : P_{10Vq} &= -(10V_q) i_2 \\ &= -(5V)(15A) = -75W \\ P_{9A} &= -V_{9A}(9A) \\ &= -(15V)(9A) = -135W \\ &\quad \underline{\quad \quad \quad} \\ &\quad \quad \quad -210W \end{aligned}$$

The circuit's interconnection invalid.

P2.05b_6ed

What is the power delivered in this circuit?

$P_{\text{delivered}} =$ ☒ W

What is the power absorbed in this circuit?

$P_{\text{absorbed}} =$ ☒ W

$$P_{abs} : P_{30V} (8A)(30V) = 240 W$$

Copyright © 2011 Pearson Education, Inc. publishing as Prentice Hall

P2.02_9ed

Is the circuit's interconnection valid? yes or no?

Answer: no

the circuit interconnection is invalid


C4

A resistor is a passive circuit element. Resistors can only (absorb/deliver) power.

Fill in the blank with your answer.

Answer: absorb

6

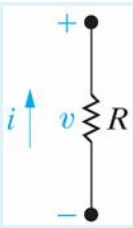

$$v = 51 \text{ V} \quad i = -5 \text{ A}$$

$$v = -iR$$


$$R = -v/i = -51/(-5) = 10.2 \, \Omega$$

CQ2.02

Given: $v = 51$ Volts $i = -5$ AmpsFind the unknown resistance R . $R = ?? \, \Omega$ Ohms

Answer: 10.2 ✓

7

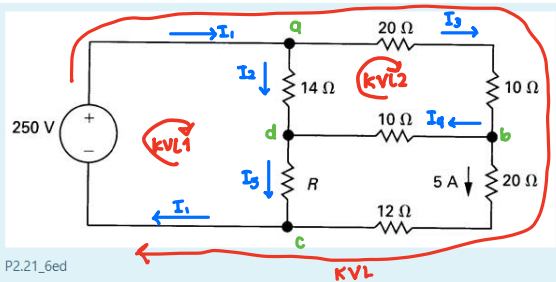

P2.21_6ed

a) Find the value of the unknown resistor R $R = 60 \, \Omega$ (Ohm) ✓

b) Find the power absorbed/delivered by the 250V source.

 $P_{250V} = -2000 \text{ W}$ ✓ $-$ = Delivering $+$ = Absorbing

$$\text{KVL: } -250 \text{ V} + 20I_2 + 10I_3 + 20(5) + 12(5) = 0$$

$$I_3 = 3 \text{ A}$$

$$\text{Node b: } -I_2 + I_4 + 5 \text{ A} = 0$$

$$I_4 = 3 \text{ A} - 5 \text{ A} = -2 \text{ A}$$

$$\text{Node a: } -I_1 + I_2 + I_3 = 0 \rightarrow I_2 = I_1 - I_3$$

$$\text{Node c: } -5 \text{ A} - I_5 + I_1 = 0 \rightarrow I_5 = -5 \text{ A} + I_1$$

$$I_2 = 8 \text{ A} - 3 \text{ A} = 5 \text{ A}$$


$$I_5 = -5 \text{ A} + 8 \text{ A} = 3 \text{ A}$$

$$\begin{aligned} \text{KVL2: } -14I_2 + 20I_3 + 10I_4 &= 0 \\ -14(I_1 - I_3) + 30(3) + 10(-2) &= 0 \\ -14I_1 + 14(3) + 90 - 20 &= 0 \\ I_1 &= 8 \text{ A} \end{aligned}$$

$$\begin{aligned} \text{KVL1: } -250 \text{ V} + 14I_2 + RI_5 &= 0 \\ -250 \text{ V} + 14(5) + R(3) &= 0 \\ R &= 60 \, \Omega \end{aligned}$$

$$P_{250V} = -(250)(8) = -2000 \text{ W}$$

8

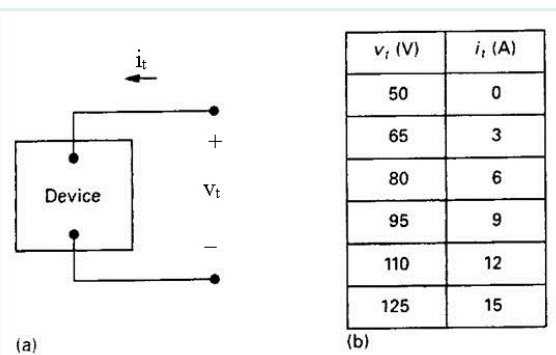

P2.18_6ed

The voltage and current were measured at the terminals of the device as shown in the table (b).

What is the value of the current source and resistor known to make up the device?

Current Source = 10 A ✓


Resistor = 5 Ω (Ohm) ✓

$$V = iR$$

$$R = \frac{v}{i} = \frac{65-50}{3-0} = 5 \, \Omega$$

$$I = \frac{v}{R} = \frac{50}{5} = 10 \text{ A}$$

9

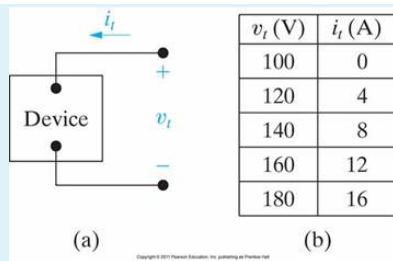

P2.14_9ed

The voltage and current were measured at the terminals of the device as shown in the table (b). What is the value of the current source and resistor known to make up the device?

Current Source $i = 20$ A


Resistor $R = 5$ Ω (Ohm)

$$V = iR$$

$$R = V/i = \frac{120-100}{4-0} = 5 \Omega$$

$$I = V/R = 100/5 = 20 A$$

10

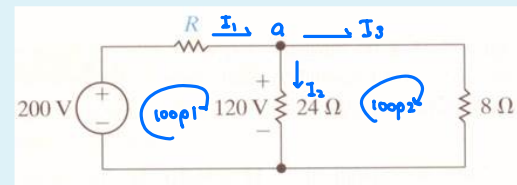

AP2.06_9ed

Use Ohm's Law and Kirchhoff's laws to find the value of R in this circuit. $R = ?? \Omega$ (Ohm)

Answer: 4

$$V = iR$$

$$I_2 = 120V/24\Omega = 5A$$

$$KVL2: -120V + 8I_3 = 0$$

$$I_3 = 15A$$

$$\text{Node } q: I_1 = I_2 + I_3$$


$$= 5A + 15A$$

$$= 20A$$


$$KVL1: -200V + RI_1 + 120V = 0$$

$$20R = 80$$

$$R = 4 \Omega$$

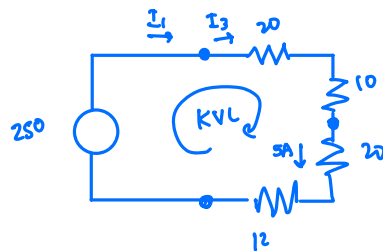
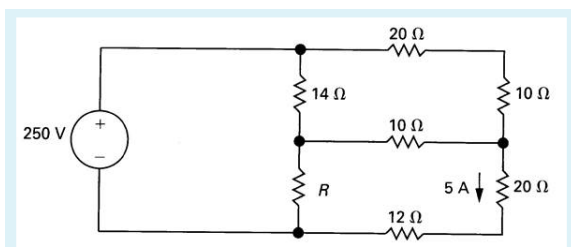
$$KVL: -250V + 20I_3 + 10I_2 + 20(5) + 12(5) = 0$$



P2.21_6ed

a) Find the value of the unknown resistor R

$R = 60$ Ω (Ohm)

b) Find the power absorbed/delivered by the 250V source.

$P_{250V} = -2000$ W "- " = Delivering "+ " = Absorbing