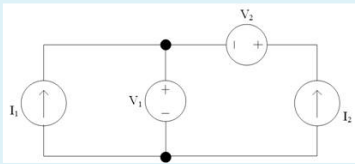


QUIZ 02




Quiz 2-1

Given: $I_1 = 13$ Amps $V_1 = 227$ Volts $I_2 = 2$ Amps $V_2 = 67$ Volts

What is the current through the voltage source V_1 ?

Answer: ✓

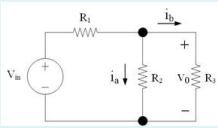

Quiz 2-2b

Given: $V_m = 60$ Volts

$R_1 = 4 \Omega$ (Ohm) $R_2 = 20 \Omega$ (Ohm) $R_3 = 80 \Omega$ (Ohm)

a) Find the value of i_R . $i_R =$ ✓ A

b) Find the value of v_0 . $v_0 =$ ✓ V

c) Find the power dissipated in each resistor.


$P_{R1} =$ ✓ W $P_{R2} =$ ✓ W $P_{R3} =$ ✓ W

d) Find the power delivered by the V_m source.

$P_{V_m} =$ ✓ W

Remember: "-" = Delivering "+" = Absorbing

QUIZ 03

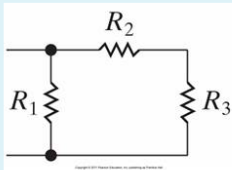


Quiz 3 - Q1f

Given: $R_1 = 1 \text{ k}\Omega$ (Ohms) $R_2 = 60 \Omega$ (Ohms) $R_3 = 190 \Omega$ (Ohms)

Find the equivalent resistance R_{Eq} .

$R_{Eq} =$ ✓ Ω (Ohms)

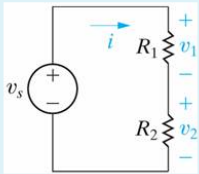


Quiz 3 - Q2e

Given: $v_s = 60$ Volts $R_1 = 450 \Omega$ (Ohms) $R_2 = 800 \Omega$ (Ohms)

a) Find the voltage v_1 . $v_1 =$ ✓ Volts

b) Find the voltage v_2 . $v_2 =$ ✓ Volts

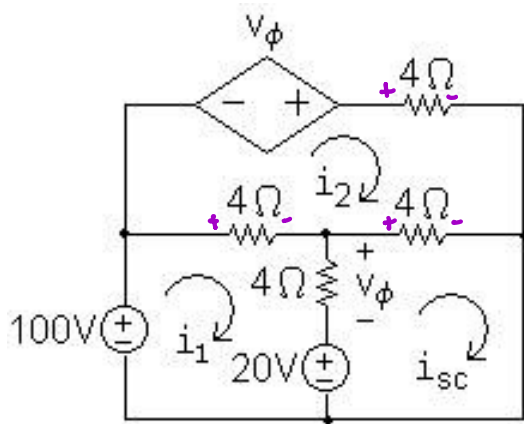c) Find the current i . $i =$ ✓ mA (milli Amp)



$$100 - 4(i_1 - i_2) - 4(i_1 - i_{sc}) - 20 = 0$$

$$-8i_1 + 4i_2 + 4i_{sc} + 80 = 0 \quad (1)$$

$$20 + 4(i_1 - i_{sc}) - 4(i_{sc} - i_2) = 0$$

$$4i_1 + 4i_2 - 8i_{sc} + 20 = 0 \quad (2)$$

$$V_\phi = 4(i_1 - i_{sc})$$

$$V_\phi - 4i_2 + 4(i_{sc} - i_2) + 4(i_1 - i_2) = 0$$

$$4(i_1 - i_{sc}) - 4i_2 + 4(i_{sc} - i_2) + 4(i_1 - i_2) = 0$$

$$8i_1 - 12i_2 = 0 \quad (3)$$


$$\begin{cases} -8i_1 + 4i_2 + 4i_{sc} = -80 \\ 4i_1 + 4i_2 - 8i_{sc} = -20 \\ 8i_1 - 12i_2 = 0 \end{cases} \quad \begin{cases} i_1 = 45 \text{ A} \\ i_2 = 30 \text{ A} \\ i_{sc} = 40 \text{ A} \end{cases}$$

$$P_{V_\phi} = i_2 V_\phi = i_2 [4(i_1 - i_{sc})]$$

$$= (30)[4(45 - 40)]$$

$$= 600 \text{ (-)}$$

Quiz 07

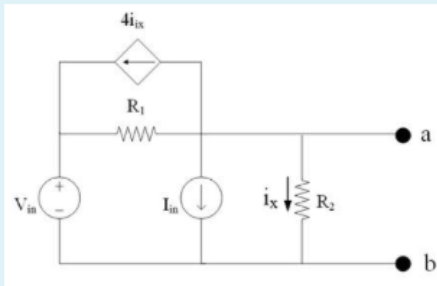

Quiz 7a

Given: $V_{in} = 20 \text{ V}$ $I_{in} = 4 \text{ A}$ $R_1 = 2 \text{ } \Omega$ (Ohms) $R_2 = 6 \text{ } \Omega$ (Ohms)

Find the Thévenin equivalent circuit with respect to the terminals ab.

$$V_{Th} = 4.5 \text{ V}$$

$$R_{Th} = 0.75 \text{ } \Omega \text{ (Ohms)}$$

$$\text{NODE } V_A: \frac{20 - V_A}{2} - 4 - 4i_x - i_n = 0$$

$$\text{NODE } V_B: i_n = \frac{V_B}{6} + i_x$$

$$20 - V_A - 8 - 8i_x - 2i_n = 0$$



$$12 - V_A - 8(V_B/6) - 2(V_B/6) = 0$$

$$72 - 6V_A - 8V_B - 2V_B = 0 \quad V_A = V_B$$

$$72 - 6V_A - 10V_A = 0$$

$$16V_A = 72$$

$$V_A = 4.5 = V_{Th}$$

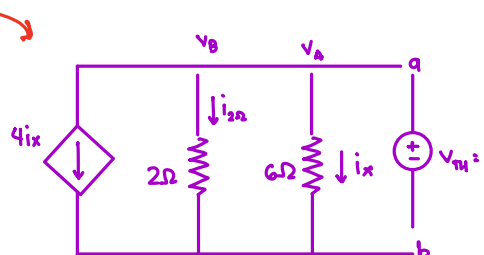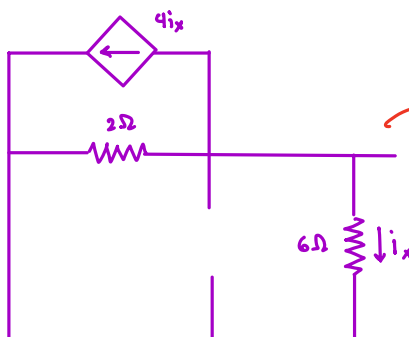

$$\frac{V}{I} = R_{Th}$$

$$\frac{1}{I} = R_{Th}$$

$$R_{Th} = \frac{V}{I} = \frac{1}{4/3} = \frac{3}{4}$$

$$= 0.75 \Omega$$

$$V_{Th} = V_A = V_B$$


$$i_x = \frac{V_{Th}}{6\Omega} = \frac{1}{6}$$

$$4i_x = 4(V_B) = 2/3$$

$$i_{2\Omega} = \frac{V_{Th}}{2\Omega} = \frac{1}{2}$$

$$I = \frac{2}{3} + \frac{1}{6} + \frac{1}{2} = \frac{4}{3}$$

QUIZ 08

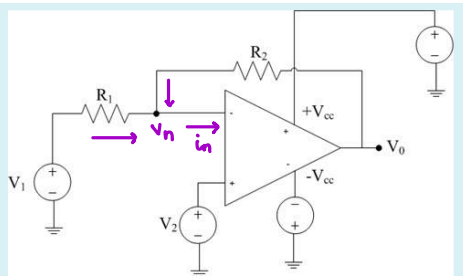

Quiz 8f

You may assume the opamp is ideal.

Given: $V_1 = -2.0$ Volts $V_2 = 1.0$ Volts
 $R_1 = 6,000$ W (Ohm) $R_2 = 14,000$ W (Ohm)

The power supplies voltages are $+V_{cc} = 15$ Volts $-V_{cc} = -15$ Volts

Using the linear region opamp equations, find the voltage V_0 .

$V_0 = 8$ ✓

Is the opamp operating in the linear region?

Yes ✓

Now use all of the ideal opamp assumptions and state the output voltage.

$V_0 = 8$ ✓ Volts

$$\text{NODE } V_n: \frac{V_n - V_1}{R_1} + \frac{V_n - V_o}{R_2} - i_n = 0$$

$$\left[\frac{1.0 + 2.0}{6000} + \frac{1.0 - V_o}{14000} = 0 \right] 42000$$

$$(3.0)(7) + 3(1.0) - 3V_o = 0$$

$$V_o = 8 \text{ V}$$

$$i_n = 0$$

$$V_n = V_2 = 1.0 \text{ V}$$

QUIZ 09

Quiz 9g

A circuit has the following measured voltage and current at the input terminals.

$$v(t) = 12 \sin(250t + 15^\circ) \text{ V}$$

$$i(t) = 15 \sin(250t - 15^\circ) \text{ A}$$

a) What is the frequency ω (Omega) in radians of the time varying input?

$\omega = 250$ ✓ rad/sec

b) What is the frequency f in Hertz of the time varying input?

$f = 39.79$ ✓ Hz

c) What is the period T in ms (milli sec) of the time varying input?

$T = 25.13$ ✓ ms (milli sec)

d) What is the phase angle Φ_v in radians of the terminal voltage in the cosine convention?

$\Phi_v = 0.2618$ ✗ rad

e) What is the phase angle Φ_i in radians of the terminal current in the cosine convention?

$\Phi_i = -1.833$ ✓ rad

f) What is the rms voltage value of the terminal voltage?

$V_{rms} = 8.485$ ✓ V_{rms}

g) What is the rms current value of the terminal current?

$I_{rms} = 10.61$ ✓ A_{rms}

$$v(t) = V_m \cos(\omega t + \phi)$$

$$i(t) = I_m \sin(\omega t + \phi)$$

$$(a) \omega = 250 \text{ rad/s}$$

$$(b) f = \omega/2\pi = 250/2\pi = 39.79 \text{ Hz}$$

$$(c) T = 2\pi/\omega = 2\pi/250 = 0.02513 \approx 25.13 \text{ ms}$$

$$(d) \Phi_v = 15^\circ \approx 0.2618 \text{ rad}$$

$$(e) i(t) = 15 \sin(250t - 15^\circ)$$

$$\cos(90^\circ - \theta) = \sin \theta$$

$$i(t) = 15 \cos[90^\circ - (250t - 15^\circ)]$$

$$= 15 \cos(-250t + 105^\circ)$$

$$= 15 \cos[-(250t - 105^\circ)]$$


$$\cos(-t) = \cos t$$

$$= 15 \cos(250t - 105^\circ)$$

$$\Phi_i = -105^\circ \approx -1.833 \text{ rad}$$

$$(f) V_{rms} = \frac{V_m}{\sqrt{2}} = \frac{12}{\sqrt{2}} = 8.485$$
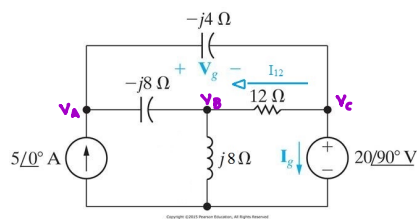
$$(g) I_{rms} = \frac{I_m}{\sqrt{2}} = \frac{15}{\sqrt{2}} = 10.61$$



$$5\angle 0^\circ \rightarrow 5 + j0$$

$$20\angle 90^\circ \rightarrow 0 + j20$$

$$\text{NODE } V_A: -5 + \frac{V_A - V_C}{-j4} + \frac{V_A - V_B}{-j8} = 0$$

$$\text{NODE } V_B: \frac{V_B - V_A}{-j8} + \frac{V_B}{j8} + \frac{V_B - V_C}{12} = 0$$

$$\left[-5 + \frac{V_A - V_C}{-j4} + \frac{V_A - V_B}{-j8} = 0 \right] -j8$$

$$j40 + 2V_A - 2V_C + V_A - V_B = 0$$

$$j40 + 3V_A - 2(j20) - V_B = 0$$

$$3V_A - V_B = 0$$

$$3V_A = V_B$$

$$V_A = V_B/3$$

$$\left[\frac{V_B - V_A}{-j8} + \frac{V_B}{j8} + \frac{V_B - (j20)}{12} = 0 \right] j24$$

$$-3V_B + 3V_A + 3V_B + j2V_B - j40 = 0$$

$$3V_A + j2V_B + 40 = 0$$

$$3(V_B/3) + j2V_B + 40 = 0$$


$$V_B + j2V_B + 40 = 0$$

$$V_B(1 + j2) = -40$$

$$V_B = \frac{-40}{1 + j2} \cdot \frac{1 - j2}{1 - j2} = \frac{-40(1 - j2)}{1 + 4} = -8 + j16$$

$$I_{12} = \frac{V_C - V_B}{12} = \frac{j20 - (-8 + j16)}{12} = \frac{8 + j4}{12} = \frac{2}{3} + j\frac{1}{3} \approx 0.667 + j0.333$$

QUIZ 11

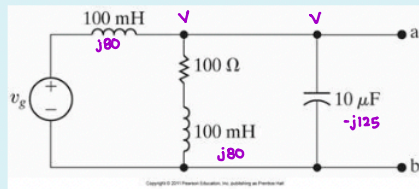

Quiz 11b

The sinusoidal voltage source in the circuit is developing a voltage equal to $200 \cos(800t + 45^\circ)$ V_{rms}.

a) Find the Thévenin voltage with respect to the terminals a,b.

Express your answer in polar form.

Magnitude $|V_{Th}| = 221.139$ ✗ V

Angle = 12.03 ✓ ° (Degrees)

b) Find the Thévenin impedance with respect to the terminals a,b.

Express your answer in polar form.

Magnitude $|Z_{ab}| = 88.46$ ✓ Ω (Ohm)

Angle = 57.03 ✓ ° (Degrees)

$$Z_L = j\omega L = j(800)(100 \times 10^{-3}) = j80$$

$$Z_C = \frac{-j}{\omega C} = \frac{-j}{(800)(10 \times 10^{-6})} = -j125$$

$$V_g = 200 \angle 45^\circ \approx 100\sqrt{2} + j100\sqrt{2}$$

$$\text{NODE } V: \left[\frac{V - V_g}{j80} + \frac{V}{100 + j80} + \frac{V}{-j125} = 0 \right] j80$$

$$V \left[1 + \frac{j8}{10 + j8} - 0.64 \right] = V_g$$

$$V \left[\frac{j8}{10 + j8} + 0.36 \right] = V_g$$

$$V \left[\frac{j8 + 3.6 + j2.88}{10 + j8} \right] = 100\sqrt{2} + j100\sqrt{2}$$

$$V = \frac{(100\sqrt{2} + j100\sqrt{2})(10 + j8)}{(3.6 + j10.88)}$$

$$= \frac{(200 \angle 45^\circ)(2\sqrt{41} \angle 38.66^\circ)}{(11.46 \angle 71.69^\circ)}$$

$$V_{Th} = 223.50 \angle 11.97^\circ$$

$$\begin{aligned} 100 + j80 \parallel -j125 &= \frac{(100 + j80)(-j125)}{100 + j80 - j125} = \frac{(20\sqrt{41} \angle 38.66^\circ)(125 \angle -90^\circ)}{5\sqrt{41} \angle -24.23^\circ} \\ &= 145.98 \angle -27.11^\circ \approx 129.94 - j66.52 \end{aligned}$$

$$\begin{aligned} V_{Th} &= \frac{(145.98 \angle -27.11^\circ) V_g}{129.94 - j66.52 + j80} \\ &= \frac{(145.98 \angle -27.11^\circ)(200 \angle 45^\circ)}{130.64 \angle 5.92^\circ} \\ &= 223.48 \angle 11.97^\circ \end{aligned}$$

$$\begin{aligned} Z_{Th} &= 145.98 \angle -27.11^\circ \parallel j80 \\ &= \frac{(145.98 \angle -27.11^\circ)(80 \angle 90^\circ)}{129.94 - j66.52 + j80} \\ &= \frac{(145.98 \angle -27.11^\circ)(80 \angle 90^\circ)}{130.64 \angle 5.92^\circ} \\ &= 89.40 \angle 68.81^\circ \end{aligned}$$

QUIZ 10

$$V = 250 \angle 0^\circ \approx 250$$

$$\frac{V_L - V}{1 + j4} + \frac{V_L}{-j100} + \frac{V_L}{26 + j39} = 0$$

$$V_L \left[\frac{1}{1 + j4} - \frac{1}{j100} + \frac{1}{26 + j39} \right] = \frac{V}{1 + j4}$$

$$V_L \left[\frac{1 - j4}{17} - \frac{-j100}{10K} + \frac{26 - j39}{2197} \right] = \frac{V}{1 + j4}$$

$$\left[V_L \left(\frac{1 - j4}{17} + \frac{j}{100} + \frac{26 - j39}{169} \right) \right] = \frac{V}{1 + j4} (17)(100)(169)$$

$$V_L \left[16900(1 - j4) + 2873j + 1700(26 - j39) \right] = \frac{V(17)(100)(169)}{1 + j4}$$

$$\begin{aligned} V_L (20300 - j69827) &= \frac{V(287300)}{(1 + j4)(20300 - j69827)} = \frac{(250)(287300)}{20300 + j11373 + 279308} \\ &= \frac{71825000}{299608 + j11373} = \frac{299608 - j11373}{299608 + j11373} \cdot \frac{299608 - j11373}{299608 - j11373} \\ &= (8 \times 10^{-4}) (299608 - j11373) \\ &= 239.6864 - j9.0984 \end{aligned}$$

$$V_L = 239.6864 - j9.0984 \approx 239.86 \angle -2.17^\circ$$

$$\begin{aligned} I_L &= \frac{V_L}{26 + j39} = \frac{239.6864 - j9.0984}{26 + j39} \cdot \frac{26 - j39}{26 - j39} \\ &= \frac{6231.8464 - j9584.328 - 354.8376}{2197} = \frac{5877.0088 - j9584.328}{2197} \\ &= 2.675 - j4.36 \approx 5.11 \angle -58.47^\circ \end{aligned}$$

$$P_{avg} = \frac{239.86(5.11)}{2} \cos(-2.17^\circ - 58.47^\circ)$$

=

$$Q = -\frac{(250)(5.11)}{2} \sin(0 - 58.47)$$

$$= -544.45 \text{ W}$$

$$pf = \cos(\theta_V - \theta_I) = \cos(0 - 58.47) = 0.52$$

$$\begin{aligned} Z_L &= 1228.68 \angle -60.64 \\ &\approx 600.95 \end{aligned}$$

Given this set of equations:

$$\frac{v_0 - 10V}{10\Omega} + \frac{v_0}{40\Omega} + \frac{v_0 - (-20i_\Delta)}{20\Omega} = 0$$

$$v_0\left(-\frac{1}{10\Omega}\right) + i_\Delta\left(-\frac{1}{3}\right) = -1.333$$

Find the voltage and current.

$v_0 =$ ✓ V

$i_\Delta =$ ✓ A

