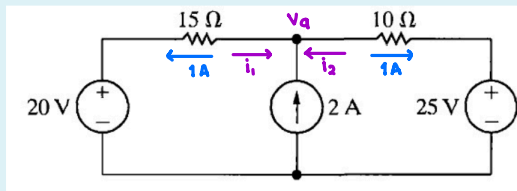


1.



AP4.13_9ed

Find the power absorbed/delivered by the 2 A current source in this circuit.

$$P_{2A} = -70 \text{ W}$$

"+" = absorbed and "-" = delivered

$$i_1 + i_2 + 2A = 0$$


$$\left[\frac{20 - v_a}{15} + \frac{25 - v_a}{10} + 2 = 0 \right] 30$$

$$40 - 2v_a + 75 - 3v_a + 60 = 0$$

$$v_a = 35 \text{ V}$$

$$P = iV = (2)(35) = 70 \text{ W (-)}$$

2.

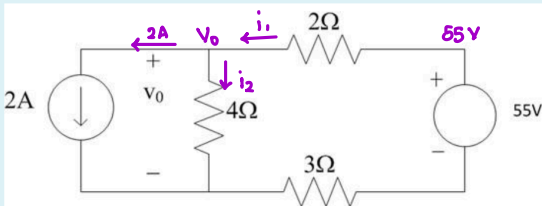

P4.02_6ed

Use the node-voltage method.

a) Find the voltage v_0 across the 2A current source in this circuit.

$$v_0 = 20 \text{ V}$$

b) Find the power absorbed/delivered by the 2A current source.

$$P_{2A} = 40 \text{ W}$$

$$i_1 - i_2 - 2A = 0$$


$$\left[\frac{55 - v_0}{2+3} - \frac{v_0}{4} = 2 \right] 20$$

$$220 - 4v_0 - 5v_0 = 40$$

$$v_0 = 20 \text{ V}$$

$$P = iV = (2)(20) = 40 \text{ W}$$

3.

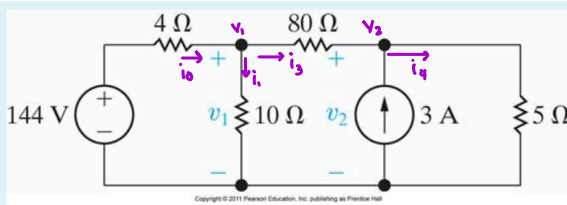

P4.06_9ed

Use the node-voltage method to find v_1 and v_2 in this circuit.

$$v_1 = 100 \text{ V}$$

$$v_2 = 20 \text{ V}$$

$$i_0 - i_1 - i_3 = 0$$

$$\left[\frac{144 - v_1}{4} - \frac{v_1}{10} - \frac{v_1 - v_2}{80} = 0 \right] 80$$

$$2880 - 20v_1 - 8v_1 - v_1 + v_2 = 0$$

$$-29v_1 + v_2 = -2880$$

$$i_3 - i_4 + 3 = 0$$

$$\left[\frac{v_1 - v_2}{80} - \frac{v_2}{5} + 3 = 0 \right] 80$$

$$v_1 - v_2 - 16v_2 = -240$$

$$v_1 - 17v_2 = -240$$


$$17 \left[-29v_1 + v_2 = -2880 \right]$$

$$-492 = -49200$$

$$v_1 = 100 \text{ V}$$

$$v_2 = 20 \text{ V}$$

4.

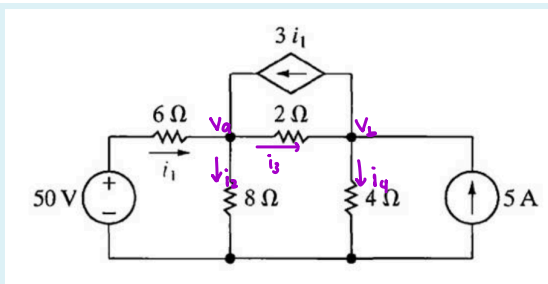

AP4.03b_9ed

Use the node-voltage method to find the power absorbed/delivered by each source in this circuit.

$$P_{50V} = -150 \text{ W}$$

$$P_{5A} = -80 \text{ W}$$

$$P_{3i_1} = -144 \text{ W (power associated with the dependent current source)}$$

"+" = absorbed and "-" = delivered

$$i_1 + 3i_1 - i_2 - i_3 = 0$$

$$4i_1 - i_2 - i_3 = 0$$

$$\left[4 \left(\frac{50 - v_a}{6} \right) - \frac{v_a}{8} - \frac{v_a - v_b}{2} = 0 \right] 24$$

$$4(200 - 4v_a) - 3v_a - 12v_a + 12v_b = 0$$

$$-31v_a + 12v_b = -800 \longrightarrow -31v_a + 12v_b = -800$$

$$-3i_1 + i_3 - i_4 + 5 = 0$$

$$\left[-\frac{50 - v_a}{2} + \frac{v_a - v_b}{2} - \frac{v_b}{4} + 5 = 0 \right] 4$$

$$-100 + 2v_a + 2v_a - 2v_b - v_b + 20 = 0$$

$$(4v_a - 3v_b = 80) \quad 4$$

$$-15v_a = -480$$

$$v_a = 32 \text{ V}$$

$$v_b = 16 \text{ V}$$


$$i_1 = \frac{50 - 32}{6} = 3 \text{ A}$$

$$P_{50V} = (3)(50) = -150 \text{ W}$$

$$P_{5A} = (5)(v_b) = (5)(16) = -80 \text{ W}$$

$$P_{3i_1} = (3i_1)(v_a - v_b) = [3(3)](32 - 16) = -144 \text{ W}$$

5.

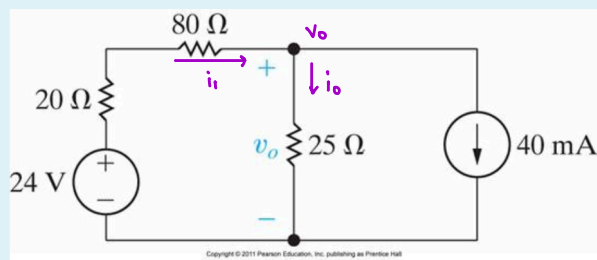

P4.09_9ed

Use the node-voltage method to find v_o in this circuit.

$$v_o = 4 \text{ V}$$


$$i_1 - i_o - 0.04 = 0$$

$$\left[\frac{24 - v_o}{100} - \frac{v_o}{25} - 0.04 = 0 \right] 100$$

$$24 - v_o - 4v_o - 4 = 0$$

$$v_o = 4 \text{ V}$$

6.

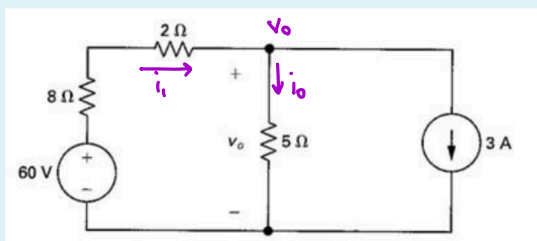

P4.05_6ed

Use the node-voltage method.

a) Find v_o in this circuit.

$$v_o = 10 \text{ V}$$

b) Find the power absorbed/delivered by the 3A current source.

$$P_{3A} = 30 \text{ W}$$

$$i_1 - i_o - 3 = 0$$


$$\left[\frac{60 - v_o}{10} - \frac{v_o}{5} - 3 = 0 \right] 10$$

$$60 - v_o - 2v_o - 30 = 0$$

$$v_o = 10 \text{ V}$$

$$P_{3A} = (3)(v_o) = (3)(10) = 30 \text{ W}$$

7.

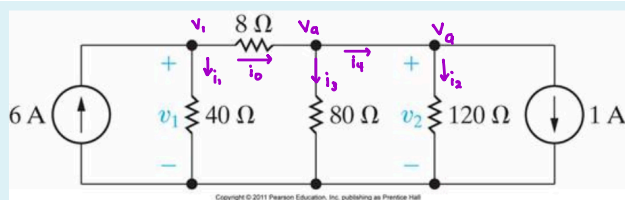

P4.08_9ed

Use the node-voltage method to find v_1 and v_2 in this circuit.

$$v_1 = 120 \text{ V}$$

$$v_2 = 96 \text{ V}$$

$$6 - i_1 - i_o = 0$$

$$\left[6 - \frac{v_1}{40} - \frac{v_1 - v_2}{8} = 0 \right] 40$$

$$240 - v_1 - 5v_1 + 5v_2 = 0$$

$$-6v_1 + 5v_2 = -240$$

$$i_o - i_3 - i_4 = 0$$

$$\left[\frac{v_1 - v_2}{8} - \frac{v_2}{80} - i_4 = 0 \right] 80$$

$$10v_1 - 10v_2 - v_2 - 80i_4 = 0$$

$$10v_1 - 11v_2 - 80 \left[\frac{v_2}{120} + 1 \right] = 0$$

$$i_4 - i_2 - 1 = 0$$

$$i_4 = \frac{v_2}{120} + 1$$

$$\left[10v_1 - 11v_2 - \frac{2}{3}v_2 - 80 = 0 \right] 3$$

$$30v_1 - 33v_2 - 2v_2 - 240 = 0$$

$$30v_1 - 35v_2 = 240$$

$$(-6v_1 + 5v_2 = -240) 5$$

$$-10v_1 + 25v_2 = -1200$$

$$v_2 = 96 \text{ V} = v_2$$

$$v_1 = 120 \text{ V}$$

$$\text{NODE } 10 \text{ V: } i_\Delta = i_1 + i_2$$

$$\left[i_\Delta = \frac{10 - 20i_\Delta}{30} + \frac{10 - v_o}{10} \right] 30$$

$$30i_\Delta = 10 - 20i_\Delta + 30 - 3v_o$$

$$50i_\Delta + 3v_o = 40$$

$$[60i_\Delta + 3v_o = 40] 4$$

$$[40i_\Delta + v_o = 40] -5$$

$$7v_o = -40$$

$$v_o = -40$$


$$\text{NODE } v_o: i_2 - i_o - i_3 = 0$$

$$\left[\frac{v_o - 10}{10} - \frac{v_o}{40} - \frac{v_o - 20i_\Delta}{20} = 0 \right] 40$$

$$4v_o - 40 - v_o - 2v_o + 40i_\Delta = 0$$

$$40i_\Delta + v_o = 40$$


8.

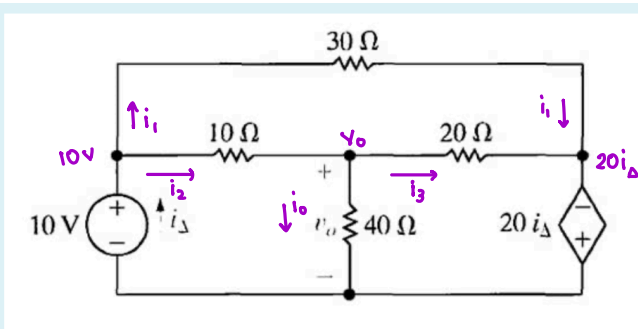

AP4.04_9ed

Use the node-voltage method to find v_o in the circuit shown

$$v_o = 24 \text{ V}$$

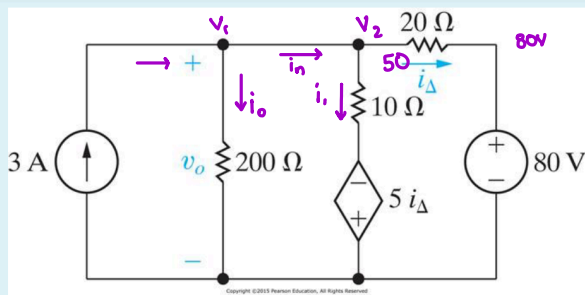

P4.17_10ed

a) Use the node-voltage method to find v_o in the circuit shown

$$v_o = 50 \text{ V}$$

b) Find the power absorbed/delivered by the dependent source P_{ds} .

$$P_{ds} = 31.875 \text{ W}$$

c) Find the power absorbed/delivered by the independent sources.

$$P_{3A} = -150 \text{ W}$$


$$P_{80V} = -120 \text{ W}$$

$$i_1 = \frac{50 - (-7.5)}{10} = \frac{57.5}{10} = 5.75$$

$$i_\Delta = \frac{50 - 80}{20} = \frac{-30}{20} = -1.5$$

$$P = (-7.5)(5.75)$$

10.

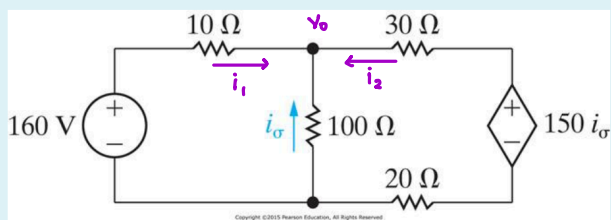

P4.18_10ed

Use the node-voltage method to find the power absorbed/delivered by the dependent source P_{ds} .

$$P_{ds} = -750 \text{ W}$$

$$\text{Node } V_o: i_\sigma = i_1 + i_2$$

$$\left[i_\sigma + \frac{V_o - 160}{10} + \frac{V_o - 150i_\sigma}{50} = 0 \right] 50$$

$$50i_\sigma + 5V_o - 800 + V_o - 150i_\sigma = 0$$

$$-100i_\sigma + 6V_o = 800$$

$$-100\left(\frac{V_o}{100}\right) + 6V_o = 800$$

$$-V_o + 6V_o = 800$$

$$V_o = 200 \text{ V}$$

$$i_\sigma = \frac{200}{100} = 2 \text{ A}$$

$$V = 150 i_\sigma = 300 \text{ V}$$