

CPE166 Quiz 1 Results for Casey Chan

❗ Correct answers are hidden.


Score for this attempt: **100** out of 100

Submitted Mar 1 at 2:54pm

This attempt took 23 minutes.

Question 1

18 / 18 pts

 

Design the above circuit in Verilog by selecting one correct answer from each drop box below.

module cir (A, B, C, F);

__input__ A, B, C;

__output__ F;

__wire__ D, E;

assign D = __~(A | B)__;

assign E = __B & C__;

assign F = __D ^ E__;

endmodule

Answer 1:

input

Answer 2:

output

Answer 3:

wire

Answer 4:

$\sim (A \mid B)$

Answer 5:

B & C

Answer 6:

$D \wedge E$

Question 2

18 / 18 pts

```
// This is a testbench for question 1.
module cir_tb;

  __reg ____ A, B, C  ;

  __wire ____ F  ;

  __integer ____ i;

  cir_uut ( ____ A, B, C, F ____ );

  initial

  begin

    for ( i = 0; i < ____ 8 ____ ; i=i+1 )
      begin
        ____ { A, B, C } = i; ____ ;
        #10;
      end

    #10 $stop;
  end

endmodule
```

Answer 1:

reg

Answer 2:

wire

Answer 3:

integer

Answer 4:

A, B, C, F

Answer 5:


8

Answer 6:

{ A, B, C } = i;

Question 3

4 / 4 pts

 

// The verilog design of cir.v is the same as that used in question 1.

```
module question3 ( A, B, Y );
```

input A, B;

output Y;

cir g1 (.A ([Select]), .B (

[Select]), .C (

[Select]), .F(

[Select]));

endmodule

Answer 1:

~B

Answer 2:

B

Answer 3:


A

Answer 4:

Y

Question 4

18 / 18 pts

 

Design the above circuit in Verilog and select one answer for each drop box below.

```
module cir2 ( A, D, C, CLK );  
  
input A, D, CLK;  
  
output C;  
  
____wire ____ E;  
  
____reg ____ B;  
  
____reg ____ C;  
  
assign E = ~ C;  
  
always@( ____ A or D or E ____)  
begin  
  
    if ( ____ D ____)  
        ____ B=A ____;  
    else  
        ____ B=E ____;  
  
end  
  
always@( ____ negedge CLK ____)  
    ____ C<=B ____;  
  
endmodule
```

Answer 1:

wire

Answer 2:

reg

Answer 3:

reg

Answer 4:

A or D or E

Answer 5:

D

Answer 6:

B=A

Answer 7:

B=E

Answer 8:

negedge CLK

Answer 9:

C<=B

Question 5

12 / 12 pts

Design a counter circuit in Verilog. The counter updates its value on the rising edge of the clock. It counts from 0 to 219, and then repeats..

```
module cir4 ( clk, cnt );    // cnt is the counter output
input  clk;
```

```
// Use minimally allowed number of bits for
```

```
// the following blanks.
```

```
output [ __7__ : 0 ] cnt;
```

```
reg    [ __7__ : 0 ] cnt;
```

```
always@(posedge clk)
```

```
begin
```

```

if ( cnt ==  )      // Type a decimal number
here
    cnt <=  ;      // Type a decimal number
here
    else
        cnt <= cnt + 1;
end
endmodule

```

Answer 1:


219

Answer 2:

0

Question 6

30 / 30 pts

 

Design the above finite state machine in Verilog by selecting one correct answer for each of the drop boxes below.

```
module fsm ( reset, clk, a, y );

input  reset, clk, a;

output a;

reg    a;

parameter S0 = 2'b00, S1=2'b01, S2=2'b10, S3=2'b11;

__reg [1:0] __ cs, ns;
// cs: current state, ns: next state

always@( posedge clk or posedge reset )
begin
    if(reset)
        __cs<=S0 __;
    else
        __cs <= ns __;
end

always@( cs or a )
begin
    case( cs)
        S0:    ns = S2;
        S1:    if (a) ns = __S1 __;
                else ns = __S0 __;

        S2:    if (a) ns = __S1 __;
                else ns = __S3 __;

        S3:    if (a) ns = __S3 __;
                else ns = __S0 __;

        default: ns = S0;

    endcase
end

always@( cs )
begin
    case( cs)
        S0:    y= __0 __;
        S1:    y= __0 __;
```


S2: y= __0__;

S3: y= __1__;

default: y = 0;

endcase

end

Answer 1:

reg [1:0]

Answer 2:

posedge clk or posedge reset

Answer 3:

cs<=S0

Answer 4:

cs <= ns

Answer 5:

S1

Answer 6:

S0

Answer 7:

S1

Answer 8:

S3

Answer 9:

S3

Answer 10:

S0

Answer 11:

CS

Answer 12:

0

Answer 13:

0

Answer 14:

0

Answer 15:

1

Quiz Score: **100** out of 100