
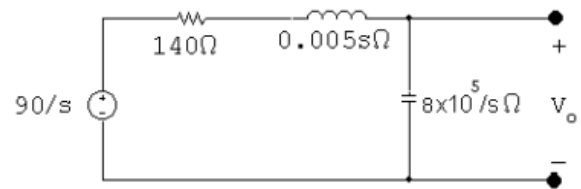


Solution of Homework-04 ENGR 117

5 Questions 20 points each

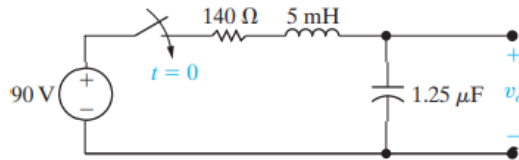Q-1 Find V_o and v_o in the circuit shown below if the initial energy is zero and the switch is closed at $t=0$. Also find the transfer function and identify the poles and zeros for this circuit. (Use circuit transform method)



$$\begin{aligned}
 V_o &= \frac{(90/s)(8 \times 10^5/s)}{140 + 0.005s + (8 \times 10^5/s)} \\
 &= \frac{144 \times 10^8}{s(s^2 + 28,000s + 16 \times 10^7)} \\
 &= \frac{144 \times 10^8}{s(s + 8000)(s + 20,000)} \\
 &= \frac{K_1}{s} + \frac{K_2}{s + 8000} + \frac{K_3}{s + 20,000}
 \end{aligned}$$

$$K_1 = \frac{144 \times 10^8}{16 \times 10^7} = 90$$

$$K_2 = \frac{144 \times 10^8}{(-8000)(12,000)} = -150$$

$$K_3 = \frac{144 \times 10^8}{(-12,000)(-20,000)} = 60$$

$$V_o = \frac{90}{s} - \frac{150}{s + 8000} + \frac{60}{s + 20,000}$$

$$v_o(t) = [90 - 150e^{-8000t} + 60e^{-20,000t}]u(t) \text{ V}$$

$$H(s) = \frac{v_o}{v_i} = \frac{144 \times 10^8}{s(s + 8000)(s + 20,000)} \text{ divided by } 90/s$$

$$H(s) = \frac{1.6 \times 10^8}{(s + 8000)(s + 20,000)}$$

No Zeros



2 Poles: -8000 and -20000

Q-2 There is no energy stored in the circuit shown below at the time the voltage source is turned on. (Use circuit transform method)

$$v_g = 325u(t) \text{ V.}$$

a) Find V_o and I_o

b) Find v_o and i_o

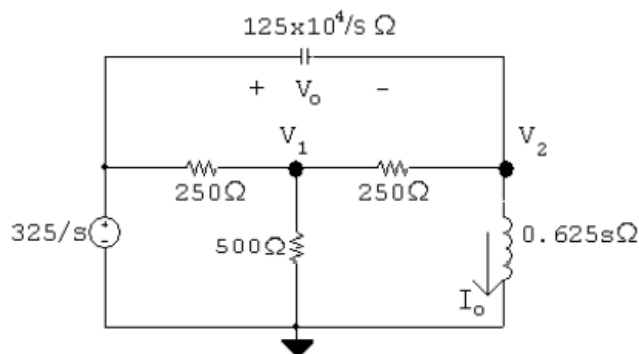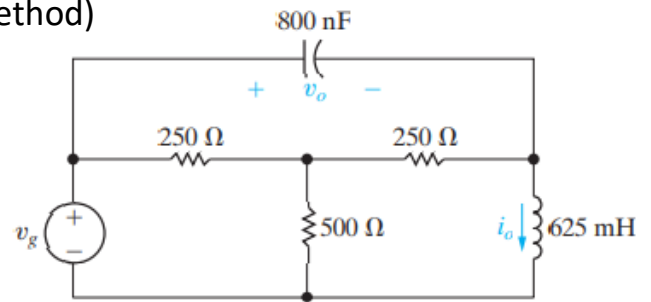

$$\frac{V_1 - 325/s}{250} + \frac{V_1}{500} + \frac{V_1 - V_2}{250} = 0$$

$$\frac{V_2}{0.625s} + \frac{V_2 - V_1}{250} + \frac{(V_2 - 325/s)s}{125 \times 10^4} = 0$$

Thus,

$$5V_1 - 2V_2 = \frac{650}{s}$$

$$-5000sV_1 + (s^2 + 5000s + 2 \times 10^6)V_2 = 325s$$

$$\Delta = \begin{vmatrix} 5 & -2 \\ -5000s & s^2 + 5000s + 2 \times 10^6 \end{vmatrix} = 5(s + 1000)(s + 2000)$$

$$N_2 = \begin{vmatrix} 5 & 650/s \\ -5000s & 325s \end{vmatrix} = 1625(s + 2000)$$

$$V_2 = \frac{N_2}{\Delta} = \frac{1625(s + 2000)}{5(s + 1000)(s + 2000)} = \frac{325}{s + 1000}$$

$$V_o = \frac{325}{s} - \frac{325}{s + 1000} = \frac{325,000}{s(s + 1000)}$$


$$I_o = \frac{V_2}{0.625s} = \frac{520}{s(s + 1000)} = \frac{0.52}{s} - \frac{0.52}{s + 1000}$$

[b] $v_o(t) = (325 - 325e^{-1000t})u(t) \text{ V}$

$$i_o(t) = (520 - 520e^{-1000t})u(t) \text{ mA}$$

Q-3 Draw the magnitude and phase Bode diagram for the following transfer function.

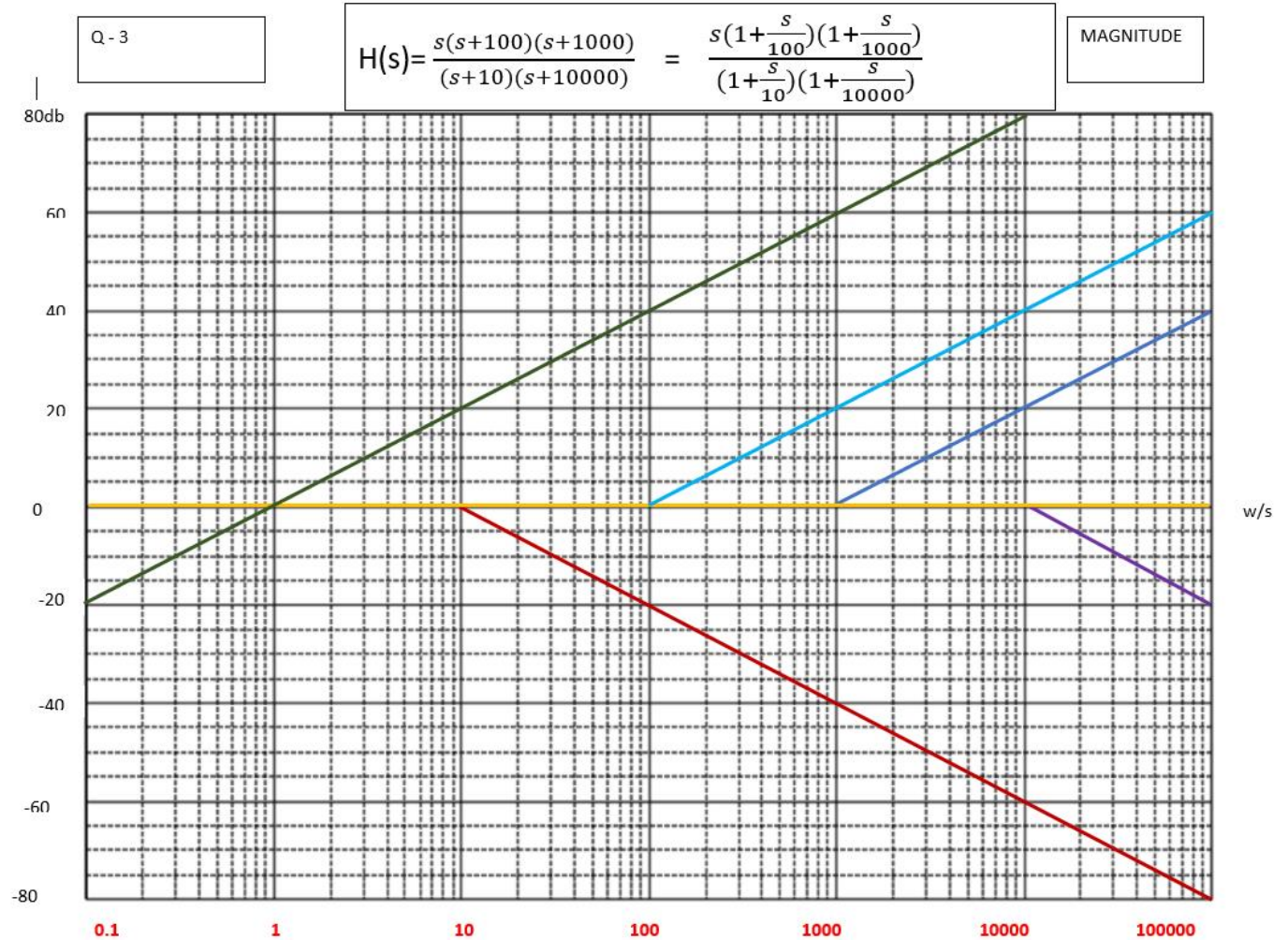
$$H(s) = \frac{s(s+100)(s+1000)}{(s+10)(s+10000)}$$



Q - 3

$$H(s) = \frac{s(s+100)(s+1000)}{(s+10)(s+10000)} = \frac{s(1+\frac{s}{100})(1+\frac{s}{1000})}{(1+\frac{s}{10})(1+\frac{s}{10000})}$$


MAGNITUDE

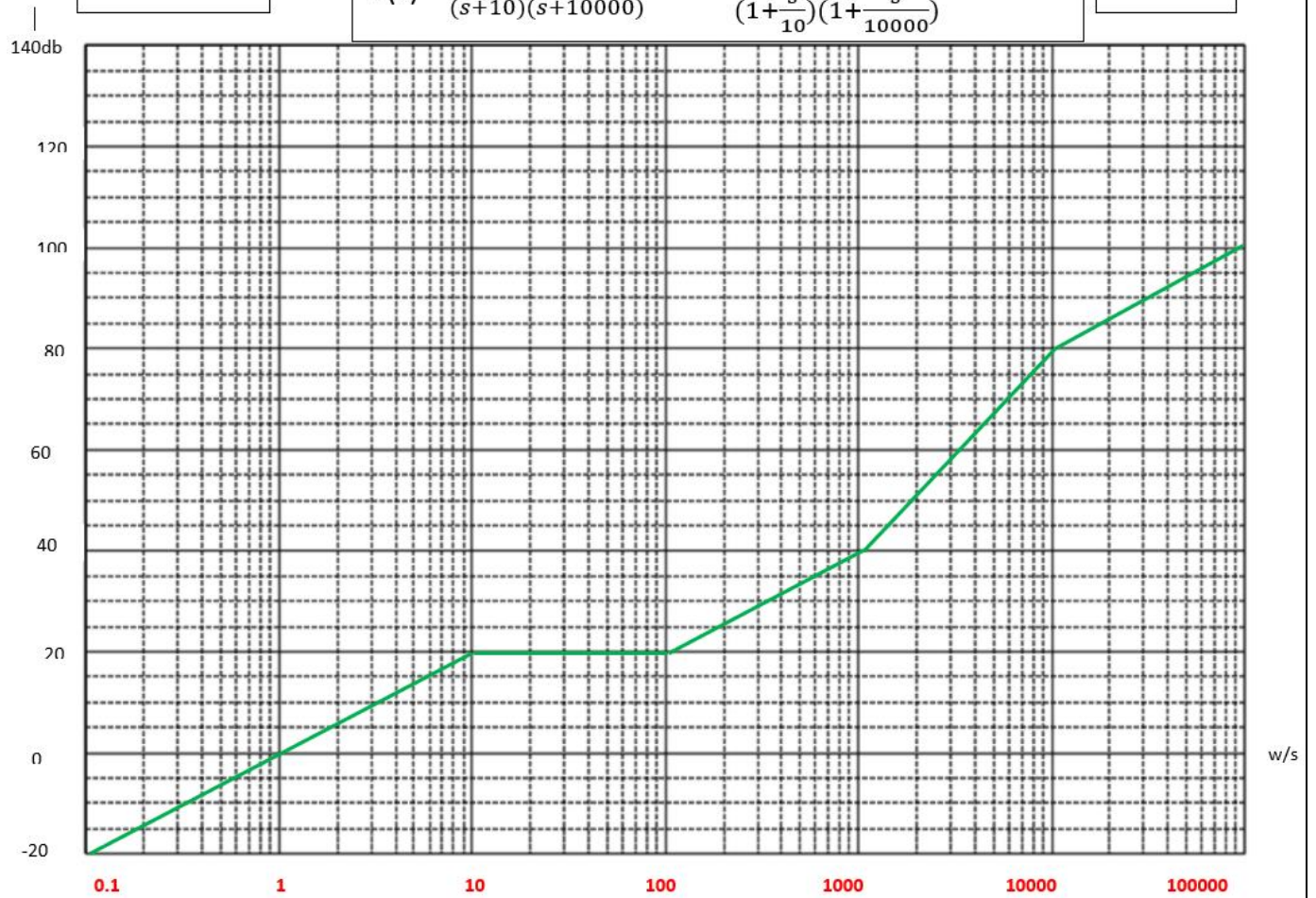

Q - 3


$$H(s) = \frac{s(s+100)(s+10000)}{(s+10)(s+10000)} = \frac{s(1+\frac{s}{100})(1+\frac{s}{10000})}{(1+\frac{s}{10})(1+\frac{s}{10000})}$$

PHASE

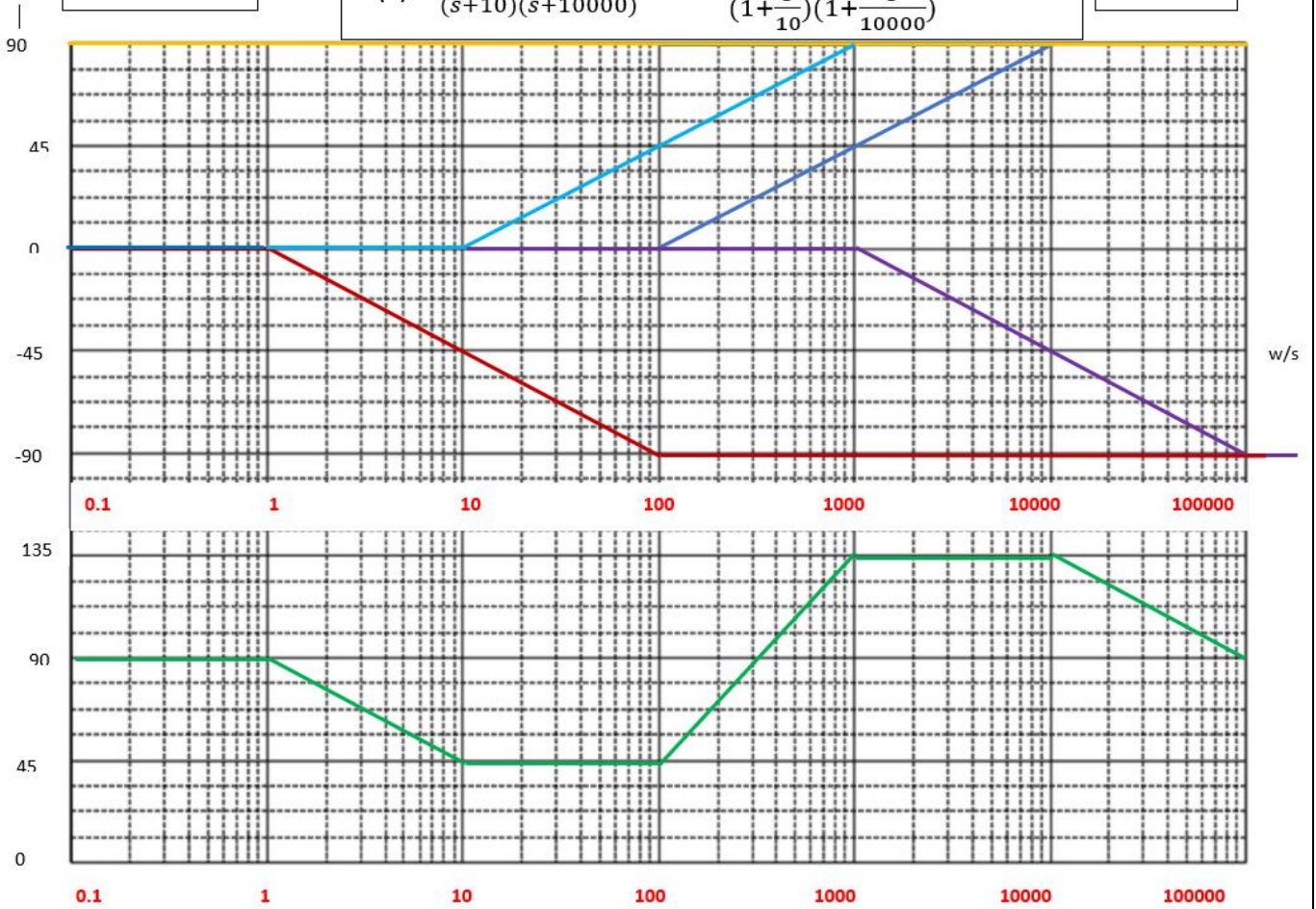

Q-4 Draw the magnitude and phase Bode diagram for the following transfer function.

$$H(s) = \frac{(s+3)}{(s+30)(s+300)}$$

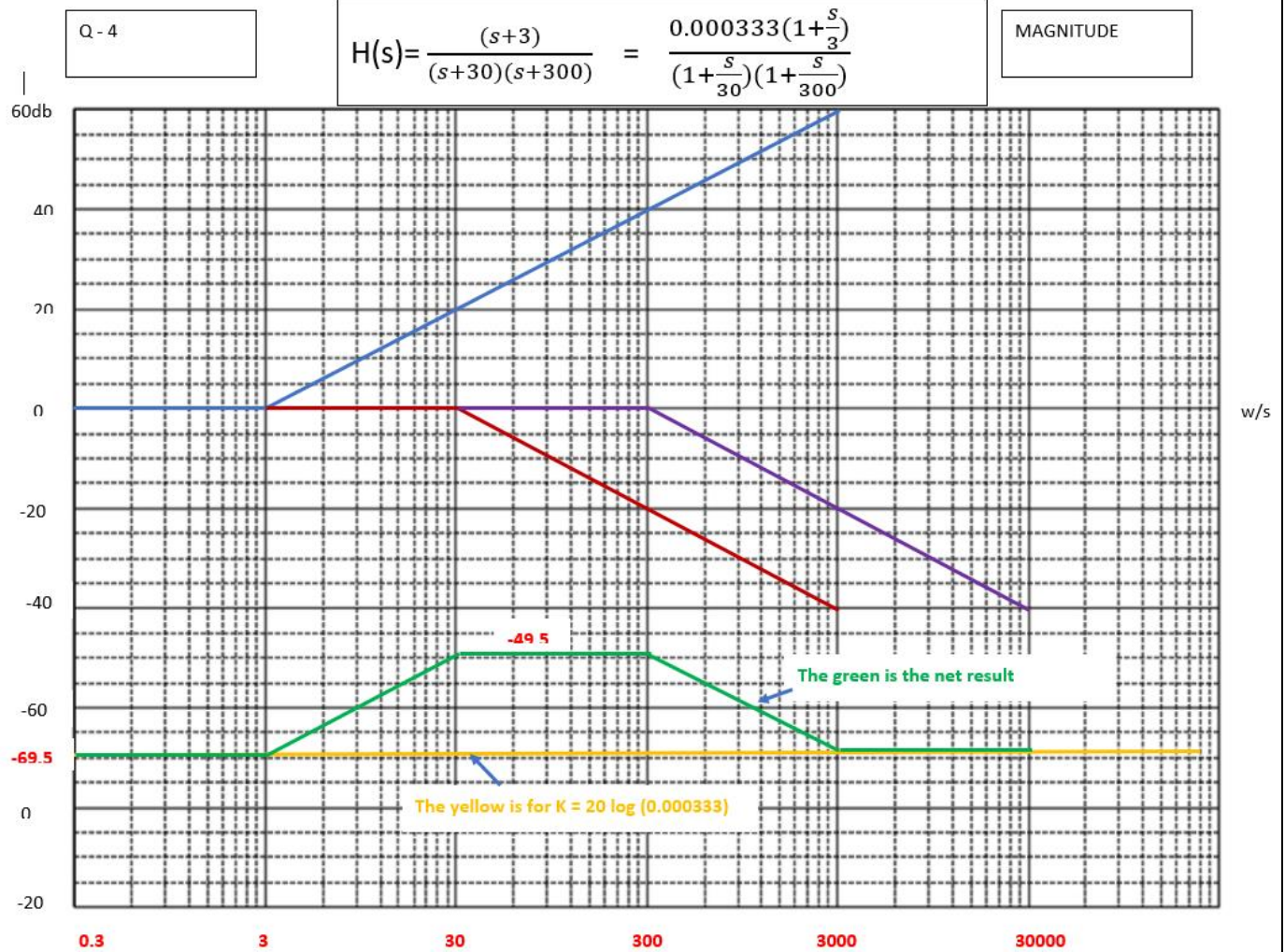


Q - 4

$$H(s) = \frac{(s+3)}{(s+30)(s+300)} = \frac{0.000333(1+\frac{s}{3})}{(1+\frac{s}{30})(1+\frac{s}{300})}$$


Phase

90 degree

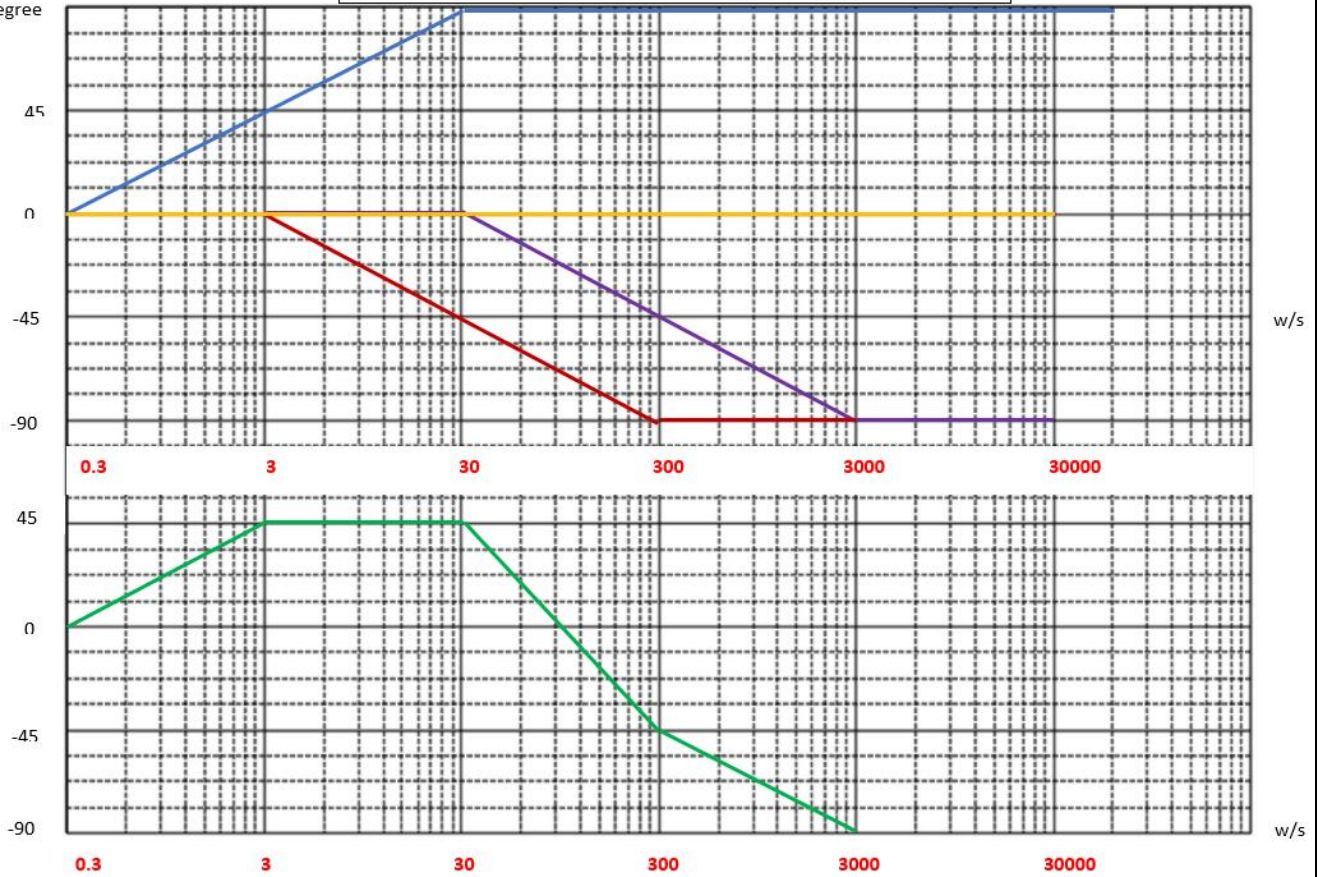

Q-5 Draw the magnitude and phase Bode diagram for the following transfer function.

$$H(s) = \frac{(s+1)(s+10)}{s(s+10)^2}$$

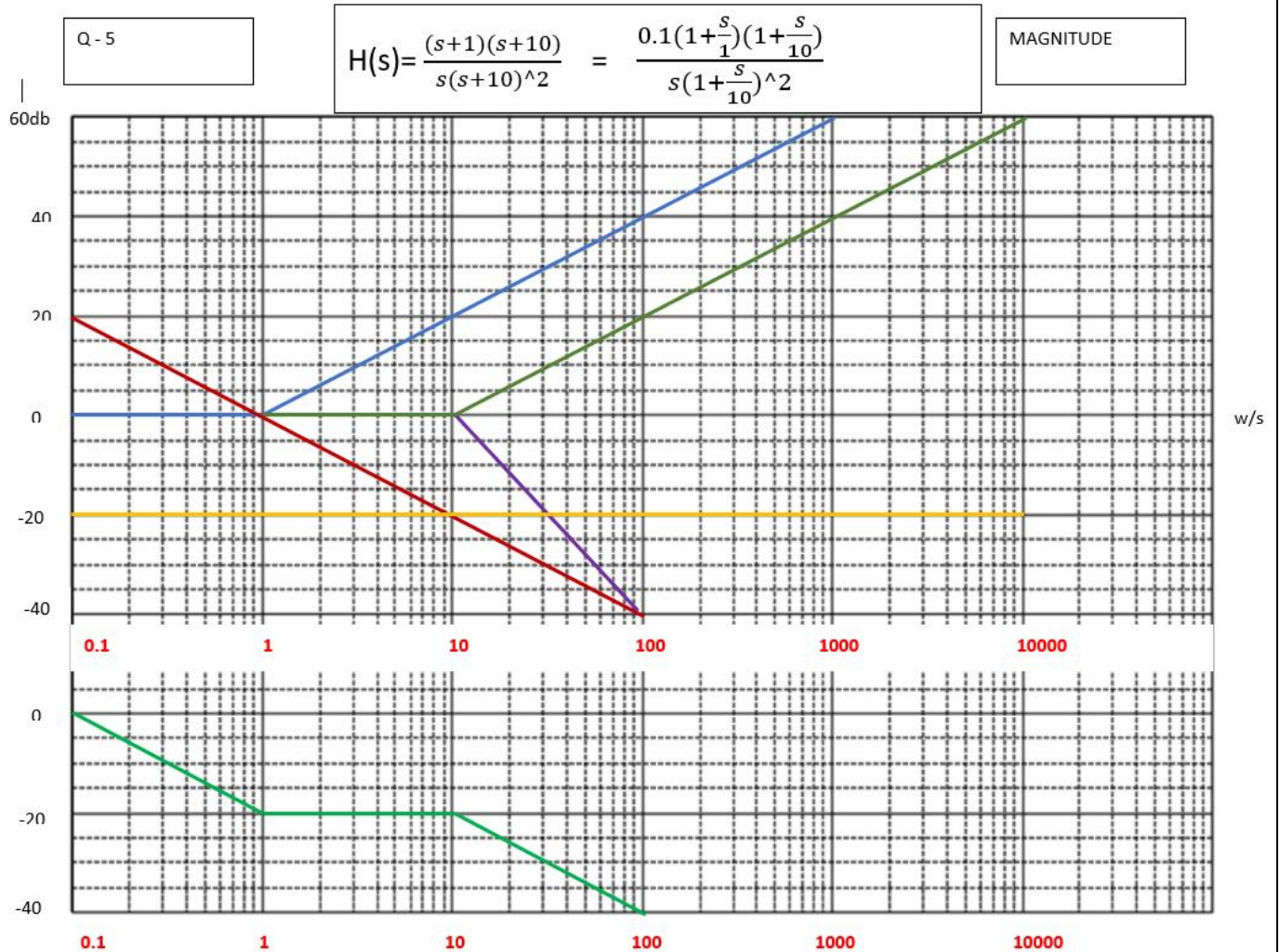

Q - 5

$$H(s) = \frac{(s+1)(s+10)}{s(s+10)^2} = \frac{0.1(1+\frac{s}{1})(1+\frac{s}{10})}{s(1+\frac{s}{10})^2}$$

Phase

