

Midterm I EEE 117 Date 02/24/2022 (1:30 - 3:00 p.m.)

SOLUTION

Q-1 Use phasor method to add the following sinusoidal: **(20 points)**

$$V_1 = 25 \sin (4000t + 45^\circ)$$

$$V_2 = 72 \sin (4000t + 27^\circ)$$

$$V_3 = 150 \cos (4000t - 87^\circ)$$

$$V_4 = 10 \cos (4000t - 143^\circ)$$

$$V(t) = 242.897 \cos (4000 t + -78.06^\circ)$$

Q-2 A $90 \, \Omega$ resistor, a 32 mH inductor, and a 5uF capacitor are connected in series across the terminals of a sinusoidal voltage source. The steady-state expression for the source voltage is $750 \cos (5000t + 30^\circ) \text{ V}$. **(Note: 750 is Max^m Value)**

Calculate the steady-state current $i(t)$ by the phasor method. **(20 points)**

ω	=	5000	rad/sec
V_i	=	750	V
Phase	=	30	deg.
R	=	90	ohm
L	=	32	mH
X_L	=	160	ohm
C	=	5	uf
X_C	=	40	Ohm

Vs	649.5191 + j	375	=	750	<i>L</i>	30
R	90 + j	0	=	90	<i>L</i>	0
ZL	9.8E-15 + j	160	=	160	<i>L</i>	90
ZC	2.45E-15 + j	-40	=	40	<i>L</i>	-90
ZT	90 + j	120	=	150	<i>L</i>	53.1301
I	4.598076 + j	-1.9641	=	5	<i>L</i>	-23.1301 = 5 Cos (5000 t + -23.13 °)



Q-3 For the following ideal transformer, Find V_2 and I_2 : **(20 points)**

if $N_1 = 5$

$N_2 = 25$

$V_1 = 3V$

$I_1 = 1.5 A$

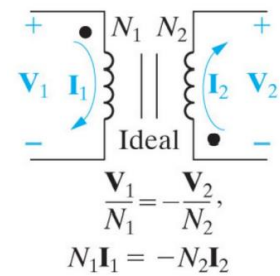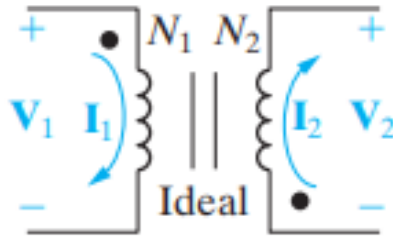

$V_2 = (-3 \cdot 25) / 5 = -15 V$


$I_2 = -5 \cdot 1.5 / 25 = -0.3 A$

Q-4 Analyze the circuit and find: **(40 points)**

- Currents and voltages for each branch.
- Complex power " S_2 " in branch 2.
- Active (P), Reactive (Q) and Apparent (S) powers in branch 2.

$i_g = 100 \cos 10000t \text{ mA}$

(100 is Max^m Value)

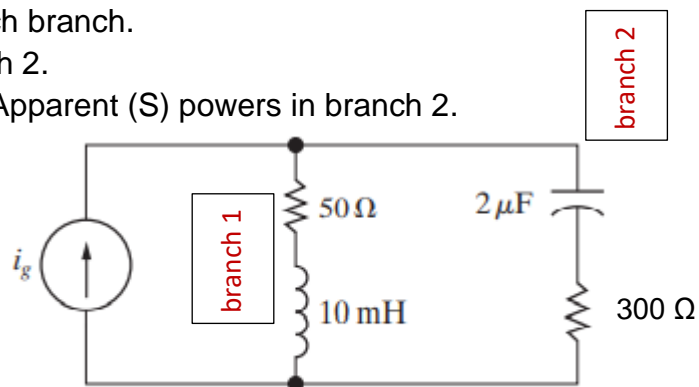

I (branch 1)	0.082 + j -0.0260000
V (branch 1)	6.7 6.9000000
I (branch 2)	0.018 0.0260000
V (branch 2)	6.7 + j 6.9000000

I (conj) (branch 2)	0.018 + j -0.0260000
$S_2 = 1/2 \cdot V \cdot I(\text{conj})$	0.15 + j -0.0250000

P = 0.15 watt

Q = - 0.025 VAR

S = 0.152 VA