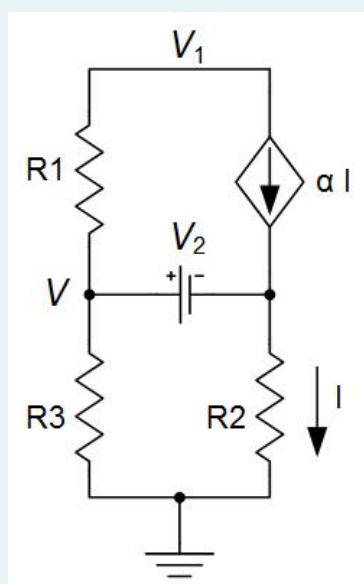


Started on	Monday, 18 July 2022, 9:34 PM
State	Finished
Completed on	Monday, 18 July 2022, 11:48 PM
Time taken	2 hours 14 mins
Grade	9.0 out of 10.0 (90%)

Question 1

Correct

Mark 1.0 out of 1.0



For the circuit shown, what is the value of the voltage V in volts? Use: $V_1 = 6.1\text{V}$, $V_2 = 1.0\text{V}$, $R_1 = 11.7\text{k}\Omega$, $R_2 = 1.4\text{k}\Omega$, $R_3 = 12.0\text{k}\Omega$ and $\alpha = 0.81$.

Answer: ✓

The correct answer is: 2.16

Correct

Marks for this submission: 1.0/1.0.

Question **2**

Correct

Mark 1.0 out of 1.0

If a 17.7pF capacitor is connected in parallel with a 18.4pF capacitor and a 39.4pF capacitor, then what is the total capacitance of this parallel combination in pico Farads?

Answer: ✓

The correct answer is: 75.50

Correct

Marks for this submission: 1.0/1.0.

Question **3**

Correct

Mark 1.0 out of 1.0

If a 1.1k Ω resistor has 3.7 volts across it, then what is the value of the current flowing through this resistor in milliamps?

Answer: ✓

The correct answer is: 3.36

Correct

Marks for this submission: 1.0/1.0.

Question **4**

Correct

Mark 1.0 out of 1.0

If a 27.5pF capacitor, a 29.2pF capacitor and a 38.7pF capacitor are all connected in series, then what is the total capacitance of this series combination in pico Farads?

Answer: ✓

The correct answer is: 10.37

Correct

Marks for this submission: 1.0/1.0.

Question **5**

Correct

Mark 1.0 out of 1.0

The energy stored by a resistor is given by :

Select one:

- ☒ a. None of the these
- ☐ b. $R \cdot I^2 / 2$
- ☐ c. $R \cdot V \cdot V / 2$
- ☐ d. $R \cdot V / I$
- ☐ e. $R \cdot V \cdot I$



The correct answer is: None of the these

Correct

Marks for this submission: 1.0/1.0.

Question **6**

Correct

Mark 1.0 out of 1.0

If a circuit has 3 nodes and 2 loops in it, then :

Select one:

- ☐ a. Both Nodal and Mesh analysis will require solving the same number of equations
- ☐ b. Mesh analysis will require solving more equations than Nodal analysis
- ☐ c. None of these
- ☐ d. It is impossible to determine which method will require solving more equations
- ☒ e. Nodal analysis will require solving more equations than Mesh analysis



The correct answer is: Nodal analysis will require solving more equations than Mesh analysis

Correct

Marks for this submission: 1.0/1.0.

Question 7

Correct

Mark 1.0 out of 1.0

Inductors in parallel can be combined to find the total equivalent inductance by :

Select one:

- ☐ a. Multiplying the inductances together
- ☐ b. Adding the inductances together
- ☐ c. None of the these
- ☒ d. Taking the reciprocal of the sum of the reciprocals of each inductance
- ☐ e. Adding the reciprocal of each inductance together



The correct answer is: Taking the reciprocal of the sum of the reciprocals of each inductance

Correct

Marks for this submission: 1.0/1.0.

Question 8

Correct

Mark 1.0 out of 1.0

Nodal analysis is easier to perform than Mesh analysis for circuits that have fewer loops than nodes.

Select one:

- ☐ True
- ☒ False



The correct answer is 'False'.

Correct

Marks for this submission: 1.0/1.0.

Question 9

Correct

Mark 1.0 out of 1.0

The Thevenin's equivalent voltage for a circuit is equal to the Norton's equivalent current divided by the Norton's equivalent resistance for the same circuit.

Select one:

- ☐ True
- ☒ False



The correct answer is 'False'.

Correct

Marks for this submission: 1.0/1.0.

Question **10**

Correct

Mark 0.0 out of 1.0

The Thevenin's equivalent voltage for a circuit is found by measuring the output voltage of the circuit while the output is short circuited.

Select one:

☐ True

☒ False ✓

The correct answer is 'False'.

Correct

Marks for this submission: 1.0/1.0. Accounting for previous tries, this gives **0.0/1.0**.

[◀ Example 1.2 on Power dissipation and efficiency](#)

Jump to...



[Quiz 1b - Signals and Amplifiers ▶](#)