

Homework-01

EEE 117

Due date 02/07/2022

Questions 1-5 2 points each

Questions 6-11 15 points each

Q-1 The rms value of $v(t) = V_{\max} \cos(\omega t + \delta)$ is given by
(a) V_{\max} (b) $V_{\max}/\sqrt{2}$ (c) $2 V_{\max}$ (d) $\sqrt{2} V_{\max}$

Q-2 If the rms phasor of a voltage is given by $V = 120/\underline{60^\circ}$ volts, then the corresponding $v(t)$ is given by
(a) $120\sqrt{2} \cos(\omega t + 60^\circ)$ (b) $120 \cos(\omega t + 60^\circ)$
(c) $120\sqrt{2} \sin(\omega t + 60^\circ)$

Q-3 If a phasor representation of a current is given by $I = 70.7/\underline{45^\circ}$ A, it is equivalent to
(a) $100 e^{j45^\circ}$ (b) $100 + j100$
(c) $50 + j50$

Q-4 With sinusoidal steady-state excitation, for a purely resistive circuit, the voltage and current phasors are
(a) in phase
(b) perpendicular with each other with V leading I
(c) perpendicular with each other with I leading V.

Q-5 For a purely inductive circuit, with sinusoidal steady-state excitation, the voltage and current phasors are
(a) in phase
(b) perpendicular to each other with V leading I
(c) perpendicular to each other with I leading V.

Q-6 Consider the sinusoidal voltage

$$v(t) = 25 \cos(400\pi t + 60^\circ) \text{ V.}$$

- a) What is the maximum amplitude of the voltage?
- b) What is the frequency in hertz?
- c) What is the frequency in radians per second?
- d) What is the phase angle in radians?
- e) What is the phase angle in degrees?
- f) What is the period in milliseconds?
- g) What is the first time after $t = 0$ that $v = 0$ V?

Q-7 Use the concept of the phasor to combine the following sinusoidal functions into a single trigonometric expression:

a) $y = 30 \cos(200t - 160^\circ) + 15 \cos(200t + 70^\circ)$,

b) $y = 90 \sin(50t - 20^\circ) + 60 \cos(50t - 70^\circ)$,

c) $y = 50 \cos(5000t - 60^\circ) + 25 \sin(5000t + 110^\circ) - 75 \cos(5000t - 30^\circ)$,


d) $y = 10 \cos(\omega t + 30^\circ) + 10 \sin \omega t + 10 \cos(\omega t + 150^\circ)$.

Q-8 A 25Ω resistor and a 10 mH inductor are connected in parallel. This parallel combination is also in parallel with the series combination of a 30Ω resistor and a $10 \mu\text{F}$ capacitor. These three parallel branches are driven by a sinusoidal current source whose current is $125 \sin(2500t + 60^\circ) \text{ A}$.

- a) Find total impedance.
- b) Analyze the circuit and find current and voltage for each component.


Q-9 For the circuit shown below.

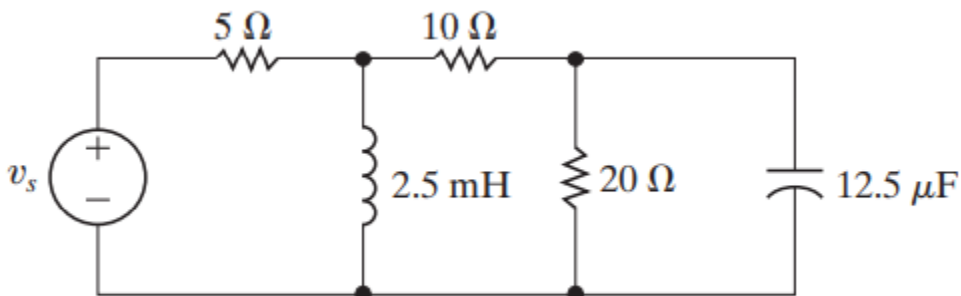- c) Find total impedance.
- d) Analyze the circuit and find current and voltage for each component. if $v_s = 25 \sin 4000t \text{ V}$.



Q-10 Analyze the circuit and find current and voltage for each component.

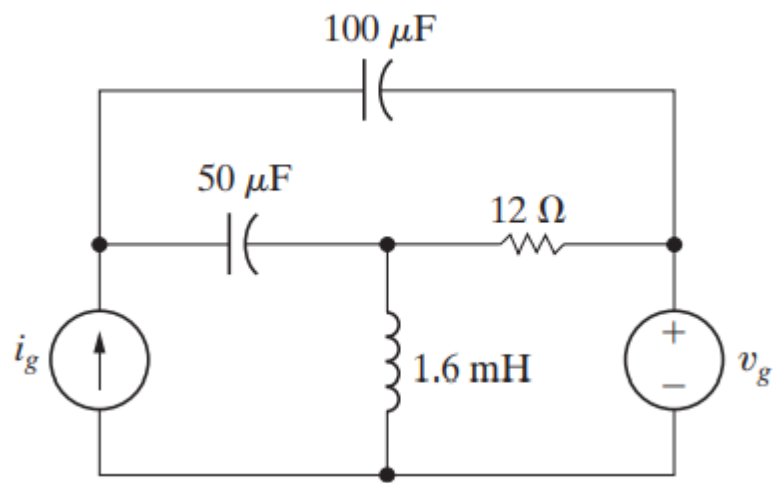if $i_g = 5 \cos 2500t$ A and $v_g = 20 \cos (2500t + 90^\circ)$ V.



Q-11 In the figure shown below, $\bar{I} = 10 \angle 0^\circ$ A, compute the phasors \bar{I}_1 , \bar{I}_2 and \bar{V} .

