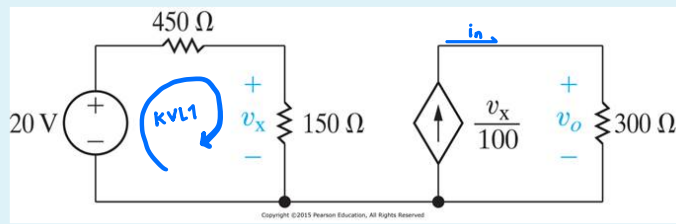


1.



P2.33_10ed

a) Find v_o .

$v_o = 15$ Volts

b) Find the total power absorbed in the circuit.

$P_{total} = 1.417$ Watts

$$KVL1: -20V + i(450\Omega) + i(150\Omega) = 0$$

$$i = \frac{1}{30} A$$

$$v_x = (\frac{1}{30}A)(150\Omega) = 5V$$

$$i_n = v_x/100 = 5/100 = 0.05 A$$

$$v_o = i_n(300\Omega) = (0.05A)(300\Omega)$$

$$v_o = 15 V$$

TOTAL POWER ABSORBED:


$$P_T = P_{450\Omega} + P_{150\Omega} + P_{300\Omega}$$

$$P = i^2 R = V^2/R$$

$$= (\frac{1}{30}A)^2(450\Omega) + (\frac{1}{30}A)^2(150\Omega) + (15V)^2/300\Omega$$

$$P_T = 17/12 \approx 1.417 W$$

2.

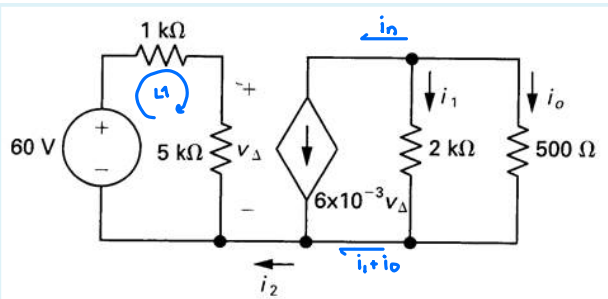

P2.26_6ed

a) Find the current i_2 .

$i_2 = 0$ A

b) Find voltage v_D .

$v_D = 50$ V

c) Find the current i_o .

$i_o = -240$ mA (milli A)

$$L1: -60V + i(1000\Omega) + i(5000\Omega) = 0$$

$$i_n = 6 \times 10^{-3} v_D = (6 \times 10^{-3})(50)$$

$$i = 0.01A$$

$$= 0.3A$$

$$v_D = (0.01A)(5k\Omega) = 50V$$

$$-v = i_1 R_1 = i_o R_o$$

$$-i_n R_{eq} = i_1 R_1 = i_o R_o$$

$$-i_n (\frac{R_1 R_o}{R_1 + R_o}) = i_1 R_1 = i_o R_o$$

$$i_2 = i_n - (i_1 + i_o)$$

$$= 0.3A - (0.06A + 0.24A)$$

$$i_2 = 0A$$

$$i_1 = \frac{-i_n R_o}{R_1 + R_o} = \frac{(0.3A)(0.5k\Omega)}{2k\Omega + 0.5k\Omega} = -0.06A$$

$$i_o = \frac{-i_n R_1}{R_1 + R_o} = \frac{(0.3A)(2k\Omega)}{2k\Omega + 0.5k\Omega} = -0.24A$$

$$v_o = 5V$$

$$KVL: -v_a + v_g + v_o = 0$$

$$v_o = 10V_a$$

$$v_g = v_a - v_o = 0.5V - 5V = -4.5V$$

$$v_a = 0.5V$$

$$KVL: -20V + v_{qa} - v_g + v_a = 0$$

$$v_{qa} = 20V + v_g - v_a$$

$$= 20V - 4.5V - 0.5V = 15V$$

$$KCL \text{ Node } a: -9A - 6A + i_3 = 0$$

$$i_3 = 15A$$

$$P_{del}: P_{10V_a} = -(10V_a) i_3$$


$$= -(5V)(15A) = -75W$$

$$P_{qa} = -v_{qa}(9A)$$

$$= -(15V)(9A) = -135W$$

$$-210W$$

3.

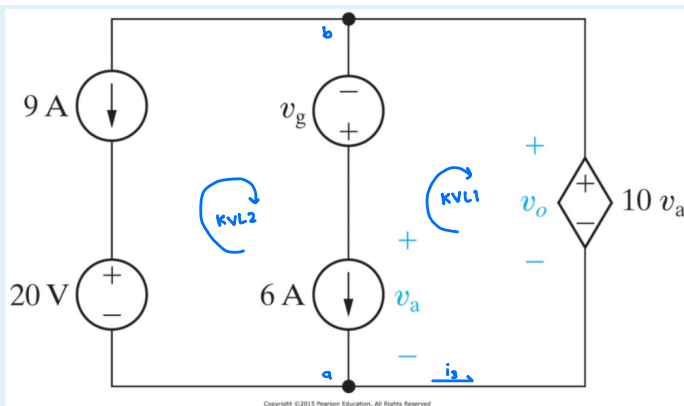


P2.10_10ed

Given that $v_o = 5$ Volts.

Find the total power delivered in the circuit. $P_{del, total} = 77 W$

Answer: -210

4.

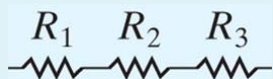

CQ3.01

Given:

$R_1 = 278053\Omega$ (Ohms) $R_2 = 89628\Omega$ (Ohms) $R_3 = 51000\Omega$ (Ohms)

Find the equivalent resistance R_{eq} .

$R_{eq} = ?? \Omega$ (Ohms)


Answer: 418681

$$R_{series} = R_1 + R_2 + R_3$$

$$= 278053\Omega + 89628\Omega + 51000\Omega$$

$$= 418681\Omega$$

5

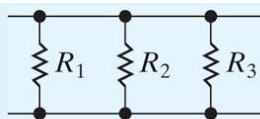


CQ3.02

Given:

$$R_1 = 29466 \, \Omega \text{ (Ohms)} \quad R_2 = 450479 \, \Omega \text{ (Ohms)} \quad R_3 = 3569 \, \Omega \text{ (Ohms)}$$

Find the equivalent resistance R_{Eq} .


$$R_{Eq} = ?? \, \Omega \text{ (Ohms)}$$

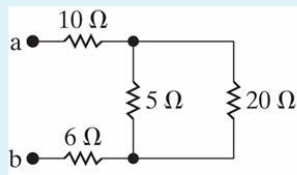Answer: ✓

P3.05a_9ed

Find the equivalent resistance seen looking into terminals a,b.


$$R_{Eq} = ?? \, \Omega \text{ (Ohms)}$$

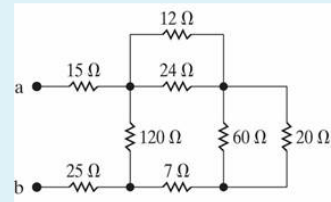Answer: ✓

P3.06a_9ed

Find the equivalent resistance seen looking into terminals a,b.

$$R_{Eq} = ?? \, \Omega \text{ (Ohms)}$$

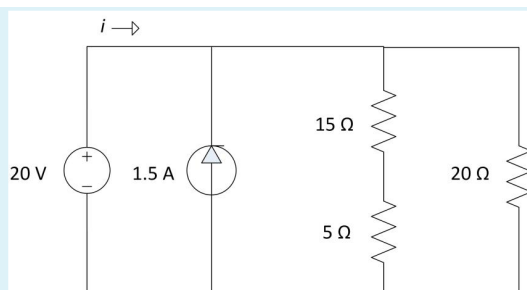
Answer: ✓

AS3.2

Find the current i in this circuit.

$$i = ?? \text{ Amps}$$

Answer: ✓

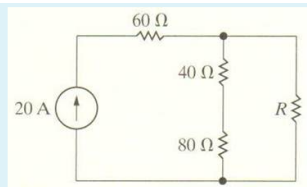

AP3.03_9ed

a) Find the value of R that will cause 4 A of current to flow through the 80 Ω resistor in the circuit.

$R = 30 \checkmark \Omega$ (Ohm)

b) How much power will the resistor R from part (a) need to dissipate?


$P_R = 7680 \checkmark$ Watts

c) How much power will the current source generate for the value of R from part (a)?

$P_{20A} = -33600 \checkmark$ Watts

"-" = "delivering" and "+" = "absorbing"

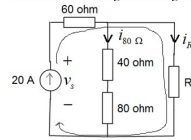(a) Consider the following circuit diagram:



Use current division to write the expression for current through the 80 Ω resistor.

$$i_{80\Omega} = (20 \text{ A}) \left(\frac{R}{R + (40 + 80)} \right)$$

$$4 = (20) \frac{R}{R + 120} \quad (\text{given } i_{80\Omega} = 4 \text{ A})$$

$$\frac{R}{R + 120} = \frac{4}{20}$$


$$20R = 4(R + 120)$$

$$20R - 4R = 4(120)$$

$$16R = 4(120)$$

$$R = \frac{4(120)}{16}$$

$$R = 30 \Omega$$

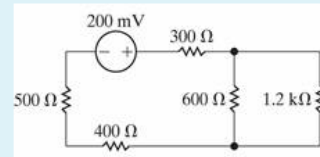

P3.03c_9ed

Find the equivalent resistance seen by the 3 mA current source.

$R_{Eq} = ?? \Omega$ (Ohms)

Answer: 1600 \checkmark