

Midterm II EEE 117 Date 04/12/2022 (1:30 - 2:45 p.m.)


SOLUTION MUST BE HAND WRITTEN AND SUBMIT THEM BEFORE 3:00 P.M.

Q-1 The switch in the circuit shown below has been in position x for a long time. At $t=0$, the switch moves instantaneously to position y. **(40 points)**

a) Construct an s-domain circuit for $t > 0$

b) Find i_0


c) Find i_0

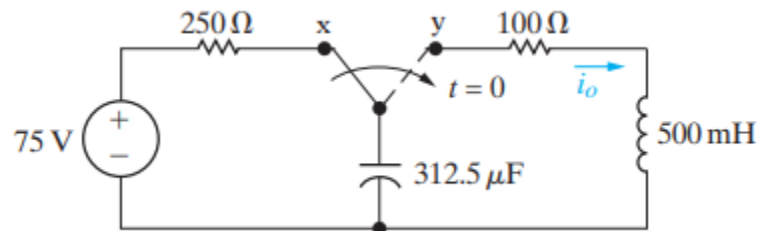

Q-2 There is no energy stored in the circuit shown below at $t=0^-$ **(20 points)**

a) Construct an s-domain circuit for $t > 0$

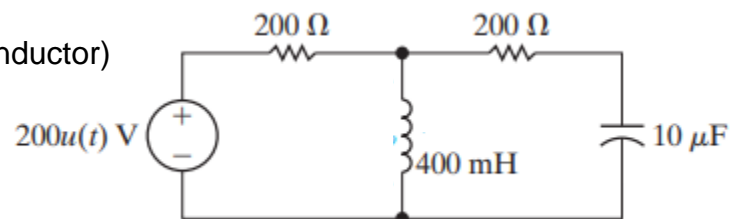b) Find $V_0(s)$ (Voltage across inductor)



Q-3 Draw Straight line Bode diagram for Amplitude and Phase. **(40 points)**

Draw on Semi log sheet and show both individual and combined results.

(Ignore damping effect)

a)
$$H(s) = \frac{40000(s+4)}{(s+400)(s+4000)}$$

b)
$$H(s) = \frac{10(s^2 + 2s + 1)}{(s^2 + 5s + 100)}$$