

# CPE 166 Quiz 2

Started: Nov 8 at 3:29pm

## Quiz Instructions

---



### Question 1

1 pts

What is the symbol used for signal assignment?

Your answer is \_\_\_\_\_  \_\_\_\_\_



### Question 2

1 pts

```
process (CLK, reset)
begin
  if (reset = '1') then
    Q <= '0';
  elsif (CLK'event and CLK = '1') then
    Q <= D;
  end if;
end process;
```

The above code is the process for which hardware?

Your answer is \_\_\_\_\_  \_\_\_\_\_



### Question 3

1 pts

```

LIBRARY ieee;
USE ieee.std_logic_1164.all;

ENTITY shiftreg is
PORT (   CLK           : IN  STD_LOGIC;
        Sin            : IN  STD_LOGIC;
        Sout           : OUT STD_LOGIC);
END shiftreg;

ARCHITECTURE behavior OF shiftreg IS
    SIGNAL sreg         : STD_LOGIC_VECTOR(3 DOWNTO 0);
BEGIN

    PROCESS (clk)
    BEGIN
        IF FALLING_EDGE(CLK) THEN
            sreg <= Sin & sreg(3 DOWNTO 1);
        END IF;
    END IF;
end process;

Sout <= sreg(0);

end behavior;

```

What is the synthesized hardware circuit for the above VHDL code?

The answer is \_\_\_\_\_ The falling edge triggered right :v

\_\_\_\_\_



#### Question 4

1 pts

```
s(15 downto 0) <= s(15)&s(15)&s(15)&s(15 downto 3);
```

What is the synthesized hardware circuit for the above VHDL code?

The answer is \_\_\_\_\_

A 16-bit arithmetic shift right by ▾

\_\_\_\_\_



### Question 5

1 pts

Generate the following waveform for signal x by using VHDL.




x <= '1', '0' after 2 ns, '1' after  ns, '0' after 4 ns, '1' after 5 ns;



### Question 6

1 pts

 

Part of the ASM chart is shown above. Fill out the blank1 for the VHDL code below.

```
process(state, A, B)
```

```
begin
```

```
case state is
```

```
when s0 => ...
```

```
when s1 => ...
```

```
when s2 => if A = '0' then next_state <= s2;
```

```
    elsif B = '0' then
```

```
        next_state <= s2;
```

```
    else next_state <= ____ s3 ____;
```

```
end if;
```

...

End case;

End process;



## Question 7

1 pts

...

Architecture circuit of mydesign is

signal m: std\_logic\_vector(1 downto 0);

signal f, g, h, k: std\_logic;

signal q, p, w: std\_logic;

begin

with m select

q <= f and g when "00",

h when "01",

h when "10",

k when others;

process( clk )

begin

if (rising\_edge clk ) then

p <= q;

w <= not p;

```

end if;

end process;


end circuit;

```


Which synthesized circuit corresponds to the VHDL design above?

Your answer is  .

(a).

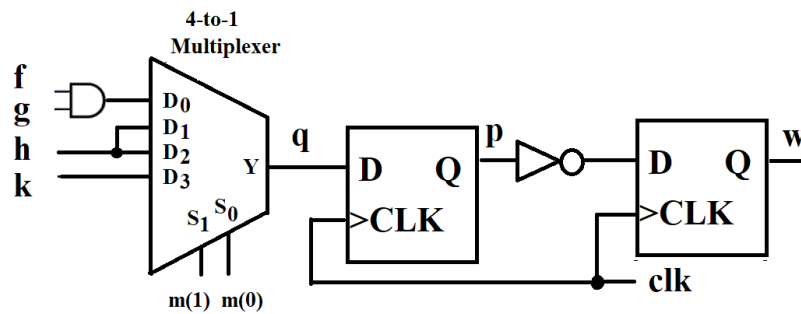

(b).

 

(c). None of above



## Question 8

1 pts

```

library ieee;

```

```

use ieee.std_logic_1164.all ;

use ieee.std_logic_unsigned.all ;

use ieee.std_logic_arith.all;

entity pulse is

port( clk, reset: in std_logic;

w: in std_logic_vector (3 downto 0) ;

y: out std_logic );

end pulse;


architecture arch of pulse is

signal r_reg : std_logic_vector(3 downto 0) ;

begin


process (clk, reset)

begin

if (reset='1') then

    r_reg <= (others=>'0');

    y    <= '0';

elsif (clk'event and clk='1') then

    if(r_reg = __"100"__ ) then

        r_reg <= (others=>'0');

        y <= '1';

    else

        r_reg <= r_reg + 1;

        y <= '0';


    end if;

end if;

```

```
end if;  
  
end process;  
  
end arch;
```

 Suppose the VHDL design above is used to design the following pulse y output based on the clk waveform shown below. The waveform y is a periodic pulse with logic '1' for one clk cycle and logic '0' for four clk cycles. The value for \_\_[blank1]\_\_ is



### Question 9

1 pts

```
library ieee;  
use ieee.std_logic_1164.all;  
use ieee.std_logic_unsigned.all;  
  
entity ram is  
port (  
    address :in  std_logic_vector ( 4 downto 0);  
    data    :inout std_logic_vector ( 1 downto 0);  
    cs     :in  std_logic;  
    we     :in  std_logic;
```



```

    oe    :in    std_logic
  );
end ram;

architecture beh_ram of ram is
type memory is array (0 to 31) of std_logic_vector (1 downto 0);
signal mem : memory ;
begin

  MEM_WRITE:
  process (address, data, cs, we)
  begin
    if (cs = '1' and we = '1') then
      mem(conv_integer(address)) <= data;
    end if;
  end process;

  MEM_READ:
  process (address, cs, we, oe, mem)
  begin
    if (cs = '1' and we = '0' and oe = '1') then
      data <= mem(conv_integer(address));
    else
      data <= (others => 'Z' );
    end if;
  end process;

end beh_ram;

```

The VHDL code above corresponds to a RAM of \_\_\_\_

32 by 2




\_\_\_\_\_



**Question 10**

 **1 pts**

The ASM chart and the corresponding VHDL design are shown below.



```
library ieee;
use ieee.std_logic_1164.all;
entity design1 is
port(
    reset,clk: in std_logic;
    strobe: in std_logic;
    y : out std_logic
);
end design1;

architecture arch of design1 is
    constant S0: std_logic:= '0';
    constant S1: std_logic:= '1';
```

```
signal cs, ns: std_logic;

begin

process (clk, reset)

begin

if reset = '1' then

    cs <= S0;

elsif (rising_edge(clk)) then

    cs <= ns;

end if;

end process;


process(cs, strobe)

begin

case cs is

when S0=> if strobe = '1' then

ns <= S1;

else

ns <= S0;

end if;

when S1=> if strobe = '1' then

ns <= S1;

else

ns <= S0;

end if;

when others=> ns <= S0;

end case;

end process;
```

y <= '1' when \_\_\_\_\_ (cs=S0) and (strobe='1') \_\_\_\_\_ else '0';

end arch;

The above VHDL design is used to detect \_\_\_\_\_ rising edge \_\_\_\_\_ of  
the strobe input.

No new data to save. Last checked at 3:31pm

Submit Quiz