

## Solution Homework-01 EEE 117

Questions 1-5    2 points each

Questions 6-11    15 points each

**Q- 1** The rms value of  $v(t) = V_{\max} \cos(\omega t + \delta)$  is given by  
(a)  $V_{\max}$                       (b)  $V_{\max}/\sqrt{2}$                       (c)  $2 V_{\max}$                       (d)  $\sqrt{2} V_{\max}$

**Q-2** If the rms phasor of a voltage is given by  $V = 120/\underline{60^\circ}$  volts, then the corresponding  $v(t)$  is given by  
(a)  $120\sqrt{2} \cos(\omega t + 60^\circ)$                       (b)  $120 \cos(\omega t + 60^\circ)$   
(c)  $120\sqrt{2} \sin(\omega t + 60^\circ)$

**Q-3** If a phasor representation of a current is given by  $I = 70.7/\underline{45^\circ}$  A, it is equivalent to  
(a)  $100 e^{j45^\circ}$                       (b)  $100 + j100$   
(c)  $50 + j50$

**Q-4** With sinusoidal steady-state excitation, for a purely resistive circuit, the voltage and current phasors are  
(a) in phase  
(b) perpendicular with each other with V leading I  
(c) perpendicular with each other with I leading V.

**Q-5** For a purely inductive circuit, with sinusoidal steady-state excitation, the voltage and current phasors are  
(a) in phase  
(b) perpendicular to each other with V leading I  
(c) perpendicular to each other with I leading V.

<b>Q- 1</b>	<b>b</b>
<b>Q-2</b>	<b>a</b>
<b>Q-3</b>	<b>c</b>
<b>Q-4</b>	<b>a</b>
<b>Q-5</b>	<b>b</b>

**Q-6** Consider the sinusoidal voltage

$$v(t) = 25 \cos(400\pi t + 60^\circ) \text{ V.}$$

- a) What is the maximum amplitude of the voltage?
- b) What is the frequency in hertz?
- c) What is the frequency in radians per second?
- d) What is the phase angle in radians?
- e) What is the phase angle in degrees?
- f) What is the period in milliseconds?
- g) What is the first time after  $t = 0$  that  $v = 0$  V?

<b>a</b>	V <sub>m</sub>	=	25 V
<b>b</b>	f=w/2pi	=	200 Hz
<b>c</b>	w	=	1256.637 radian/s
<b>d</b>	Phase angle	=	1.047198 radian
<b>e</b>	Phase angle	=	60 degree
<b>f</b>	T	=	5 ms
<b>g</b>	t	=	416.67 us

**Q-7** Use the concept of the phasor to combine the following sinusoidal functions into a single trigonometric expression:

a)  $y = 30 \cos(200t - 160^\circ) + 15 \cos(200t + 70^\circ),$

b)  $y = 90 \sin(50t - 20^\circ) + 60 \cos(50t - 70^\circ),$

c)  $y = 50 \cos(5000t - 60^\circ) + 25 \sin(5000t + 110^\circ) - 75 \cos(5000t - 30^\circ),$

d)  $y = 10 \cos(\omega t + 30^\circ) + 10 \sin \omega t + 10 \cos(\omega t + 150^\circ).$

a)

$y =$	-23.06048	+	j	3.83479
$y =$	23.37715	L	170.559	
$y = 23.377 \cos ( 200 t + 170.559 )$				

b)

$y =$	-10.2606	+	j	-140.954
$y =$	141.3269	L	265.837	
$y = 141.33 \cos ( 50 t + 265.837 )$				

c)



$y =$	-16.45959	+	j	2.74923
$y =$	16.68761	L	170.517	
$y = 16.688 \cos ( 5000 t + 170.517 )$				

d)

$y =$	0	+	j	0
$y =$	0	L	0	
$y = 0$				

**Q-8** A  $25\ \Omega$  resistor and a  $10\text{ mH}$  inductor are connected in parallel. This parallel combination is also in parallel with the series combination of a  $30\ \Omega$  resistor and a  $10\ \mu\text{F}$  capacitor. These three parallel branches are driven by a sinusoidal current source whose current is  $125 \sin(2500t + 60^\circ)\text{ A}$ .

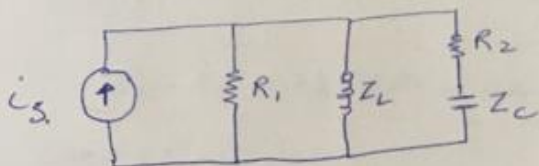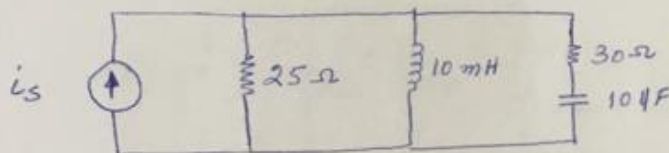- Find total impedance.
- Analyze the circuit and find currents for each component.



$$a) \frac{1}{Z_{eq}} = \frac{1}{R_1} + \frac{1}{Z_L} + \frac{1}{(R_2 + Z_C)}$$

$$\frac{1}{Z_{eq}} = \frac{1}{25 \angle 0} + \frac{1}{25 \angle 90} + \frac{1}{50 \angle -53.13}$$

$$\frac{1}{Z_{eq}} = (0.04 \angle 0) + (0.04 \angle -90) + 0.02 \angle 53.13$$

$$\frac{1}{Z_{eq}} = (0.04 + j0) + (0 - j0.04) + (0.012 + j0.016)$$

$$\frac{1}{Z_{eq}} = 0.052 + j0.024 = 0.05727 \angle -24.775$$

$$Z_{eq} = 17.46 \angle 24.775$$

$$i_s = 125 \sin(2500t + 60^\circ)\text{ A}$$

$$X_L = j\omega L = 2500 \times \frac{10}{1000}$$

$$X_L = 25$$


$$Z_L = 0 + j25 = 25 \angle 90$$

$$X_C = \frac{1}{j\omega C} = \frac{1}{2500 \times 10 \times 10^{-6}}$$

$$X_C = 40$$

$$Z_C = 0 - j40 = 40 \angle -90$$

$$R_2 + Z_C = (30 + j0) + (0 - j40) \\ = 30 - j40 \\ = 50 \angle -53.13^\circ$$

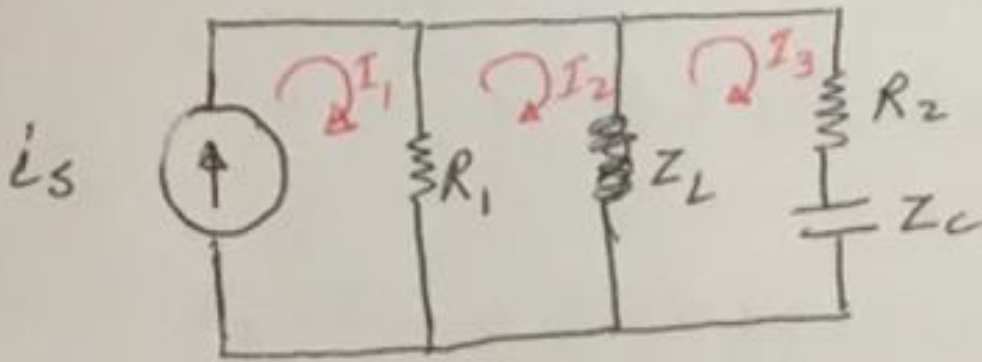

Loop 1:  $i_s = 125 \sin(2500t + 60) = 125 \cos(2500t - 30)$   
 $i_s = 125 \angle -30^\circ = 108.25 - j62.5$

$$I_1 = i_s$$

Loop 2:  $R_1(I_2 - I_1) + Z_L(I_2 - I_3) = 0$   
 $R_1 I_2 - R_1 I_1 + Z_L I_2 - Z_L I_3 = 0$   
 $(R_1 + Z_L)I_2 - Z_L I_3 = R_1 I_1$   
 $(25 + j25)I_2 - (0 + j25)I_3 = (2706.33 - j1562.5) \quad \text{--- (1)}$

Loop 3:  $Z_L(I_3 - I_2) + (R_2 + Z_C)I_3 = 0$   
 $-Z_L I_2 + (R_2 + Z_L + Z_C)I_3 = 0$   
 $(0 - j25)I_2 + (30 - j15)I_3 = 0 \quad \text{--- (2)}$

Solve eq (1) & (2) we get

$$I_2 = 21.31 - j54.55$$

$$I_3 = 29.26 + j32.39$$

$$I_{R_1} = I_1 - I_2 = 86.94 - j7.95 = 87.303 \angle -5.224^\circ \text{ A}$$



$$I_L = I_2 - I_3 = -7.95 - j86.94 = 87.303 \angle 264.775^\circ \text{ A}$$

$$I_{(R_2 + C)} = I_3 = 29.26 + j32.39 = 43.65 \angle 47.91^\circ \text{ A}$$



**Q-9** For the circuit shown below.

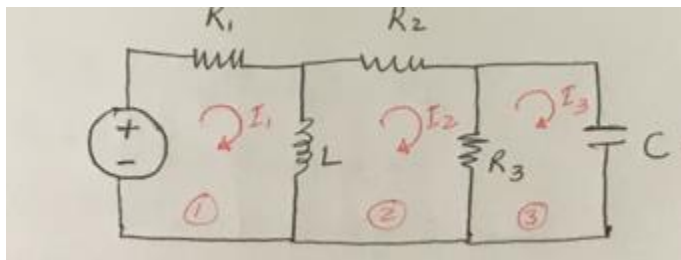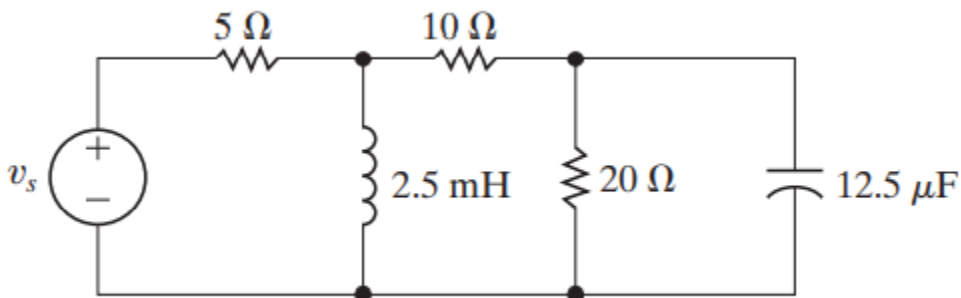- c) Find total impedance.
- d) Analyze the circuit and find currents for each component.  
if  $v_s = 25 \cos 4000t$  V.



$$V_s = 25 \angle 0 = 25 + j0$$

$$R_1 = 5 \Omega = 5 \angle 0 = 5 + j0$$

$$R_2 = 10 \Omega = 10 \angle 0 = 10 + j0$$

$$R_3 = 20 \Omega = 20 \angle 0 = 20 + j0$$

$$L = 2.5 \text{ mH} \Rightarrow X_L = \omega L = 4000 \times 2.5 \times 10^{-3} = 10 \Omega$$

$$Z_L = 10 \angle 90 = 0 + j10$$

$$C = 12.5 \mu\text{F} \Rightarrow X_C = \frac{1}{\omega C} = \frac{1 \times 10^6}{4000 \times 12.5} = 20 \Omega$$

$$Z_C = 20 \angle -90 = 0 - j20$$

Total Impedance:

$$Z_x = \left( \frac{Z_C \times R_3}{Z_C + R_3} \right) + R_2 = \left[ \frac{(20 \angle -90)(20 \angle 0)}{(20 - j20)} \right] + (10 + j0)$$

$$Z_x = \left( \frac{400 \angle -90}{28.28 \angle -45} \right) + (10 + j0) = (14.14 \angle -45) + (10 + j0)$$

$$Z_x = (10 - j10) + (10 + j0) = (20 - j10) = 22.36 \angle -26.56$$

$$Z_T = \left( \frac{Z_L \times Z_x}{Z_L + Z_x} \right) + R_1 = \left[ \frac{(10 \angle 90)(22.36 \angle -26.56)}{(0 + j10) + (20 - j10)} \right] + (5 + j0)$$

$$Z_T = \left( \frac{220.36 \angle 63.44}{20 + j0} \right) + (5 + j0) = (11.02 \angle 63.44) + (5 + j0)$$

$$Z_T = (4.927 + j9.857) + (5 + j0)$$

$$Z = 9.927 + j9.857 \approx 13.99 \angle 44.8^\circ$$

Loop 1:

$$R_1 I_1 + Z_L(I_1 - I_2) = V_s$$

$$(R_1 + Z_L)I_1 - Z_L I_2 = V_s$$

$$(5 + j10)I_1 - (0 + j10)I_2 = 25 + j0$$

$$(5 + j10)I_1 + (0 - j10)I_2 = 25 + j0 \quad \text{--- (1)}$$

Loop 2:

$$Z_L(I_2 - I_1) + R_2 I_2 + R_3(I_2 - I_3) = 0$$

$$-Z_L I_1 + (R_2 + R_3 + Z_L)I_2 - R_3 I_3 = 0$$

$$-(0 + j10)I_1 + (30 + j10)I_2 - (20 + j0)I_3 = 0$$

$$(0 - j10)I_1 + (30 + j10)I_2 + (-20 + j0)I_3 = 0 \quad \text{--- (2)}$$

Loop 3:



Loop 3:

$$R_3(I_3 - I_2) + Z_C I_3 = 0$$

$$-R_3 I_2 + (R_3 + Z_C) I_3 = 0$$

$$-(20 + j0) I_2 + (20 - j20) I_3 = 0$$

$$(-20 + j0) I_2 + (20 - j20) I_3 = 0 \quad \text{--- (3)}$$

Solve these equations we get

$$I_1 = 1.25 - j1.25 = 1.767 \angle -45^\circ$$

$$I_2 = 0.625 + j0.625 = 0.883 \angle 45^\circ$$

$$I_3 = 0 + j0.625 = 0.625 \angle 90^\circ$$



$$I_{R_1} = I_1, \quad I_{R_2} = I_2, \quad I_C = I_3$$

$$I_L = I_1 - I_2 = 0.625 - j1.875 = 1.976 \angle -71.56^\circ$$

$$I_{R_3} = I_2 - I_3 = 0.625 + j0 = 0.625 \angle 0^\circ$$

**Q-10** Analyze the circuit and find currents for each component.

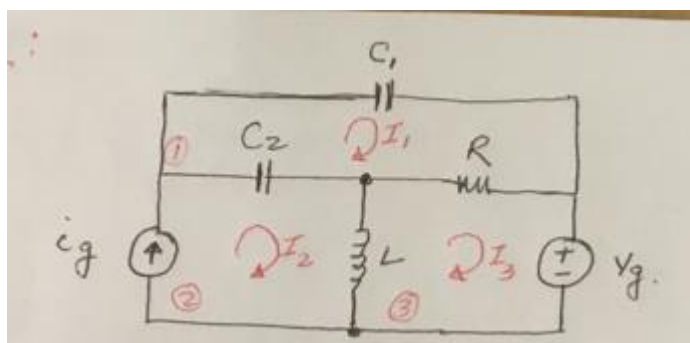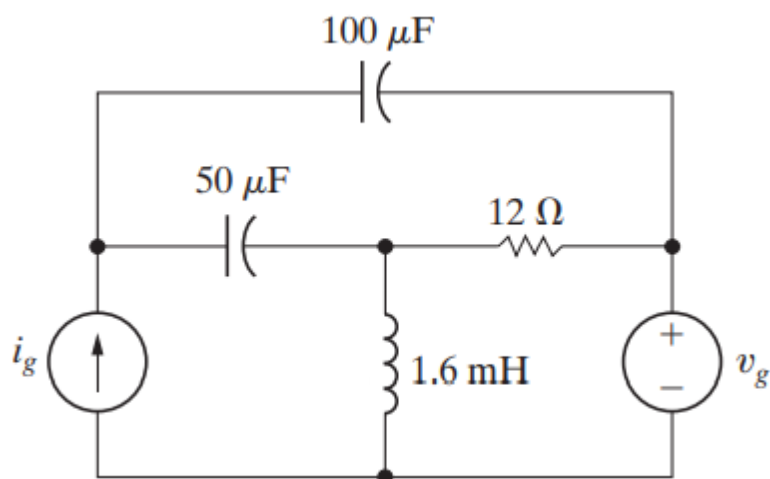if  $i_g = 5 \cos 2500t$  A and  $v_g = 20 \cos (2500t + 90^\circ)$  V.



$$\begin{aligned}
 i_g &= 5 \cos 2500t = 5 \angle 0 = 5 + j0 \text{ A} \\
 v_g &= 20 \cos(2500t + 90) = 20 \angle 90 = 0 + j20 \text{ V} \\
 R &= 12 \Omega = 12 \angle 0 = 12 + j0 \\
 C_1 &= 100 \mu\text{F} \Rightarrow X_{C_1} = \frac{1}{\omega C} = \frac{1 \times 10^6}{2500 \times 100} = 4 \Omega \\
 Z_{C_1} &= 4 \angle -90 = 0 - j4 \\
 C_2 &= 50 \mu\text{F} \Rightarrow X_{C_2} = \frac{1}{\omega C} = \frac{1 \times 10^6}{2500 \times 50} = 8 \Omega \\
 Z_{C_2} &= 8 \angle -90 = 0 - j8 \\
 L &= 1.6 \text{ mH} \Rightarrow X_L = \omega L = 1.6 \times 10^{-3} \times 2500 = 4 \Omega \\
 Z_L &= 4 \angle 90 = 0 + j4
 \end{aligned}$$

Loop 1:

$$Z_{C_1} I_1 + R(I_1 - I_3) + Z_{C_2}(I_1 - I_2) = 0$$

$$(R + Z_{C_1} + Z_{C_2})I_1 - Z_{C_2}I_2 - RI_3 = 0$$

$$[(12+j0) + (0-j4) + (0-j8)]I_1 - (0-j8)I_2 - (12+j0)I_3 = 0$$

$$(12-j12)I_1 + (0+j8)I_2 + (-12+j0)I_3 = 0 \quad \text{--- (1)}$$

Loop 2:

$$I_2 = i_g = 5\angle 0 = 5+j0$$

Loop 3:

$$Z_L(I_3 - I_2) + R(I_3 - I_1) = -V_g$$

$$-RI_1 - Z_L I_2 + (R + Z_L)I_3 = -V_g$$

$$RI_1 + Z_L I_2 - (R + Z_L)I_3 = V_g$$

$$(12+j0)I_1 + (4\angle 90)(5\angle 0) - (12+j0+0+j4)I_3 = 0+j20$$

Since  $I_2 = i_g$  so

$$(12+j0)I_1 + 20\angle 90 - (12+j4)I_3 = (0+j20)$$

$$(12+j0)I_1 + (-12-j4)I_3 = (0+j20) - (0+j20)$$

$$(12+j0)I_1 + (-12-j4)I_3 = 0 \quad \text{--- (2)}$$

Put the value of  $I_2$  in eq ① we get.

$$(12 - j12)I_1 + (8 \angle 90)(5 \angle 0) + (-12 - j0)I_3 = 0$$

$$(12 - j12)I_1 + (-12 - j0)I_3 = -40 \angle 90$$

$$(12 - j12)I_1 + (-12 - j0)I_3 = 0 - j40 \quad \text{--- ③}$$

Solve eq ② & eq ③ for  $I_1$  &  $I_3$  we get.

$$I_1 = 4.66 - j0.666 = 4.713 \angle -8.125$$

$$I_3 = 4 - j2 = 4.472 \angle -26.56$$

$$I_{C1} = I_1 = 4.66 - j0.666 = 4.713 \angle -8.125$$

$$I_{C2} = -I_2 + I_1 = (5 + j0) + (4.66 - j0.666)$$

$$= -0.34 - j0.666 = 0.747 \angle 242.95$$


$$I_R = I_1 - I_3 = (4.66 - j0.666) - (4 - j2)$$

$$= 0.66 + j1.334 = 1.488 \angle 63.67$$

$$I_L = I_2 - I_3 = (5 + j0) - (4 - j2)$$

$$= 1 + j2 = 2.236 \angle 63.43$$

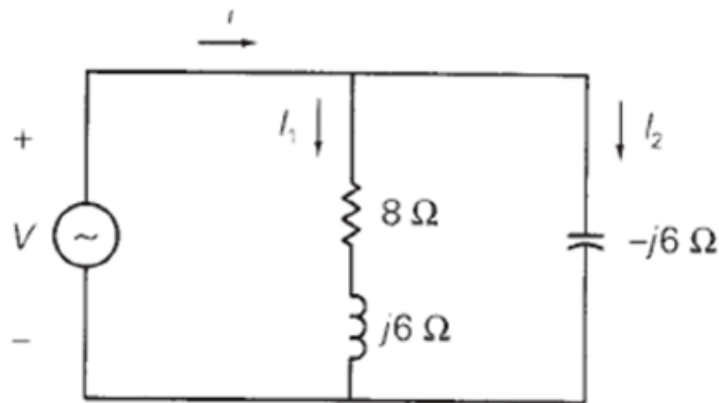**Q-11** In the figure shown below,  $\bar{I} = 10\angle 0^\circ \text{ A}$ , compute the phasors  $\bar{I}_1$ ,  $\bar{I}_2$  and  $\bar{V}$ .



Q-11

$\bar{I} = 10 + 0j = 10\angle 0^\circ \text{ A}$   
 $R = 8 + 0j = 8\angle 0^\circ \Omega$   
 $Z_L = 0 + j6 = 6\angle 90^\circ \Omega$   
 $Z_C = 0 - j6 = 6\angle -90^\circ \Omega$   
 $Z_1 = R + Z_L = 8 + j6 = 10\angle 36.87^\circ \Omega$

$Z_T = \frac{Z_1 \times Z_C}{Z_1 + Z_C} = \frac{(10\angle 36.87^\circ)(6\angle -90^\circ)}{(8 + j6) + (0 - j6)} = 7.5\angle -53.13^\circ \Omega$

$\bar{V} = \bar{I} Z_T = (10\angle 0^\circ)(7.5\angle -53.13^\circ) = 75\angle -53.13^\circ \text{ V}$

$\bar{I}_1 = \frac{\bar{V}}{Z_1} = \frac{75\angle -53.13^\circ}{10\angle 36.87^\circ} = 7.5\angle -90^\circ \text{ A}$

$\bar{I}_2 = \frac{\bar{V}}{Z_C} = \frac{75\angle -53.13^\circ}{6\angle -90^\circ} = 12.5\angle 36.87^\circ \text{ A}$