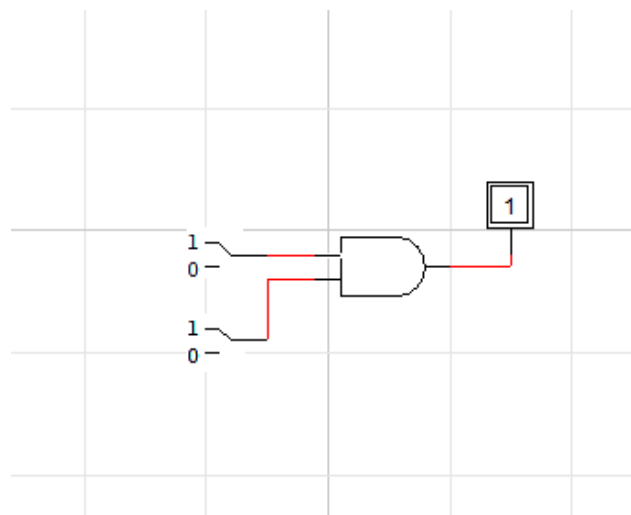


Part 1: Simulation of AND gate with Binary switches and Binary Probe.



Part 2. Simulation for D Flip Flop with a binary switch and Clock.

