

**California State University, Sacramento**  
**The College of Engineering and Computer Science**

**CPE 166 Advanced Logic Design**

Final Exam Part 2

Fall 2022

Student Name: **Vigomar Kim Algador**

Part 2.1. [15 points ] Fill out the 2 tables below.

	<p>Redesign the circuit on the left of this table with resource sharing strategy using only 1 adder. Draw the equivalent circuit diagram below.</p>
--	---

Draw the synthesized schematics for the following Verilog codes.

```

reg m, w;
wire a, b, c, d, e, s;


assign d = ~a & b | c ;

always@(posedge clk)
begin
    m <= d;
end

always @( s or m or d or e )
begin
    if(s)
        w = m;
    else
        w = d & e;
end

```

**Your Schematic:**

 

**Part 2.2** [15 points] An SRAM has **8-bit** databus and **5-bit** address bus. The SRAM function table is shown below:

WE	CS	OE	I/O	Function
X	L	X	High-Z	Standby
L	H	L	High-Z	Output Disabled
L	H	H	Data	Read Data
H	H	X	Data	Write Data

The CS, WE, and OE signals in the above function table are high active. Design the above SRAM in **VHDL**

```
library ieee;
use ieee.std_logic_1164.all;
use ieee.std_logic_unsigned.all;
```

```
entity ram is
port (    address : in std_logic_vector (4 downto 0) ;
        data    : inout std_logic_vector (7 downto 0) ;
        cs      : in std_logic ;
        we      : in std_logic ;
        oe      : in std_logic );
```

```
end ram;
architecture beh_ram of ram is
```

```
type memory is array (0 to 31) of std_logic_vector (7 downto 0);
signal mem: memory;
begin
    MEM_WRITE:
    process (address, data, cs, we) begin
        if (cs = '1' and we = '1') then
            mem(conv_integer(address)) <= data;
        end if;
    end process;
    MEM_READ:
    process (address, cs, we, oe, mem) begin
        if (cs = '1' and we = '0' and oe = '1') then
            data <= mem(conv_integer(address));
        else
            data <= (others => 'Z' );
        end if;
    end process;
end beh_ram;
```

**Part2.3.** [25 points] Implement a **VHDL** design, which writes “11100111” to all of the address locations of the SRAM you designed in question 4. Use SRAM you designed in question 4 as one component in your question 5 design.

### FSM DESIGN

```
library ieee;
use ieee.std_logic_1164.all;
```

```
entity mem_fsm is
port( clk, reset: in std_logic;
      address: out std_logic_vector (4 downto 0);
      data: inout std_logic_vector (7 downto 0);
      cs, we, oe: out std_logic );
end mem_fsm;
```

```
architecture beh of mem_fsm is
type state_type is (s0, s1, s2, s3, s4);
signal state : state_type;
begin
```

```
process (clk, reset) begin
  if reset = '1' then
    state <= s0;
  elsif (rising_edge(clk)) then
    case state is
      when s0 =>
        state <= s1;
        address <= 0;
      when s1 =>
        state <= s2;
        address <= 0;
      when s2 =>
        address <= address + 1;
        if (address == 32)
          state <= s3;
        else
          state <= s2;
        end if;
      when s3 =>
        state <= s4;
        address <= 0;
```

```
      when s4 =>
        address <= address + 1;
        if (address == 32)
          state <= s0;
        else
          state <= s4;
        end if;
      when others =>
        state <= s0;
        address <= 0;
    end case;
  end if;
end process;
```

```
process (state) begin
  case state is
    when s0 =>
      cs <= 0; we <= 0; oe <= 0;
      data <= 4'bzzzzzzzz;
    when s2 =>
      cs <= 1; we <= 1; oe <= 0;
      data <= 4'b11100111;
    when s3 =>
      cs <= 1; we <= 0; oe <= 1;
      data <= 4'b11100111;
    when s4 =>
      cs <= 1; we <= 0; oe <= 1;
      data <= 4'b11100111;
    when others =>
      cs <= 0; we <= 0; oe <= 0;
      data <= 4'bzzzzzzzz;
  end case;
end process;
end beh;
```

## TOP DESIGN

```
library ieee;  
use ieee.std_logic_1164.all;
```

```
entity top is  
port( clk, reset: in std_logic;  
      address: out std_logic_vector (4 downto 0);  
      data: out std_logic_vector (7 downto 0);  
      cs, we, oe: out std_logic );  
end top;
```

architecture behavioral of top is

```
component ram  
port ( address: in std_logic_vector (4 downto 0) ;  
      data: inout std_logic_vector (7 downto 0) ;  
      cs, we, oe: in std_logic );  
end component;
```

```
component mem_fsm  
port( clk, reset: in std_logic;  
      address: out std_logic_vector (4 downto 0);  
      data: inout std_logic_vector (7 downto 0);  
      cs, we, oe: out std_logic );  
end component;
```

```
begin  
  g1: ram port map (address, data, cs, we, oe);  
  g2: mem_fsm port map (clk, reset, address, data, cs, we, oe);  
end behavioral;
```